

## E1.4 SOLUTIONS

### Solution 1


a) Assuming  $V_{DD}$  is sufficiently large for the MOSFET to be active, the drain current will be  $I_D = K(V_{GS} - V_t)^2 = K(-V_S - V_t)^2$ . The same current flows in the source resistor  $R_S$ , so we also have  $V_S = I_D R_S$ . Combining these equations we find  $V_S$  satisfies:

$$V_S^2 + (2V_t - 1/KR_S)V_S + V_t^2 = 0 \quad \text{or} \quad 4V_S^2 - 13V_S + 9 = 0$$

The roots are  $V_S = 1$  V,  $9/4$  V, and we can reject the latter because it implies a sub-threshold value for  $V_{GS}$ . With  $V_S = 1$  V, we have  $(V_{GS} - V_t) = 0.5$  V and  $I_D = K(0.5)^2 = 0.05$  mA.

At the minimum  $V_{DD}$ , the MOSFET will be at pinch-off, with  $V_{DS} = 0.5$  V. The drain voltage will be  $V_D = V_S + V_{DS} = 1.5$  V, and the supply voltage will be  $V_{DD} = V_D + I_D R_D$ . With  $V_D = 1.5$  V,  $I_D = 0.05$  mA and  $R_D = 56$  k $\Omega$ , this gives  $V_{DD} = 4.3$  V. [6]

b)

 

Ignoring base current, KVL in the loop including  $R$  and the EBJs gives:

$$V_{BE1} = V_{BE2} + I_{OUT}R$$

Using the reduced Ebers-Moll eqn we can express the  $V_{BE}$ s in terms of the input and output currents:

$$V_T \ln(I_{IN}/I_S) = V_T \ln(I_{OUT}/I_S) + I_{OUT}R$$


Cleaning this up gives:

$$V_T \ln(I_{IN}/I_{OUT}) = I_{OUT}R \quad \text{or} \quad I_{IN} = I_{OUT} \exp(I_{OUT}R/V_T)$$

Rearranging the above equation, the value of  $R$  is given by  $R = V_T \ln(I_{IN}/I_{OUT})/I_{OUT}$ . With  $I_{IN} = 100$   $\mu$ A,  $I_{OUT} = 10$   $\mu$ A,  $V_T = 25$  mV, this gives  $R = 5.76$  k $\Omega$ . [6]

c)

SSEC (helpful but not req'd):

 

The (signal) base-emitter voltages of the two transistors are:

$$v_{be1} = i_{b1} r_{be1} \quad ; \quad v_{be2} = i_{b2} r_{be2}$$

and the sum of these is the input voltage at the B terminal, i.e.  $v_{be1} + v_{be2} = v_{in}$ .

From the SSEC we can see that  $i_{b2} = (1 + \beta_1)i_{b1}$ . The quiescent base currents also satisfy  $I_{B2} = (1 + \beta_1)I_{B1}$ , so  $r_{be2} = V_T/I_{B2} = r_{be1}/(1 + \beta_1)$ . It follows that  $i_{b2} r_{be2} = i_{b1} r_{be1}$  and hence that  $v_{be2} = v_{be1} = v_{in}/2$  as required. [5]

The total collector current is  $i_c = g_{m1}v_{be1} + g_{m2}v_{be2} = (g_{m1} + g_{m2})v_{in}/2 = (I_{C1} + I_{C2})v_{in}/(2V_T)$ . But  $I_{C1} + I_{C2}$  is the total collector bias current, so  $i_c = I_C v_{in}/(2V_T)$ , and the transconductance is  $g_m = i_c/v_{in} = I_C/(2V_T)$  which is half that of a BJT. [3]

d) Both MOSFETs are enhancement mode and diode-connected, and  $V_{DD} > V_{IN} + |V_{IP}|$  so we know both devices are active. We can therefore write:

$$I_D = K_N(V - V_{IN})^2 = K_P(V - 3 - V_{IP})^2$$

Taking the -ve square root (to ensure opposite polarity devices are both above threshold), and rearranging, we obtain:

$$V = [3 + V_{IP} + \sqrt{(K_N/K_P)V_{IN}}]/[1 + \sqrt{(K_N/K_P)}] = [2 + \sqrt{(5/2)}]/[1 + \sqrt{(5/2)}] \Rightarrow V = 1.39 \text{ V.} \quad [6]$$

e) With Class B, there is a dead-band at low signal levels where neither transistor is conducting (conduction angle  $< 180^\circ$ ), and this gives rise to cross-over distortion. The advantage is that the power consumption is low (~zero under quiescent conditions).

With Class AB, the transistors are biased so that there is a small overlap in the conduction (conduction angle  $> 180^\circ$ ), with both transistors conducting at low signal levels. The cross-over distortion is significantly reduced, but the power consumption is higher.

Class A has both transistors conducting at all times (conduction angle =  $360^\circ$ ) so there is no cross-over distortion; however, the power consumption is very high. [6]

f) For  $t < 0$ , the transistor is conducting, with  $I_B = (5 - 0.7)/220k = 19.5 \mu\text{A}$ . The circuit is in steady state, so the capacitor carries no current and, since  $\beta I_B > V_{CC}/R_C$  ( $3.91 \text{ mA} > 2.5 \text{ mA}$ ), we know the transistor is saturated. We therefore have  $V_{OUT} = V_{CAP} = 0.2 \text{ V}$  at  $t = 0^-$ .

The transistor switches off at  $t = 0$ , and the capacitor starts to charge up via the two series resistors. The new steady-state value for  $V_{CAP}$  is  $+5 \text{ V}$ , so the trajectory for  $V_{CAP}$  is:

$$V_{CAP} = 5 + (0.2 - 5)\exp(-t/\tau) = 5 - (4.8)\exp(-t/\tau)$$

where  $\tau = (1k + 2k) \times 5n = 15 \mu\text{s}$  is the time constant. Since  $V_{OUT} = (2V_{CAP} + V_{CC})/3$ , the corresponding trajectory for  $V_{OUT}$  is:

$$V_{OUT} = 5 - (3.2)\exp(-t/\tau)$$

$V_A$  is the value of  $V_{OUT}$  at  $t = 0^+$  which is  $V_A = 1.8 \text{ V}$ .

$V_B$  is the value of  $V_{OUT}$  at  $t = 20 \mu\text{s}$  which is  $V_B = 5 - (3.2)\exp(-20/15) = 4.16 \text{ V.} \quad [5]$

From the graph it is clear that when the transistor is switched on again at  $t = 20 \mu\text{s}$  it is initially in active mode. In this case, the value of  $V_{OUT}$  at  $t = 20^+ \mu\text{s}$  will be that of a Thévenin source with o/c voltage  $4.16 \text{ V}$  and source resistance  $1k/2k = 667 \Omega$  loaded by a current of  $\beta I_B = 3.91 \text{ mA}$ . So,  $V_C = 4.16 - 3.91m \times 667 = 1.55 \text{ V.} \quad [3]$

## Solution 2

a) With the configuration shown, the quiescent emitter current is set by the bias current source, so we can write:


$$I_E = (1 + \beta)I_B = (1 + \beta)(V_{OUT} - V_{BE})/R_F = I_{BIAS} \Rightarrow R_F = (1 + \beta)(V_{OUT} - V_{BE})/I_{BIAS}$$

With  $V_{OUT} = 4$  V,  $I_{BIAS} = 1$  mA (neglecting  $r_c$ ),  $\beta = 200$ , and assuming  $V_{BE} \approx 0.7$  V, this gives  $R_F = 663$  k $\Omega$ . [4]

Rearranging the above equation gives  $V_{OUT} = R_F I_{BIAS}/(1 + \beta) + V_{BE}$ . With  $\beta = 300$  this gives  $V_{OUT} = 2.90$  V, and with  $\beta = 100$  it gives  $V_{OUT} = 7.26$  V. [2]

The sensitivity of  $V_{OUT}$  to  $\beta$  variation could be reduced by adding a resistor between the base and ground, chosen so that it carries a current comparable to or larger than  $I_B$ . [2]

b) SSEC:

 

Applying KCL at the output node:

$$g_m v_{in} + v_{out}/r_o + v_{out}/r_c + (v_{out} - v_{in})/R_F = 0$$

$$\Rightarrow A_v = v_{out}/v_{in} = -(g_m - 1/R_F)(r_o//r_c//R_F)$$

$$\text{Putting } g_m = I_C/V_T = 40 \text{ mS}, r_c = 120 \text{ k}\Omega$$

$$r_o = V_A/I_C = 100 \text{ k}\Omega \Rightarrow A_v = -2016.$$

[6 (SSEC) + 3]

Applying KCL at the input node, the input current is:

$$i_{in} = v_{in}/r_{be} + (v_{in} - v_{out})/R_F = v_{in}[1/r_{be} + (1 - A_v)/R_F]$$

The input resistance is therefore  $R_{in} = v_{in}/i_{in} = r_{be}/[R_F/(1 - A_v)]$ . With  $r_{be} = \beta/g_m = 5$  k $\Omega$  and  $R_F/(1 - A_v) = 663\text{k}/2017 = 329$   $\Omega$  gives  $R_{in} = (5\text{k}/329) = 309$   $\Omega$ . [3]

c) At signal frequencies, where the capacitor has negligible impedance, the feedback resistor in the original SSEC is replaced by shunt resistors of  $R_F/2$  at the input and output. The voltage gain and input resistance will now be given by:

$$A_v = -g_m(r_o//r_c//R_F/2) = -0.04 \times 46.8\text{k} = -1872$$

$$R_{in} = r_{be}/(R_F/2) = 4.96 \text{ k}\Omega$$

The input resistance has increased from 309  $\Omega$  to  $\sim 5$  k $\Omega$ . [6]

d) With the modified feedback network in place, the input resistance is dominated by the base-emitter resistance of the transistor. This can be increased by adding an emitter follower before the amplifying transistor or by converting the amplifying transistor to a Darlington pair. [Other solutions are also acceptable, e.g. source follower.] [4]

### Solution 3

a) Since Q3 & Q4 are matched, we know  $I_{D3} = I_{D4} = I$ , so we can determine the gate/drain voltage of Q3 from:

$$I = K(V_{G3} + 10 - V_t)^2 \Rightarrow V_{G3} = -10 + V_t + \sqrt{I/K}$$

where we have taken the +ve square root to ensure Q3, Q4 are above threshold. With  $I = 0.25 \text{ mA}$ ,  $K = 0.5 \text{ mA/V}^2$ ,  $V_t = 1 \text{ V}$ , this gives  $V_{G3} = -9 + 1/\sqrt{2} = -8.3 \text{ V}$ . We then obtain the value of  $R_{BIAS}$  as  $R_{BIAS} = -V_{G3}/I = 8.3 \text{ k}\Omega$ . [4]


Under quiescent conditions, with  $V_{IN1} = V_{IN2}$ , we have  $I_{D1} = I_{D2} = I/2 = 0.125 \text{ mA}$ . For a quiescent output voltage of +5 V we require  $R_D = (10 - 5)/0.125\text{m} = 40 \text{ k}\Omega$ . [2]

Under quiescent conditions Q1 and Q2 have  $V_{GS} = V_t + \sqrt{I/2K} = 1.5 \text{ V}$ . The voltage at the drain of Q4 is  $V_{D4} = V_{IN} - V_{GS}$  so, when  $V_{IN} = 0$  we have  $V_{D4} = -1.5 \text{ V}$ . [2]

b) Upper limit: Q2 will remain active while  $V_{D2} \geq V_{IN2} - V_t$  (and similarly for Q2). For the CMVR calculation we assume  $V_{IN1} = V_{IN2} = V_{IN}$ , in which case  $V_{D2} = 5 \text{ V}$  while Q2 remains active, and the above inequality becomes  $V_{IN} \leq 6 \text{ V}$ . [3]

Lower limit: Q4 will remain active while  $V_{D4} \geq V_{G4} - V_t$ . From part a) we know that  $V_{G4} = (-9 + 1/\sqrt{2}) \text{ V}$ , so the above inequality becomes  $V_{D4} \geq (-10 + 1/\sqrt{2})$ . We also know from part a) that Q1 and Q2 have  $V_{GS} = 1.5 \text{ V}$ , so the corresponding inequality for  $V_{IN}$  is  $V_{IN} \geq (-8.5 + 1/\sqrt{2}) \text{ V}$  or  $V_{IN} \geq -7.8 \text{ V}$ . [3]

c) SSEC:

 

From the symmetry of the circuit, when a purely differential voltage is applied there will be zero signal voltage at the source of Q1,Q2, i.e.  $v_s = 0$  when  $v_{in1} = -v_{in2} = v_d/2$ . We can therefore analyse the RH half-circuit as a CE amplifier. Applying KCL at the output, the output voltage is obtained as:

$$v_{out} = g_m(R_D//r_o)v_d/2 \\ \Rightarrow A_d = v_{out}/v_d = g_m(R_D//r_o)/2$$

[6 (SSEC) + 3]

Q2 has  $I_D = 0.125 \text{ mA}$ , so  $g_m = 2\sqrt{KI_D} = 0.5 \text{ mA/V}$ ,  $r_o = V_A/I_D = 800 \text{ k}\Omega$ , giving  $A_d = 9.5$ . [3]

d) The maximum gain will be achieved when the current mirror is used to couple Q1's drain current across to the output side. This will give a  $2\times$  enhancement of the gain. Also,  $R_D$  will be replaced by  $r_o$  in the gain expression, so we will have  $A_d = 2\times g_m(r_o//r_o)/2 = g_m r_o/2$ .

With  $g_m = 0.5 \text{ mA/V}$  and  $r_o = 800 \text{ k}\Omega$  this gives  $A_d = 200$ . [4]