

VHDL 2007 SOLUTIONS
A=Analysis, D = Design, B = Bookwork

Question 1 is COMPULSORY, and constitutes 40% of marks, 72 minutes time, 15 minutes per part.

Solution to Question 1.

1.

a)

(i) P1 inverts z on every edge of clk. It is therefore not synthesisable, since flip-flops must trigger on one edge not both.

(ii) P2 has identical semantics to a positive edge triggered T flip-flop, so it synthesises.

[4A]

b)

```
--from question
ENTITY ram IS
PORT(
    write, clk: IN std_logic;
    addr: IN std_logic_vector(3 DOWNTO 0);
    din: IN std_logic(7 DOWNTO 0);
    dout: OUT std_logic_vector(7 DOWNTO 0)
);
END ram;


ARCHITECTURE synth OF ram IS
    TYPE ramtype IS ARRAY (0 TO 15) OF std_logic_vector( 7 DOWNTO 0);
    SIGNAL ramloc : ramtype;
BEGIN
    dout <= ramloc(conv_integer(unsigned(addr)));

    P1: PROCESS
    BEGIN
        WAIT UNTIL clk'EVENT AND clk='1';
        IF write = '1' THEN
            ramloc(conv_integer(unsigned(addr)))<=din;
        END IF;
    END PROCESS P1;
END ARCHITECTURE synth;
```

[4D]


VHDL 2007 SOLUTIONS
A=Analysis, D = Design, B = Bookwork

c)

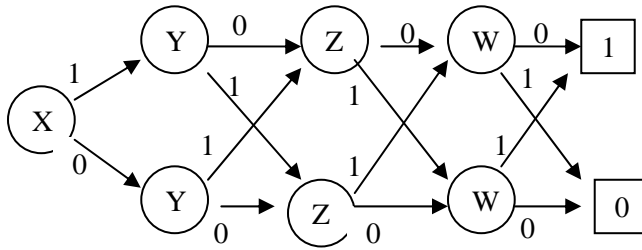

[4B]

d)

 

[4A]

VHDL 2007 SOLUTIONS
A=Analysis, D = Design, B = Bookwork

e)

```
--from question
ENTITY iobuf IS
    PORT(dir,clk:IN std;
          za,zb:INOUT std_logic
    );
END iobuf;

ARCHITECTURE synth OF iobuf IS
    SIGNAL za_del, zb_del: std_logic;
BEGIN

P1: PROCESS
BEGIN
    WAIT UNTIL clk'EVENT AND clk='1';
    za_del <= za;
    zb_del <= zb;
END PROCESS P1;

P2: PROCESS(dir, za_del, zb_del)
BEGIN
    WAIT UNTIL clk'EVENT AND clk='1';
    IF dir='1' THEN
        zb <= za_del; za <= 'Z';
    ELSE
        za <= zb_del; zb <= 'Z';
    END IF;
END PROCESS P2;

END synth;
```

[4D]

VHDL 2007 SOLUTIONS
A=Analysis, D = Design, B = Bookwork

Students must answer two questions from questions 2-4, each question carries 30% of marks and takes 54 minutes.

Solution to Question 2

3.

a)

Must be in a package, so:

```
PACKAGE mypak IS
SUBTYPE word IS std_logic_vector(15 DOWNT0 0);
END PACKAGE;
```

[3B]

b)

```
ENTITY tram IS
PORT(
    din: IN word;
    dout: OUT word;
    clk, write: IN std_logic;
    addr: In std_logic_vector(3 DOWNT0 0)
);
END tram;
```

[2B]

VHDL 2007 SOLUTIONS
A=Analysis, D = Design, B = Bookwork

c)

```
ARCHITECTURE synth OF transpose IS
    TYPE fsmtype IS (state1, state2, state3);
    SIGNAL state: fsmtype;
    SIGNAL regs: word;
    SIGNAL write, wen, dsel, asel: std_logic;
    SIGNAL data, adata : word;
    SIGNAL count, addr : STD_LOGIC_VECTOR(3 DOWNTO 0);

BEGIN

    I1: ENTITY tram PORT MAP(datain, dataout, clk, write, addr);

    ALU : PROCESS
    BEGIN
        WAIT UNTIL clk'EVENT AND clk = '1';
        IF state=state2 THEN
            regs <= SIGNED(regs)+SIGNED(data);
        END IF;
        IF reset='1' THEN regs<= (OTHERS=>'0'); END IF;
    END PROCESS ALU;

    COUNT : PROCESS
    BEGIN
        WAIT UNTIL clk'EVENT AND clk = '1';
        IF reset='1' OR state=state3 THEN
            count <= "0000";
        ELSE
            count <= UNSIGNED(count) + 1;
        END IF;
    END PROCESS COUNT;

    MUX : PROCESS(state, data, adata, count)
    BEGIN
        IF state=state3 THEN dataout <= adata; ELSE dataout <=data; END IF;
        addr <= count;
        IF state=state2 THEN
            addr <= (count(1), count(0), count(3), count(2));
        END IF;
    END PROCESS MUX;

    FSM : PROCESS
    BEGIN
        WAIT UNTIL clk'EVENT AND clk='1';
        IF reset THEN state <= state1;
        ELSE
            IF count=std_logic_vector("1111") THEN
                CASE state IS
                    WHEN state1 => state <= state2;
                    WHEN state2 => state <= state3;
                END CASE;
            END IF
        END IF;
    END PROCESS FSM;

END ARCHITECTURE synth;  -- of transpose
```

[15D]

VHDL 2007 SOLUTIONS
A=Analysis, D = Design, B = Bookwork

Solution to Question 3

a)

```
FUNCTION roundn(n: INTEGER; x: SIGNED) RETURN SIGNED IS
VARIABLE xx:SIGNED(x'LENGTH DOWNT0 1);
CONSTANT zeros: SIGNED(N DOWNT0 1):= (OTHERS => '0');
BEGIN
  xx := x;
  xx := signed(xx)+ unsigned(xx(n) & zeros);
  FOR i IN n DOWNT0 1 LOOP xx(i) := '0'; END LOOP;
  RETURN xx;
END;
```

[4D]

b) cb , ca , $cb+cb^2$, $ca+ca^2$. The circuit computes the Mandelbrot recurrence for two values of c in parallel.

[4D]

c)

```
TYPE complex IS ARRAY (1 DOWNT0 0) OF SIGNED(m-1 DOWNT0 0);
(Element type could be std_logic_vector)
```

[2B]

VHDL 2007 SOLUTIONS
A=Analysis, D = Design, B = Bookwork

d)

```
ARCHITECTURE synth OF mandelbrot IS
    SIGNAL z_int, c : complex;
    SIGNAL zii, zir, zrr : SIGNED(2*m-1 DOWNT0 0);
    SIGNAL count      : STD_LOGIC;

    FUNCTION roundn(n: INTEGER; x: SIGNED) return SIGNED IS
    VARIABLE xx:SIGNED(x'LENGTH DOWNT0 1);
    CONSTANT zeros: SIGNED(N DOWNT0 1):= (OTHERS => '0');
    BEGIN
        xx := x;
        xx := signed(xx)+ unsigned(xx(n) & zeros);
        FOR i IN n DOWNT0 1 LOOP xx(i) := '0'; END LOOP;
        RETURN xx;
    END;

BEGIN
    P1: PROCESS
    BEGIN
        zrr <= z_int(0)*z_int(1);
        zii <= z_int(1)*z_int(1);
        zir <= z_int(1)*signed(z_int(0));
        z_int(0) <= roundn(zrr-zii)+c(0);
        z_int(1) <= roundn(zir)+c(1);
        count <= NOT count;
        IF reset = '1' THEN
            z_int(0) <= (OTHERS=>'0');
            z_int(1) <= (OTHERS=> '0');
            count <= '0';
        END IF;
    END PROCESS P1;

    P2: PROCESS(count,ca,cb)
    BEGIN
        IF count='1' THEN c <= ca; ELSE c <= cb; END IF;
    END PROCESS P2;

    z <= z_int;

END ARCHITECTURE synth;
```

[10D]

VHDL 2007 SOLUTIONS
A=Analysis, D = Design, B = Bookwork

Solution to Question 4

a)

A constant index selects a bit at zero cost. A variable index turns into a multiplexer to select the given bit.

As operand of a logical operator constant values simplify to '0', '1' or straight connection, or (XOR & XNOR only) an inverter. Variable values must invoke the relevant operator.

Constant expressions can be derived from:

CONSTANTS

FOR indexes

GENERICs

[4B]

b)

(i) 2 X 2-input multiplexers

(ii) 4 X 4-input multiplexers

[2B]

c)

ARCHITECTURE synth OF switch IS

 TYPE grid IS ARRAY (0 TO n+1) OF std_logic_vector(n-1 DOWNT0 0);

 SIGNAL x: grid;

BEGIN

 G1: FOR a IN 0 TO n-1 GENERATE

 G2: FOR b IN 0 TO 2**(N-1)-1 GENERATE

 P: ENTITY permute GENERIC MAP(n=>n, m=>1)

 PORT MAP(p=>sel(a DOWNT0 a),

 xin =>(x(a)(x0(a,b)), x(a)(x1(a,b))),

 xout =>(x(a+1)(x0(a,b)),x(a+1)(x1(a,b))));

 END GENERATE G2;

 END GENERATE G1;

END synth;

[14D]