

E1.4 SOLUTIONS

Question 1

a) Since the MOSFET is at pinch-off we know we can use the active mode drain current equation. So, we have $I_D = K(V_{GS} - V_t)^2 = 0.5 \text{ mA}$. With $K = 2 \text{ mA/V}^2$ and $V_t = -1.5 \text{ V}$ this gives $V_{GS} = -1.5 \pm 0.5 \text{ V}$. Taking the positive sign (to ensure n-ch MOSFET above threshold), we find $V_{GS} = -1 \text{ V}$, and since $V_G = 0$ this implies $V_S = 1 \text{ V}$. The source resistance can now be obtained as $R_S = V_S/I_D = 2 \text{ k}\Omega$.

The device is at pinch-off so $V_{DS} = V_{GS} - V_t = 0.5 \text{ V}$. So $V_D = 1.5 \text{ V}$, and $R_D = (V_{CC} - V_D)/I_D$ gives $R_D = 7 \text{ k}\Omega$. [6]

b) According to the resistance reflection rule, the output resistance is given by:



$$R_o = R_S/(1 + \beta) + r_e$$

With $R_S = 10 \text{ k}\Omega$, $r_e = V_T/I_E = 25 \text{ mV}/10 \text{ mA} = 2.5 \Omega$, and $\beta = 100$, this gives $R_o = 101.5 \Omega$.

(NB this is very quick if the student knows reflection rule; otherwise the result will need to be derived by small-signal analysis) [6]

c) Class B push-pull output stage:

Output waveform with 10 Vpp input:

  

[3 + 3]


When V_{IN} is positive, Q1 conducts and acts as an emitter follower, so the output follows the input but dropped down by $V_{BE} \sim 0.7 \text{ V}$. Conversely, when V_{IN} is negative, Q2 acts as the emitter follower and the output is raised above the input by $V_{BE} \sim 0.7 \text{ V}$. However, when the input voltage is near zero, neither transistor conducts and the output goes to zero. This leads to distortion in the output waveform around the zero-crossing points, as shown. [2]

d) Assuming the small-signal approximation is adequate (as suggested by the question), and using the standard result for the small-signal differential gain, we have $V = g_m R_D v_d$, where v_d is the differential input voltage. The quiescent current is 0.5 mA, so $g_m = 2\sqrt{(K I_D)} = 1 \text{ mA/V}$, and with $v_d = 200 \text{ mV}$ and $R_D = 10 \text{ k}\Omega$ we obtain $V = 2 \text{ V}$.

(NB to use the above method students need to see that the gain result they know from BJT differential amplifiers applies equally well to a MOSFET diff pair. If they don't see this they can still obtain an answer by solving large signal equations, but this will take longer.)

[6]

 e) The MOSFET has $V_{GS} = 0$, so the I-V curve (with $I = I_D$ and $V = V_{DS}$) is just the output curve at zero gate-source voltage. An n-channel device will be active if $V \geq -V_t$ and linear when $V < -V_t$ (nb reverse inequalities for p-ch device). Sketch for n-channel device is:



[6]

f) Rise time: assuming transistor has been on for a long time, it will be saturated and the output voltage will be $V_{OUT} \sim 0.2 \text{ V}$. If it switches off at $t = 0$, the new steady state will be $V_{OUT} = +5 \text{ V}$. The trajectory of V_{OUT} will therefore be:

$$V_{OUT} = 5 + (0.2 - 5)\exp(-t/\tau)$$

where $\tau = RC = 1 \mu\text{s}$ is the time constant.

Putting $V_{OUT} = 0.5 \text{ V}$, the time to 10% is $t_{10} = \tau \ln(4.8/4.5)$. Similarly, the time to 90% is $t_{90} = \tau \ln(4.8/0.5)$. The rise time is therefore $t_r = t_{90} - t_{10} = \tau \ln(4.5/0.5) = 2.2 \mu\text{s}$.

Fall time: assuming the transistor has been off for a long time, the output voltage will be $V_{OUT} = +5 \text{ V}$. If it switches on at $t = 0$, it will initially be active with $I_C = 43 \text{ mA}$ assuming $V_{BE} = 0.7 \text{ V}$. The new steady state (that would be reached if transistor remained active) is $V_{OUT} = 5 - 0.043 \times 1\text{k} = -38 \text{ V}$. The initial trajectory of V_{OUT} will therefore be:


$$V_{OUT} = -38 + (5 - -38)\exp(-t/\tau)$$

The time to 90% is $t_{90} = \tau \ln(43/42.5)$, and the time to 10% is $t_{10} = \tau \ln(43/38.5)$, so the fall time is $t_f = t_{10} - t_{90} = \tau \ln(42.5/38.5) = 99 \text{ ns}$, (Linear ramp approximation giving $t_f = 93 \text{ ns}$ also acceptable.)

[8]

Question 2

 a) Replacing input resistor network by Thévenin equivalent, bias circuit reduces to:



$$V_{BIAS} = 10 \times 33 / (33 + 150) = 1.803 \text{ V}$$

$$R_B = 33k // 150k = 27.0k$$

$$\text{KVL then gives: } I_E R_E + V_{BE} + I_B R_B = V_{BIAS}$$

$$\Rightarrow I_E = (V_{BIAS} - V_{BE}) / [R_E + R_B / (1 + \beta)]$$

$$\text{Assuming } V_{BE} = 0.7 \text{ V,}$$


$$I_E = (1.803 - 0.7) / (2.2k + 27k / 201) = 0.473 \text{ mA}$$

$$I_C = \alpha I_E = 200 \times 473 / 201 = \mathbf{0.470 \text{ mA}}$$

$$V_{OUT} = 10 - 0.47 \times 10 = \mathbf{5.30 \text{ V}}$$

[6 + 2]

b) SSEC:

 

KVL on input side:

$$i_b r_{be} + (1 + \beta) i_b Z_E = v_{in}$$

KVL on output side:

$$-\beta i_b R_C = v_{out}$$

$$\Rightarrow A_v = v_{out} / v_{in} = -\beta R_C / [r_{be} + (1 + \beta) Z_E]$$

Using $r_e = r_{be} / (1 + \beta)$ this reduces to

$$A_v = -\alpha R_C / (r_e + Z_E)$$

$$r_e = V_T / I_E = 25m / 0.473m = 52.9 \Omega$$


In mid-band, where $Z_E \rightarrow 0$, $A_v = -\alpha R_C / r_e = \mathbf{-188}$

At low frequency, where $Z_E \rightarrow 2.2 \text{ k}\Omega$, $A_v = -\alpha R_C / (r_e + Z_E) = \mathbf{-4.42}$

[6 (SSEC) + 3 + 3]

 c) At low end of mid-band, $Z_E \approx 1 / j\omega C_E$ and a HP filter is formed with r_e . The cut-off frequency is therefore given by $\omega_c r_e C_E = 1$ or $f_c = 1 / (2\pi r_e C_E)$. With $r_e = 52.9 \Omega$, for a cut-off at 1 kHz we require $C_E = 1 / (2\pi r_e f_c) = 1 / (2\pi \times 52.9 \times 1k) = \mathbf{3.0 \mu F}$

Load capacitor C_L and output resistor R_C form a LP filter with cut-off frequency $f_c = 1 / (2\pi R_C C_L) = 1 / (2\pi \times 10k \times 330p) = \mathbf{48 \text{ kHz}}$



[4 + 2 + 4]

Question 3

a) The role of the $10\text{ M}\Omega$ is to set the operating point by forcing the condition $V_{G1} = V_{OUT}$ at DC. [2]

Both MOSFETs have $V_{GD} \leq 0$ and hence are active if above threshold. The drain current expressions are therefore:

$$I_{D1} = K_1(V_{OUT} - V_{t1})^2 \quad ; \quad I_{D2} = K_2[(V_{DD} - V_{OUT})/2 - V_{t2}]^2$$

No current flows in the $10\text{ M}\Omega$, and if we also neglect the current in the $1\text{ M}\Omega$ resistors the drain currents must be equal:

$$K_1(V_{OUT} - V_{t1})^2 = K_2[(V_{DD} - V_{OUT})/2 - V_{t2}]^2$$

Taking the positive square root (to ensure both devices are above threshold) gives:


$$2\sqrt{(K_1/K_2)}(V_{OUT} - V_{t1}) = V_{DD} - V_{OUT} - 2V_{t2}$$

from which the required result follows. [6]

With $\sqrt{(K_1/K_2)} = 2$, $V_{DD} = 10\text{ V}$ and $V_{t1} = V_{t2} = 1\text{ V}$, we obtain $V_{OUT} = 12/5 = 2.4\text{ V}$.

Substituting for V_{OUT} in either of the drain current equations gives $I_{D1} = I_{D2} = 0.784\text{ mA}$. [4]

 b) SSEC (omitting MOSFET output resistances):



Ignoring the resistors (which are carrying negligible current), KCL at the output gives [6]

$$g_{m1}V_{in} + \frac{1}{2}g_{m2}V_{out} = 0$$

from which it follows that $A_v = -2g_{m1}/g_{m2} = -2\sqrt{(K_1/K_2)} = -4$. [4]

The input current is $i_{in} = (v_{in} - v_{out})/10\text{M} = v_{in}(1 - A_v)/10\text{M} = 5v_{in}/10\text{M}$, so the input resistance is $R_{in} = 2\text{ M}\Omega$. [2]

c) In the presence of a signal v_{in} , we can write the total output voltage as $V_{out} = (2.4 - 4v_{in})$, while the total input voltage is $V_{in} = 2.4 + v_{in}$. The condition for Q1 to remain active is therefore:

$$2.4 - 4v_{in} \geq 2.4 + v_{in} - V_{t1}$$

We therefore require $v_{in} \leq V_{t1}/5 = 0.2\text{ V}$ for Q1 to remain active.

Q2 will remain active provided $(V_{DD} - V_{OUT})/2 > V_{t2}$ or $V_{OUT} < 8\text{ V}$. The limiting case would correspond to $v_{in} = -1.4\text{ V}$.

So, the constraint on Q1 is the limiting factor, and range of input signal amplitudes over which both transistors will remain active is **from 0 to 0.2 V (0.4 V peak-to-peak)**. [6]