

EEE PART II: MEng, BEng and ACGI

Corrected Copy

Time allowed: 2:00 hours

Answer ALL questions.


Basic expressions for voltage gain, input and output resistance for single stage amplifiers are given on the last page.

Examiners responsible First Marker(s) : T. Constandinou
Second Marker(s) : C. Toumazou

1. This question consists of 4 sub-questions. Each item can be answered in a few words or a short paragraph with use of a diagram and/or expression where helpful. Please answer all sub-questions and simplify expressions where possible stating any assumptions made.


a) Derive expressions (by inspection) for the *voltage gain* of the amplifier circuits shown below (including r_o).

[20]

 


(i)

Fig. 1.1(a)

 


(ii)

Fig. 1.1(b)

 

(iii)

Fig. 1.1(c)

 

(iv)

Fig. 1.1(d)

b) Describe the basic principle of operation of a *bandgap voltage reference* circuit. When is such a circuit used?

[5]

c) Explain how the circuit implementation of a differential amplifier can affect the following characteristics: (i) *common mode rejection ratio*; and (ii) *input offset voltage*.

[5]

d) Draw the *bode plot* (magnitude only) for a single stage common-emitter amplifier having a capacitively coupled input and resistive load. Include the parasitic capacitances.

[5]

e) Explain the differences between *direct* and *capacitive coupling* and identify the related constraints when designing analogue integrated circuits.

[5]

2. The circuit shown below in Fig. 2.1 is an interface circuit for a photodiode.

 


Fig. 2.1

- a) State what kind of amplifier this is and what are the ideal input and output impedances. [3]
- b) By breaking the loop, determine expressions for the following (including r_o):
 - i. Open-loop gain [10]
 - ii. Feedback factor [5]
 - iii. (Open loop) input and output impedances [5]
 - iv. (Closed loop) gain, input and output impedances [7]

3. The circuit shown below in Fig. 3.1 is a 3-stage operational amplifier.

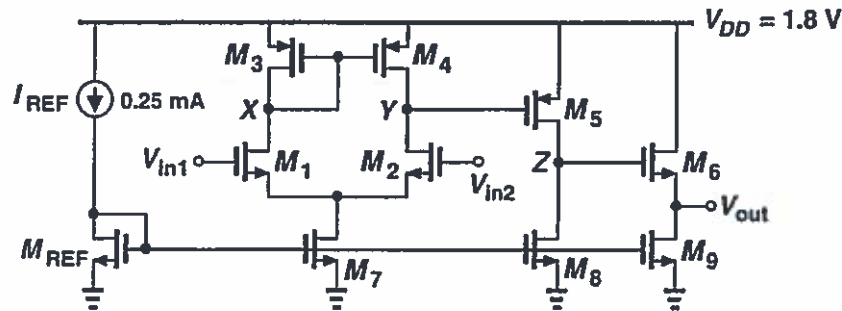


Fig. 3.1

Transistor sizing as follows:

Table 3.1


	M_{REF}	M_1	M_2	M_3	M_4	M_5	M_6	M_7	M_8	M_9
W/L	2/4	250/1	250/1	5/2	5/2	50/1	50/1	8/4	16/4	80/4

Assume all devices are in saturation and $\lambda > 0$ (i.e. $R_{out} < \infty$).

Use the following transistor parameters where needed: $\mu_n C_{ox} = 200 \mu A/V^2$, $V_{THN} = 0.4V$, $\lambda_n = 0.1V^{-1}$, $\mu_p C_{ox} = 100 \mu A/V^2$, $V_{THP} = -0.5V$, $\lambda_p = 0.2V^{-1}$

- What is the total power consumption? [4]
- Determine an expression for the voltage gain of the amplifier, $A_v = V_{out}/(V_{in2} - V_{in1})$ and evaluate. [10]
- Determine an expression for the output impedance (R_{out}) of the amplifier and evaluate. [4]
- Identify the nodes associated with poles and discuss which 2 will dominate the frequency response (excluding nodes V_{in1} and V_{in2}). [2]
- Determine expressions for these 2 pole frequencies stating any assumptions made and evaluate. Where required, use the following parasitic capacitance values: $C_{GS} = (2/3)WLC_{ox}$, $C_{ox} = 20fF/\mu m^2$, $C_{GD} = C_0W$, $C_0 = 0.5fF/\mu m$, $C_{DB} = C_{SB} = 0$. [10]

Input and Output Impedances

 

Voltage Gain Equations

