

UNIVERSITY OF LONDON
IMPERIAL COLLEGE OF SCIENCE, TECHNOLOGY AND MEDICINE

EXAMINATIONS 2000

BEng Honours Degree in Computing Part I
MEng Honours Degrees in Computing Part I
for Internal Students of the Imperial College of Science, Technology and Medicine

*This paper is also taken for the relevant examinations for the
Associateship of the City and Guilds of London Institute*

PAPER C112

HARDWARE

Wednesday 17 May 2000, 16:00
Duration: 90 minutes
(Reading time 5 minutes)

Answer THREE questions

Paper contains 4 questions

1. Sequential Circuit Design

A counter is to work in four modes determined by two input bits as follows.
When the input is 0 (0,0) the output remains at 0
When the input is 1 (0,1) the counter goes through the sequence 0,3,2,1,0,3,2,1 .
When the input is 2 (1,0) the counter goes through the sequence 0,1,2,0,1,2 . .
When the input is 3 (1,1) the counter goes through the sequence 1,2,3,1,2,3 . .

- a. Draw the state transition diagram (using the Moore finite machine model) that corresponds to the above specification
- b. Compile a state transition table in the following format:

Input		Current State		Next State	
I1	I0	Q1	Q0	D1	D0
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1				
0	1				
0	1				
0	1				
1	0				
1	0				
1	0				
1	0				
1	1				
1	1				
1	1				
1	1				

- c. Draw Karnaugh maps for D0 and D1 and determine the minimum form of the Boolean equations for D0 and D1 to implement the counter.
- d. Explain what the difference is between the Moore finite state machine and the Mealy finite state machine. For each, give one reason why a designer should choose to use it.

The four parts carry, respectively, 25%,20%,30%,25% of the marks.

2. Combinational Circuit Design

- a. Using Boolean algebra, simplify the following Boolean expression, and draw a circuit that will implement it.

$$R = ((A.B)' + B).C'$$

- b. The exclusive NOR gate (XNOR) is defined by the following truth table

		B	
		XNOR	
A	0	0	1
	1	1	0
	1	0	1

Design a circuit to implement it, and write down its Boolean equation.

- c. The full adder is defined in terms of its inputs A, B and C_{in} as

$$C_{out} = A . B$$
$$S = A \oplus B \oplus C_{in}$$


Express both boolean equations in the canonical minterm form.

- d. Find the equivalent canonical forms for the full adder using maxterms (hint: you may find it helpful to look at the truth table or Karnaugh map to do this).
- e. Explain briefly why pure Boolean algebra is inadequate as a model for describing the behaviour of a flip flop.

The five parts carry equal marks.

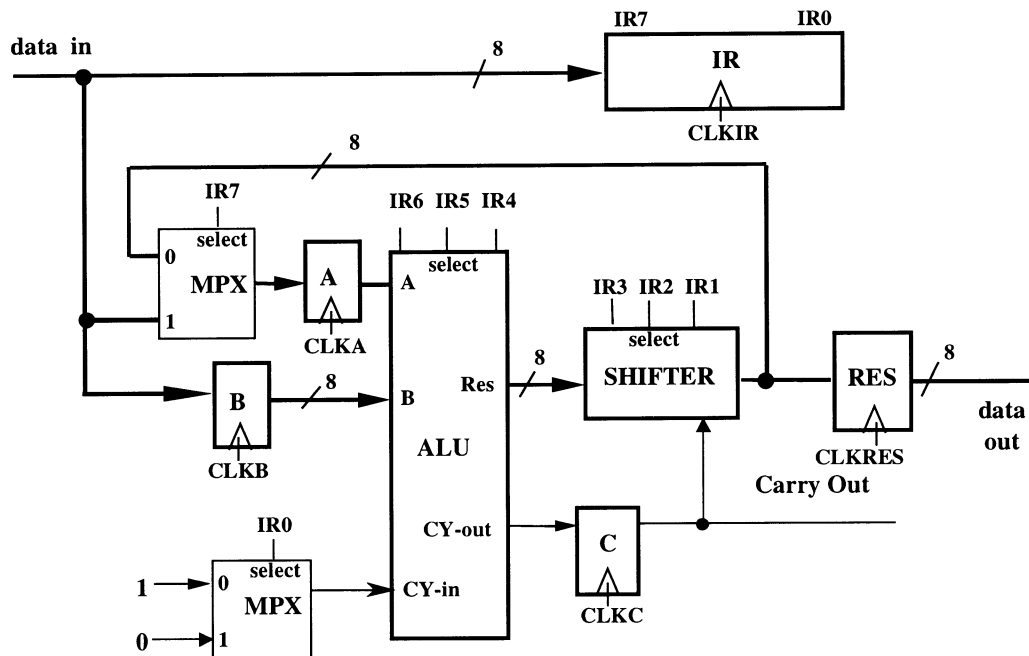3. The Manual Processor

An 8-bit manual processor has the following block diagram.



The functions of the various components are defined by the following tables:

Shifter:

Function Select	Shift	Carry in	Function
000	unchanged	1	unchanged
001	left	0	arithmetic/logical shift left
010	right	1	?
011	right	0	logical shift right
100	unchanged	data bit 7	unchanged
101	left	CY in	left shift with carry
110	right	data bit 7	arithmetic right shift
111	right	CY in	right shift with carry

ALU:

Selection Bits	000	001	010	011	100	101	110	111
Result	0	B mi A	A mi B	A pl B	A xor B	A+B	A.B	-1

The processor goes through a fixed cycle of five states in which the following clock gates are applied:

State	Clock
1	CLKIR
2	CLKA
3	CLKB and CLKC
4	CLKIR
5	CLKRES and CLKC

The following two instructions are to be designed for use with the processor:

ADD: which will add together two numbers on the *data in* lines, and place the result on the *data out* lines during state 5.

DEC: which will take a number from the *data in* lines, decrement it and place the result on the *data out* lines during state 5.


- a. Determine the register transfers that will be carried out during each state of the processor cycle, by constructing a table in the following form.

	ADD		DEC	
State	Source	Destination	Source	Destination
1	DataIn	IR		
2				
etc.				

- b. Find the contents of the instruction register in states 2 to 5 of the processor cycle for both the ADD and DEC instructions. This will be determined by the *data in* lines in states 1 and 4 and will contain don't care values.

The two parts carry equal marks.

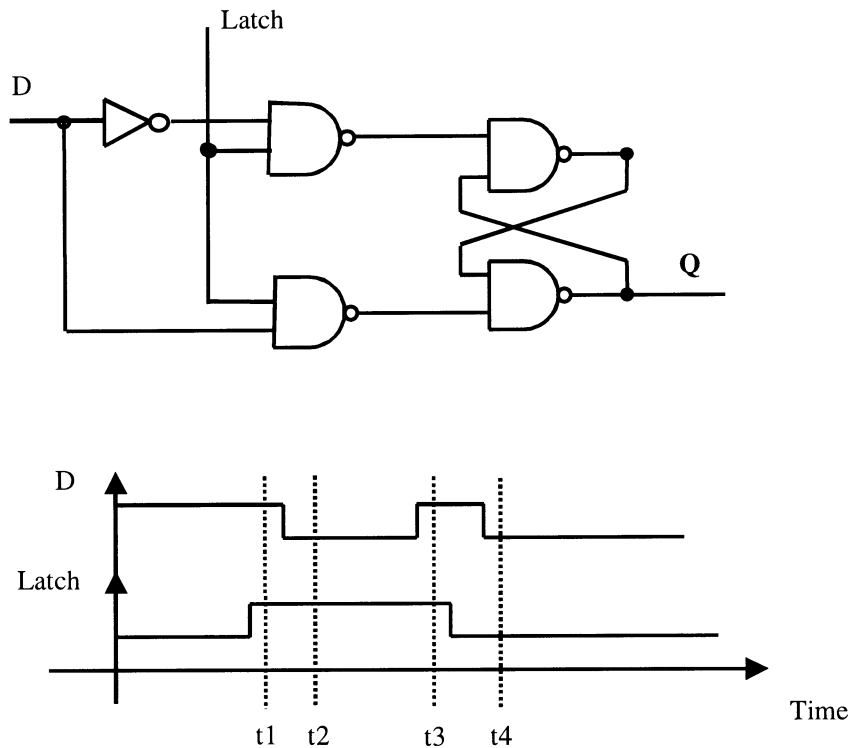a. The D-type latch has the following circuit. The inputs to the circuit, as a function of time are shown below can be treated as changing between 0 and 1.



Calculate the value of Q at the times t_1, t_2, t_3 and t_4 shown in the diagram.

- b. Show how two D-type latches of the type shown in part a may be connected together, with other gates if required, to form a D-Q flip flop.
- c. Show, with a suitable diagram, how D-Q flip flops may be connected to form a serial to parallel converter.
- d. Give an example where serial to parallel conversion is used in digital computer systems. Explain briefly why it is necessary.
- e. As part of a hardware design it is necessary to have a four bit register which will carry out two different functions. These are parallel load and rotate left. Draw a diagram showing the complete circuit of this register. You may use the following components in your design:
 - D-Q flip flops
 - AND gates
 - OR gates
 - INVERTER gates

The five parts carry, respectively, 20%, 20%, 15%, 15%, 30% of the marks.