

UNIVERSITY OF LONDON
IMPERIAL COLLEGE OF SCIENCE, TECHNOLOGY AND MEDICINE

EXAMINATIONS 2004

BEng Honours Degree in Computing Part I
MEng Honours Degrees in Computing Part I
for Internal Students of the Imperial College of Science, Technology and Medicine

*This paper is also taken for the relevant examinations for the
Associateship of the City and Guilds of London Institute*

PAPER C112

HARDWARE

Tuesday 11 May 2004, 10:00
Duration: 90 minutes
(Reading time 5 minutes)

Answer THREE questions

Paper contains 4 questions
Calculators required

1. Computer Arithmetic

- a A half adder is defined by the following truth table

A	B	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

Design a combinatorial logic circuit with inputs A and B and outputs S and C.

- b A full adder has additionally a carry in. Show how two half adders and one *OR* gate can be connected to make a full adder.
- c Negative numbers are often represented by their two's complement. This is found by flipping each bit of an n bit number and incrementing the result. Design an n-bit two's complement circuit using n half adders and any other gates you require.
- d Using four AND gates and two half adders design a two bit multiplier with inputs A1 A0 and B1 B0 and outputs O3 O2 O1 and O0.
- e Show how to connect up four of your two bit multipliers designed in part c to make a four bit multiplier.

The five parts carry equal marks

2. Sequential Circuit Design

A counter is to work in four modes determined by two input bits as follows.

When the input is (0,0) the counter goes through the sequence 0,1,2,3,0,1,2,3 .

When the input is (0,1) the counter goes through the sequence 0,2,3,0,2,3, .

When the input is (1,0) the counter goes through the sequence 0,2,1,0,2,1 . .

When the input is (1,1) the counter goes through the sequence 1,2,1,2,1,2 . .

- Draw the state transition diagram (using the Moore finite machine model) that corresponds to the above specification
- Compile a state transition table in the following format using dont-cares wherever possible:


Input		Current State		Next State	
I1	I0	Q1	Q0	D1	D0
0	0	0	0		
0	0	0	1		
0	0	1	0		
0	0	1	1		
0	1				
0	1				
0	1				
0	1				
1	0				
1	0				
1	0				
1	0				
1	1				
1	1				
1	1				
1	1				

- Draw Karnaugh maps for D0 and D1 and determine the minimum form of the Boolean equations for D0 and D1 to implement the counter.
- Explain what will happen to you circuit in the following circumstances:
 - The circuit is in state 3 and the input changes to (1,0)
 - The circuit is in stat 3 and the input changes to (1,1)
 - The circuit is in state 0 and the input changes to (1,1)

The four parts carry equal marks.

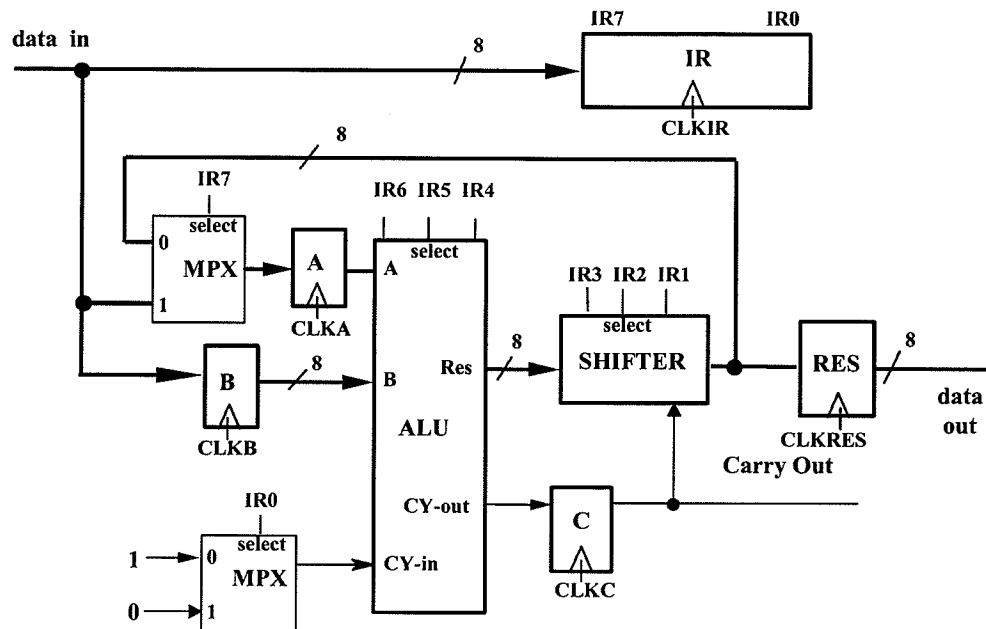3. The Manual Processor

An 8-bit manual processor has the following block diagram.



The functions of the various components are defined by the following tables:

Shifter:

Function Select	Shift	Carry in	Function
000	unchanged	1	unchanged
001	left	0	arithmetic/logical shift left
010	right	1	?
011	right	0	logical shift right
100	unchanged	data bit 7	unchanged
101	left	CY in	left shift with carry
110	right	data bit 7	arithmetic right shift
111	right	CY in	right shift with carry

ALU:

Selection Bits	000	001	010	011	100	101	110	111
Result	0	B mi A	A mi B	A pl B	A xor B	A+B	A.B	-1

The processor goes through a fixed cycle of five states in which the following clock gates are applied:

State	Clock
1	CLKIR
2	CLKA
3	CLKB and CLKC
4	CLKIR
5	CLKRES and CLKC

The following two instructions are to be designed for use with the processor:

SUB: which will subtract the first number on the *data in* lines from the second, and place the result on the *data out* lines during state 5.

INC: which will take a number from the *data in* lines, increment it and place the result on the *data out* lines during state 5.

- a. Determine the register transfers that will be carried out during each state of the processor cycle, by constructing a table in the following form.


	SUB		INC	
State	Source	Destination	Source	Destination
1	DataIn	IR		
2				
etc.				

- b. Find the contents of the instruction register in states 2 to 5 of the processor cycle for both the SUB and INC instructions. This will be determined by the *data in* lines in states 1 and 4 and will contain don't care values.

The two parts carry equal marks.

4. Registers

 - a. The D-type latch has the following circuit. The inputs to the circuit, as a function of time are shown below can be treated as changing between 0 and 1.



Calculate the value of Q at the times t1, t2, t3 and t4 shown in the diagram.

- Show how two D-type latches of the type shown in part a may be connected together, with other gates if required, to form an edge triggered D-Q flip flop.
- Show, with a suitable diagram, how D-Q flip flops may be connected to form a serial to parallel converter.
- Give an example where serial to parallel conversion is used in digital computer systems. Explain briefly why it is necessary.
- As part of a hardware design it is necessary to have a four bit register which will carry out two different functions. These are serial load (with most significant bit arriving last) and rotate left. Draw a diagram showing the complete circuit of this register. You may use the following components in your design:
 - D-Q flip flops
 - AND gates
 - OR gates
 - INVERTER gates

The five parts carry, respectively, 20%,20%,15%,15%,30% of the marks.