


# SOLUTIONS

①  
Circuit Analysis  
EE 1.1  
2008

Q1  
(a)



(b)

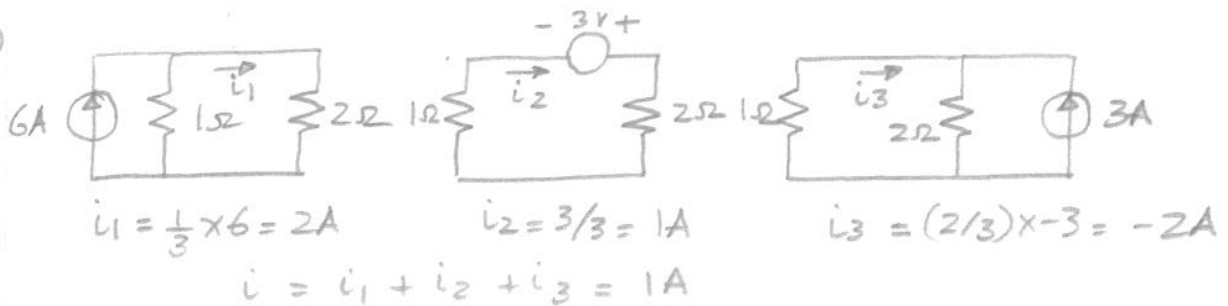


(c)

$$I_{SC} = 1 + 12/12 + 24/12 = 1 + 1 + 2 = 4 \text{ A}$$

$$R_{Th} = 3\Omega // 12\Omega // 12\Omega = 3\Omega // 6\Omega = 2\Omega$$
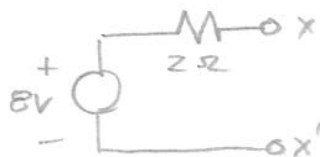
$$V_{OC} = I_{SC} \times R_{Th} = 4 \times 2 = 8 \text{ V}$$



(d)

$$\begin{aligned} 2V_1 - V_2 &= 2 - 1 = 1 & 2V_1 - V_2 &= 1 & \text{①} \\ (1 + 1/3)V_2 - V_1 &= 1 + 1 = 2 & 4V_1 + \frac{4}{3}V_2 &= 2 & \text{②} \\ \text{①} + 2 \times \text{②} &\rightarrow (8/3 - 1)V_2 = 2 \times 2 + 1 \rightarrow V_2 = 3 \text{ V} & V_1 &= 2 \text{ V} \end{aligned}$$

(e)

(i) 0V    (ii) 5V    (iii)  $\tau = C \times R_2 = 10^{-6} \times 10^6 = 1 \text{ s}$

(iv)  $V_C(t) = V_{CO} + (V_{CO} - V_{CO})(1 - e^{-t/\tau})$

$= 0 + 5(1 - e^{-t/\tau})$

$= 5 - 5e^{-t/\tau}$

(f)  $\bar{V}_s = 4 \angle 0^\circ$   $z_L = j^{2/3}$   $z_C = -j$

$$\bar{V} = \frac{z_2}{z_1 + z_2} \bar{V}_s = \frac{1}{1 + z_1 Y_2} \bar{V}_s = \frac{4}{1 + 2(-j^{2/3} + j)} = \frac{4}{1-j}$$

$$= \frac{4}{\sqrt{2} \angle -45^\circ} = 2\sqrt{2} \angle 45^\circ$$

$$v(t) = 2\sqrt{2} \cos(2t + \pi/4)$$

(g)  $\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(10^{-3})(10^{-11})}} = 10^7 \text{ rad/sec}$

$$Q = \frac{\omega_0 L}{r_s}; r_s = \frac{\omega_0 L}{Q} = \frac{10^7 \cdot 10^{-3}}{100} = 100 \Omega$$

$$z_L = -z_C, \text{ so Gain} = 1/2$$

(h)  $i_x = \frac{V_i}{R_i} - \frac{V_s}{R_f}$

$$V_s = r_m i_x = r_m \left( \frac{V_i}{R_i} - \frac{V_s}{R_f} \right)$$

$$V_s \left( 1 + \frac{r_m}{R_f} \right) = \frac{r_m}{R_i} V_i \quad \frac{V_s}{V_i} = \frac{1}{R_i \left( \frac{1}{r_m} + \frac{1}{R_f} \right)}$$

(i)  $V_1 = (-1) \times 2 = -2V$

$$V_2 = V_1 = -2V$$

$$V_{out} = V_2 + (V_{out} - V_2)$$

$$= V_2 + (V_2 - 2) = 2V_2 - 2 = -6V$$

(j)  $I_2 = y_{21} V_1 + y_{22} V_2$

$$I_2 = -V_2 / R_L$$

$$-\frac{V_2}{R_L} = y_{21} V_1 + y_{22} V_2$$

$$-V_2 \left( \frac{1}{R_L} + y_{22} \right) = y_{21} V_1$$

$$\frac{V_2}{V_1} = - \frac{y_{21}}{\frac{1}{R_L} + y_{22}}$$

2

$$(a) \quad V_L = L \frac{di_L}{dt}$$

$$i_C = C \frac{dV_C}{dt}$$

Inductor is a short circuit  $\rightarrow \text{---} \text{---} \text{---}$

Capacitor is an open circuit  $\rightarrow \text{---} \text{---} \text{---}$



6A current divides equally in resistors. So  $i = 3A$ ,  $V = 15V$

$$(b) \quad (i) \quad \tau = 10^3 \times 10^{-6} = 1 \text{ ms}$$

$$(ii) \quad V_0 = \frac{1}{2} 10V = 5V$$

$$(iii) \quad V_{\infty} = -5V$$

$$(iv) \quad V(t) = V_0 + (V_{\infty} - V_0)(1 - e^{-t/\tau})$$

$$= 5 + (-10)(1 - e^{-t/\tau})$$

$$= -5 + 10e^{-t/\tau}$$

$$(v) \quad V(2) = -5 + 10e^{-2}$$

$$=$$

$$(vi) \quad \tau_2 = 10^{-6} \times (10^3 + 2000 // 2000)$$

$$= 10^{-6} \times 2000$$

$$= 2 \text{ ms}$$

$$(c) \quad \text{Pull-up: } \tau_u = 2500 \times 0.1 \times 10^{-12}$$

$$= 250 \text{ ps}$$

$$\text{Minimum charging time} = 1.75 \times 250$$

$$= 437.5 \text{ ps}$$

$$\text{Pull-down } \tau_D = 1000 \times 0.1 \times 10^{-12}$$

$$= 100 \text{ ps}$$

$$\text{Minimum charging time} = 1.75 \times 100$$

$$= 175 \text{ ps}$$

Minimum clock period governed by pull-up

$$\tau_{\min} = 2 \tau_u = 875 \text{ ps}$$


$$\text{Maximum clock rate} = \frac{1}{\tau_{\min}} = 1.14 \text{ GHz}$$

3(a) Impedance,  $Z = \bar{V}/\bar{I}$  where  $\bar{V}$  and  $\bar{I}$  are phasor forms of element voltage  $v$  and current  $i$ .


$$Z_L = j\omega L \quad Z_C = 1/(j\omega C)$$

Reactance  $X$  is imaginary part of impedance  $Z = R + jX$
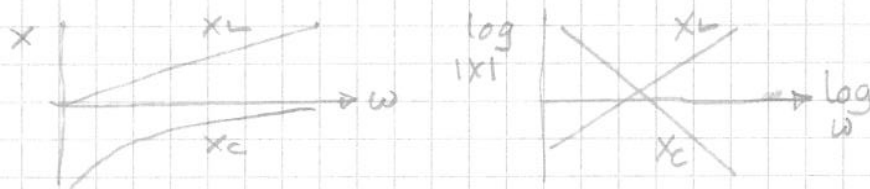
$$X_L = \omega L \quad X_C = -1/(\omega C)$$



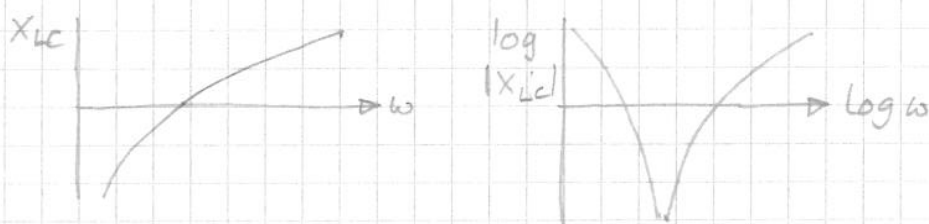
$$Z_{LC} = j\omega L + \frac{1}{j\omega C} = j\left(\omega L - \frac{1}{\omega C}\right) \quad X_{LC} = \omega L - \frac{1}{\omega C}$$



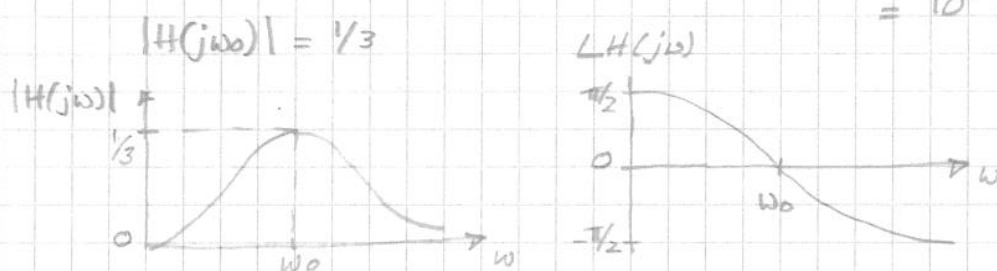(b) 
$$H(j\omega) = \frac{Z_2}{Z_1 + Z_2} = \frac{1}{1 + Z_1 Y_2} = \frac{1}{1 + (R + \frac{1}{j\omega C})(j\omega C + \frac{1}{R})}$$
  

$$= \frac{j\omega CR}{1 + j3\omega CR - (\omega CR)^2}$$

$LH(j\omega) = 0$  for  $\omega_0 CR = 1$ , i.e.  $\omega_0 = \frac{1}{CR}$   
 $= \frac{1}{10^{-9} 10^3}$   
 $= 10^6 \text{ Mrad/sec}$



(c)

	$Z_1$	$Z_2$	$Z_3$
LP	R	L	C
BP	C	L	R
HP	R	C	L


- (d)
- BPF - Channel-select filter in communication system
  - LPF - Anti-alias filter prior to sampling
    - Reconstruction filter
    - Removing out-of-band noise

4(a)


Low cost  
Short design time

⑤


(b)

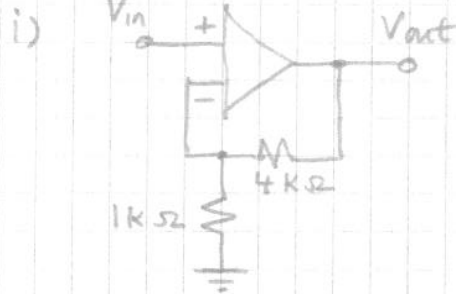


ii)

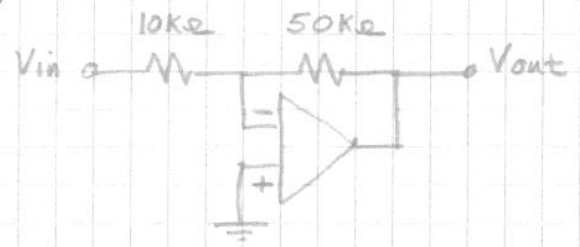


iii)

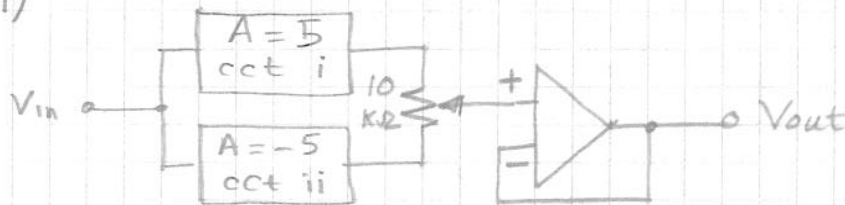

(c)

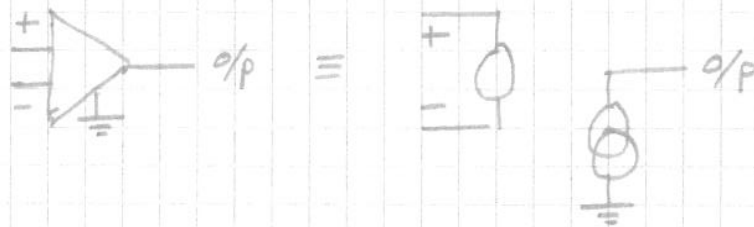

Nullator:

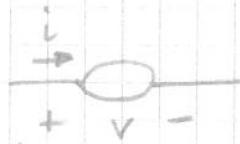

$$V = 0$$

$$i = 0$$

Norator:



$$V = \text{arbitrary}$$

$$i = \text{arbitrary}$$

Non-ideal aspects:

Stability

Finite gain-bandwidth product

(d)



(i) For high frequency design

(ii) Designs requiring very low power consumption

(e)

BJT (common emitter model)

FET

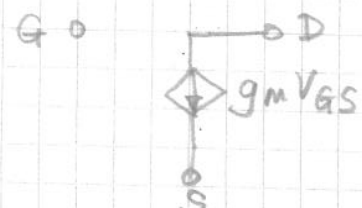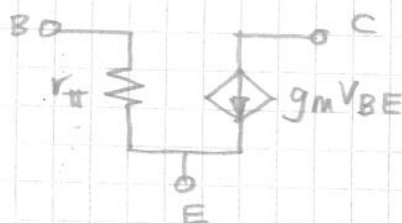

$$r_{\pi} = (1 + \beta) V_T / I_{CQ} \quad g_m = I_{CQ} / V_T$$

$$g_m = 2K(V_{GSQ} - V_{TH})$$

Nodal analysis