

# EE2-02 SOLUTIONS (ANALOGUE ELECTRONICS)

1. This question consists of 5 sub-questions. Each item can be answered in a few words or a short paragraph with use of a diagram and/or expression where helpful. Please answer all sub-questions and simplify expressions where possible stating any assumptions made.

- a) Which of the topologies shown below in Fig. 1.1 would have better performance? Explain why. [5]

 


Fig. 1.1(a)

 


Fig. 1.1(b)


Although both the circuits have the same function [1]  
— common source amplifier with active load

( $A_v = -g_{m_x}(r_{o1} || r_{o2})$  with  $x =$  CS amplifier transistor), [1]  
in ckt. (a) amplifier is NMOS whereas in (b) is PMOS. Assuming device sizes are identical design (a) would be preferable. This is because  $\mu_n > \mu_p$  (approx.  $\times 3$ ) [1] and therefore  $g_m(\text{NMOS amp}) > g_m(\text{PMOS amp})$  [1]  $\therefore A_v$  also higher. [1]

- b) Propose a *circuit topology* (e.g. common source amplifier with resistive load), for each of the following applications, in each case justifying your selection, and sketching the circuit schematic.

(i) A pre-amplifier to interface to a capacitive microphone.


[5]

 

A capacitive microphone would have a very high impedance  $\therefore$  [1]  
can provide no output current  
So amp with very high  $Z_{in}$  [1]  
needed not to load. Such an  
amp. is CS amplifier (MOSFET) [1]  
also to provide moderate  
voltage gain.

(ii) A circuit to increase the DC level of a signal by 1V.


[5]

 

CS (or source follower) stage(s)  
biased with constant current -  
appropriate for level shift [1]  
Each stage can achieve  $+V_{GS}$   
DC level shift. Suggest 2  
stages identical  $\rightarrow$  each  $+0.5V$   
(CMOS) [1]

(iii) A high frequency amplifier providing relatively high isolation between the input and output.

[5]

 

CG (or CB) amplifier exhibit very  
good high frequency response  
as there is no parasitic capacitance  
between i/p and o/p. [1]  
As a result does not suffer from the  
Miller effect. [1] Furthermore CG  
amp can be designed to match  
a 50 $\Omega$  load (since  $Z_{in} \approx 1/g_m$ ). [1]

- c) An inverting amplifier must provide a nominal gain of 20 with a gain error of 0.5%. Determine the minimum required op-amp gain.

[5]

$$\text{Gain error} = \frac{1}{A_o} \left(1 + \frac{R_1}{R_2}\right) \quad [3] - 2 \text{ for deriving} \\ 1 \text{ for expression}$$

$$\frac{1}{A_o} (1+20) = 0.5\% \rightarrow A_o = 4200 \quad [1] \quad [1]$$

- d) Determine the closed loop gain of the circuit shown below in Fig. 1.2. Assume  $\lambda = 0$ .

[5]


 


Fig. 1.2

Break the loop:

 

$$\left. \frac{V_{out}}{V_{in}} \right|_{\text{open-loop}} = \frac{V_{out}}{V_x} \cdot \frac{V_x}{V_{in}} = \frac{-R_{D1}}{\frac{1}{g_{m1}} + R_1 \parallel R_2} \times -g_{m2} (R_1 + R_2) \\ = \frac{g_{m1} g_{m2} R_{D1} (R_1 + R_2)}{1 + g_{m1} (R_1 \parallel R_2)} \quad [2]$$

$$K = \frac{R_2}{R_1 + R_2}$$

$$\therefore A_v \bigg|_{\text{closed loop}} = \frac{A_v(\text{OL})}{1 + K A_v(\text{OL})} = \frac{\frac{g_{m1} g_{m2} R_{D1} (R_1 + R_2)}{1 + g_{m1} (R_1 \parallel R_2)}}{1 + \frac{g_{m1} g_{m2} R_{D1} R_2}{1 + g_{m1} (R_1 \parallel R_2)}} \quad [1]$$

- e) Derive expressions (by inspection) for the *output resistance* of the amplifier circuits shown below in Fig. 1.3 (including  $r_o$ ).

[10]

 


Fig. 1.3(a)


 


Fig. 1.3(b)

 
(i)  $R_G$  effectively makes  $M_2$  diode connected [1]



$$\therefore R_{out} = g_{m1} r_{o1} \left( \frac{1}{g_{m2}} \parallel r_{o2} \right) + r_{o1} + \frac{1}{g_{m2}} \parallel r_{o2} [1]$$

$$\approx g_{m1} r_{o1} \left( \frac{1}{g_{m2}} \parallel r_{o2} \right) [1]$$

 (assuming 1st term greater than others) [1]



$$R_{out} = r_{o1} + g_{m1} (R_1 \parallel r_{\pi 2} \parallel r_{\pi 1}) r_{o1} + R_1 \parallel r_{\pi 1} \parallel r_{\pi 2} [1]$$

$$= r_{o1} + (1 + g_{m1} r_{o1}) (r_{\pi 1} \parallel R_1 \parallel r_{\pi 2}) [1]$$

1 mark for not simplifying/approximating [2]

- 


### Table 2.1. Transistor sizes

p5

 b) Determine an expression for the differential voltage gain of the amplifier.

[5]

Assuming perfect symmetry  $\rightarrow$  equivalent  $1/2$  ckt approx. [1]



$\therefore$  CS amplifier

$$A_v = -g_m (R_o \parallel r_o) \quad [1]$$

$$= -g_{m1} (r_{o1} \parallel (g_{m3} r_{o3} r_{o5} + r_{o3} + r_{o5}))$$



$$\approx -g_{m1} r_{o1} \quad [1]$$

$$(\text{since } r_{o1} \ll g_{m3} r_{o3} r_{o5}) \quad [1]$$

  c) Determine an expression for the common-mode voltage gain of the amplifier.

[5]

Short  $v_{in1} = v_{in2}$  and draw eqv. ckt. for CM gain



$A_v =$  CS with degen.

$$= \frac{-R_o}{1/g_m + R_s} \quad [1]$$

$$= \frac{-g_{m3} r_{o3} r_{o5}}{\frac{1}{2g_{m1}} + r_{o7}}$$

$$= \frac{-2g_{m1} g_{m3} r_{o3} r_{o5}}{2(1 + 2g_{m1} r_{o7})} \quad [1]$$

$\downarrow$   
Since  $g_{m1} r_{o7} \gg 1$

$$\approx \frac{-g_{m3} r_{o3} r_{o5}}{2 r_{o7}} \quad [1]$$

d) Use your answers to parts (b) and (c) to evaluate the common-mode rejection ratio.

[10]

$$CMRR = \frac{A_v(OM)}{A_v(CM)} \quad [1]$$

$$A_v(OM) = -g_{m1} r_{o1}$$

$$g_{m1} = \sqrt{2 I_D \mu_n C_{ox} \frac{W}{L}} = \sqrt{2 (1mA) 200\mu (400)} = 12.6mS$$

$$r_{o1} = 1/\lambda_n I_D = 1/(0.01(1mA)) = 10k\Omega$$

$$\therefore A_v = -126.49 \quad [1]$$

[2]

$$A_v(CM) = \frac{-g_{m3} r_{o3} r_{o5}}{2 r_{o7}}$$

$$g_{m3} = \sqrt{2 (1mA) (100\mu) (50)} = 3.16mS$$

$$r_{o3} = 1/\lambda_p I_{D3} = 1/(0.02(1mA)) = 5k\Omega$$

$$r_{o5} = 1/\lambda_p I_{D5} = 1/(0.02(1mA)) = 5k\Omega$$

$$r_{o7} = 1/\lambda_n I_{D7} = 1/(0.01(2mA)) = 5k\Omega$$

$$A_v(CM) = \frac{-3.16mS (5k\Omega) (5k\Omega)}{2 (5k\Omega)} = -7.9 \quad [1]$$

$$CMRR = \frac{126.49}{7.9} = 16.01 \quad [1]$$

$$= 20 \log(16.01) = 24.12dB \quad [1]$$

e) State the function of transistors  $M_1 - M_2$ ,  $M_3 - M_4$ ,  $M_5 - M_6$ , and  $M_7$  and comment on the specified device sizes.

[5]

$M_1/M_2$  - differential pair. Large  $\frac{W}{L} \rightarrow$  large  $g_m \rightarrow$  large  $A_v(OM)$  [1]

$M_3/M_4$  - cascode  $\rightarrow$  minimize W.L  $\rightarrow$  minimize capacitance [1]

$M_5/M_6$  } current sources/sinks. Large  $\frac{W}{L}$  to generate relatively large  $I_D$  for acceptable  $V_{GS}$  [1]



3. The circuit below in Fig. 3.1 illustrates a cascade of two identical common source stages.

 


Fig. 3.1

- a) Neglecting channel-length modulation and other capacitances, construct the Bode plot of  $V_{out}/V_{in}$  including both the magnitude and phase responses.

[8]

Assuming  $\lambda = 0$  and neglecting other capacitances.


DC gain:  $\frac{v_x}{v_{in}} = -g_{m1} R_D$

$\frac{v_{out}}{v_x} = -g_{m2} R_D$

$A_v = \frac{v_{out}}{v_{in}} = (g_m R_D)^2$  [1]

with 2 poles

@  $\frac{1}{R_D C_L}$  [1]

 

- b) Annotate your plot with the following: (i) Bandwidth; (ii) Phase margin; (iii) Gain Margin.

[5]



- c) Derive the transfer function of the circuit, substitute  $s = j\omega$ , and obtain an expression for  $|V_{out}/V_{in}|$ . Determine the -3dB bandwidth of the circuit.

[10]

$$\frac{V_x}{V_{in}}(s) = -g_m(R_D \parallel \frac{1}{C_L s}) = -g_m \left( \frac{R_D}{R_D C_L s + 1} \right) \quad [1]$$

$$\frac{V_{out}}{V_x}(s) = -g_m \left( \frac{R_D}{R_D C_L s + 1} \right) \quad [1]$$

$$H(s) = \frac{V_x}{V_{in}}(s) \cdot \frac{V_{out}}{V_x}(s) = \left( \frac{g_m R_D}{R_D C_L s + 1} \right)^2 \quad [1]$$

$$s \rightarrow j\omega \quad H(j\omega) = \left( \frac{g_m R_D}{1 + R_D C_L j\omega} \right)^2$$

$$|H(j\omega)| = \frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2} \quad [1]$$

-3dB bandwidth:

$$\frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2} = \frac{(g_m R_D)^2}{\sqrt{2}} \quad [2]$$

$$\Rightarrow (R_D C_L \omega)^2 + 1 = \sqrt{2}$$

$$\Rightarrow \omega = \frac{\sqrt{\sqrt{2}-1}}{R_D C_L} = \frac{0.6436}{R_D C_L} \quad [1] \quad (\text{rad/s})$$

$$2\pi f = \frac{0.6436}{R_D C_L} \Rightarrow f = \frac{0.1024}{R_D C_L} \quad (\text{Hz}) \quad [2]$$

- d) Using your answers to parts (b) and (c), design the two-stage amplifier for a total voltage gain of 15 and  $-3\text{dB}$  bandwidth of  $1.8\text{GHz}$ . Assume each stage carries a bias current of  $1\text{mA}$ ,  $C_L = 40\text{fF}$ , and  $\mu_n C_{ox} = 200\mu\text{A}/\text{V}^2$ .

[7]

Bias current =  $1\text{mA}$  (each stage)

$$C_L = 40\text{fF}$$

$$\mu_n C_{ox} = 200\mu\text{A}/\text{V}^2, A_v = 15, -3\text{dB}: 1.8\text{GHz}$$

$$\text{DC gain: } (g_m R_D)^2 = 15 \quad [1]$$

$$-3\text{dB BW: } \frac{0.10243}{R_D C_L} = 1.8\text{GHz} \quad [1]$$

$$\text{Since } C_L = 40\text{fF} \rightarrow R_D = 1422.6\Omega \quad [1]$$

$$(g_m R_D)^2 = 15 \Rightarrow g_m = 0.00275 = \frac{2I_D}{V_{GS} - V_{TH}} \quad [1]$$

$$\Rightarrow V_{GS} - V_{TH} = 0.741\text{V} \quad [1]$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \Rightarrow \frac{W}{L} = \frac{g_m}{\mu_n C_{ox} (V_{GS} - V_{TH})} = 18.2 \quad [1]$$

$$\therefore R_D = 1.42\text{k}\Omega$$

$$C_L = 40\text{fF}$$

$$V_{GS} - V_{TH} = 0.741\text{V}$$

$$\frac{W}{L} = 18.2$$