

Question 1

1. a) (i)

$$\begin{aligned} & \overline{A + (\overline{AB})C} \\ &= \overline{A((\overline{AB})C)} \\ &= A(\overline{AB} + C) \\ &= A\overline{B} + AC \end{aligned}$$

ii)

$$\begin{aligned} & ABC + B(A \oplus B) \\ &= ABC + B(\overline{A}B + A\overline{B}) \\ &= ABC + \overline{A}B \\ &= B(AC + \overline{A}) \\ &= B(C + \overline{A}) \\ &= BC + \overline{A}B \end{aligned}$$

[4]

b)

$$\begin{aligned} f &= \overline{A}\overline{B}(C \oplus D) + \overline{A}\overline{B}\overline{C}\overline{D} + ACD + ABD \\ &= \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}\overline{B}\overline{C}\overline{D} + ACD + ABD \end{aligned}$$

f

<i>CD</i>	00	01	11	10
<i>AB</i>				
00	1	0	1	0
01	0	0	0	0
11	0	1	1	0
10	1	0	1	0

$$f = \overline{B}\overline{C}\overline{D} + ABD + \overline{B}CD$$

[4]

Here, 1 mark for drawing the Karnaugh map, 1 for filling it out correctly, 1 for the correct grouping, and 1 for the final expression.

[4]

c)

f

		CD			
		00	01	11	10
AB	00	0	0	0	1
	01	1	0	0	1
	11	0	1	0	1
	10	1	0	0	1

$$f = (A + \bar{D})(B + \bar{D})(A + B + C)(\bar{A} + \bar{B} + C + D)(B + \bar{C} + \bar{D})$$

Here, 1 mark for drawing the Karnaugh map, 1 for filling it out correctly, 1 for the correct grouping, and 1 for the final expression.

[4]


d)

Decimal	Hexadecimal	Binary	BCD
5153	1421	0011 0111 1001 1000	(1) 0100 0010 0011 0010
	1CF	0000 0001 1100 1111	
-1101		1111 1011 1011 0011	

Give 2 marks per answer.

[8]


e)

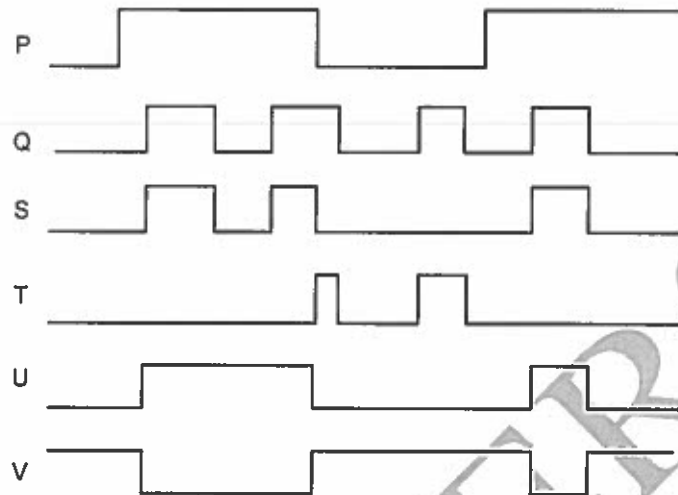

Marks: 2 marks per waveform

[8]

f)

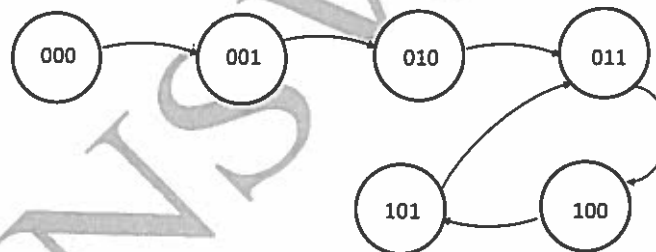

Give 2 marks correct states and 2 marks for correct interconnections.

[4]

g)

A	B	C	Y	Z
0	0	0	0	1
0	0	1	0	1
0	1	0	1	0
0	1	1	1	1
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	1


Give 0.5 marks per row of the table.

[4]

Question 2

2.

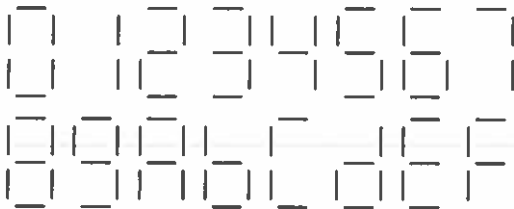(a) (i) The hexadecimal pattern is as follows:



[4]

(ii) We first draw the K-map for the top horizontal segment, with the hexadecimal number corresponding to the variables $X[3:0]$:

		X_1, X_0				
		f	00	01	11	10
X_3, X_2	00	1	0	1	1	
	01	0	1	1	1	
	11	1	0	1	1	
	10	1	1	0	1	

This gives the Boolean expression:

$$f = \overline{X_0}X_3 + X_1X_2 + X_1X_3 + \overline{X_0}X_2 + X_1X_2X_3 + X_0X_2\overline{X_3}$$

The expression may be converted directly to NAND gates only by applying De Morgan's theorem:

$$f = \overline{\overline{X_0}X_3 + X_1X_2 + X_1X_3 + \overline{X_0}X_2 + X_1X_2X_3 + X_0X_2\overline{X_3}}$$

$$= \overline{(\overline{X_0}X_3)(X_1X_2)(X_1X_3)(\overline{X_0}X_2)(X_1X_2X_3)(X_0X_2\overline{X_3})}$$

The circuit then uses 4 two-input NAND gates, 2 three-input NAND gates, 1 six-input NAND gate, and 7 inverters.

Marks: 1 marks for K-map, 1 marks for initial expression from this, 2 marks for NAND expression.

[4]

(iii)

		X1, X0			
<i>f</i>		00	01	11	10
X3, X2	00	1	0	1	1
	01	0	X	1	1
	11	1	0	1	1
	10	1	X	0	1

For a NOR implementation, we can solve in POS form:

$$\bar{f} = \overline{X1 + \bar{X0} + \bar{X3} + \bar{X2} + X1 + \bar{X3} + X2 + \bar{X0}}$$

$$\Rightarrow f = \overline{(X1 + \bar{X0}) + (X3 + \bar{X2} + X1) + (\bar{X3} + X2 + \bar{X0})}$$

Marks: 1 marks for K-map, 1 mark for the grouping and/or an initial expression, and 2 marks for the final NOR expression.

[4]

b) To determine if $A = B$ requires a bit-by-bit comparison using an XNOR gate will determine equality. To determine $A > B$ again requires a bit-by-bit comparison. Starting from the most significant bit, if $A_3 > B_3$ then $A > B$. However, if this is not true, and $A_3 = B_3$, then we need to check the next set of bits and so on. This gives the following Boolean expressions for H, E and L:

$$H = A_3 \bar{B}_3 + (\bar{A}_3 \oplus B_3) \bar{A}_2 \bar{B}_2 + (\bar{A}_3 \oplus B_3) (\bar{A}_2 \oplus B_2) \bar{A}_1 \bar{B}_1 + (\bar{A}_3 \oplus B_3) (\bar{A}_2 \oplus B_2) (\bar{A}_1 \oplus B_1) \bar{A}_0 \bar{B}_0$$

$$E = (\bar{A}_3 \oplus B_3) (\bar{A}_2 \oplus B_2) (\bar{A}_1 \oplus B_1) (\bar{A}_0 \oplus B_0)$$

$$L = \bar{A}_3 B_3 + (\bar{A}_3 \oplus B_3) \bar{A}_2 B_2 + (\bar{A}_3 \oplus B_3) (\bar{A}_2 \oplus B_2) \bar{A}_1 B_1 + (\bar{A}_3 \oplus B_3) (\bar{A}_2 \oplus B_2) (\bar{A}_1 \oplus B_1) \bar{A}_0 B_0$$

Alternatively, given H and E as above, we have: $L = \bar{H} \cdot \bar{E}$

Give 2 marks for identifying logic, and 2 marks each for the three Boolean expressions.

[8]

c) The 8 bit numbers $A[7:0]$ and $B[7:0]$ can each be broken up into two halves containing the upper four and lower four bits. We can then use COMP modules to compare $A[7:4]$ with $B[7:4]$, and $A[3:0]$ with $B[3:0]$.

[2]

Additional combinational logic is necessary to allow the H, E and L outputs of each COMP module to be compared and obtain the comparison between $A[7:0]$ and $B[7:0]$. The following logic will produce H, E and L:


$H = 1$ if $A[7:4] > B[7:4]$, OR: $A[7:4] = B[7:4]$ AND $A[3:0] > B[3:0]$.

$L = 1$ if $A[7:4] < B[7:4]$, OR: $A[7:4] = B[7:4]$ AND $A[3:0] < B[3:0]$.

$E = 1$ if $A[7:4] = B[7:4]$ AND $A[3:0] = B[3:0]$.

[4]

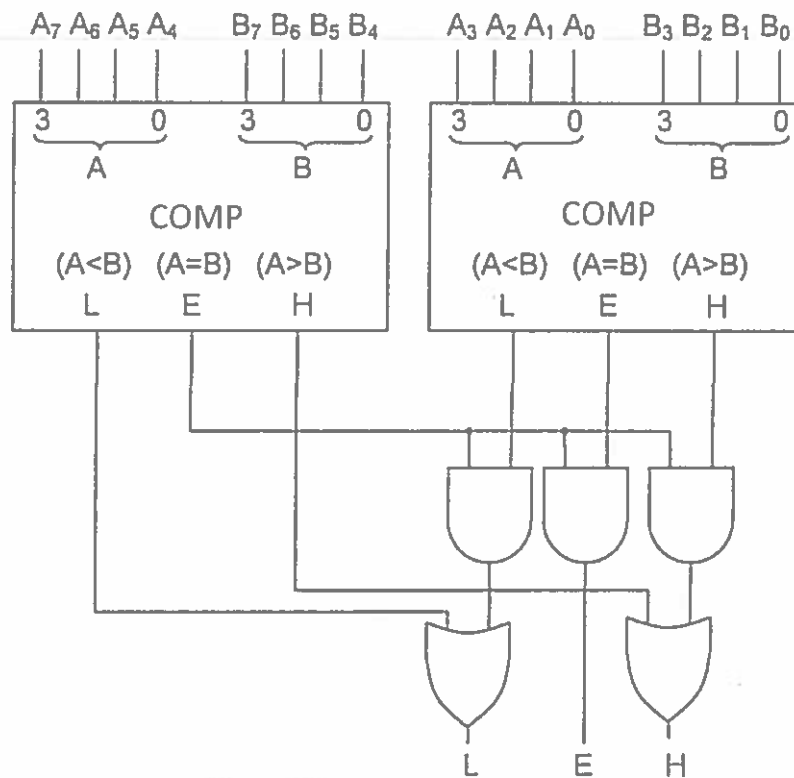This gives the following circuit diagram:



[4]

Question 3

3. a) With A, B as the present state of the FSM, A^+ , B^+ as the next state, X input and Y output, we have the following state transition table:

A	B	X	A^+	B^+	Y^+
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

Give 2 marks for basic table format and 0.5 marks for each correct row of the table.

[6]

- b) For an FSM implemented using D-flip-flops, the next state of the flip-flop is simply the present input to the flip-flop. This gives the following Karnaugh maps and Boolean equations:

For A^+ :

		AB			
		00	01	11	10
X	0	0	1	1	0
	1	0	0	0	1

$$\Rightarrow A^+ = \bar{X}B + X\bar{A}\bar{B}$$

For B^+ :

		AB			
		00	01	11	10
X	0	0	0	1	0
	1	1	0	0	1

$$\Rightarrow B^+ = X\bar{B} + \bar{X}AB$$

For Y

		AB			
		00	01	11	10
X	0	0	0	0	0
	1	1	0	0	1

$$\Rightarrow Y = X\bar{B}$$

Give 1 mark for each K-map and 1 mark for each Boolean expression.

[6]

- c) Using the result of (b) it can be seen that 2 OR gates and 4 AND gates are necessary. Note that the Y term does not need an additional AND gate as it is available within the expression for B^+ .

[4]

d) The state transition table may be redrawn with one-hot encoding as follows:

S ₃ S ₂ S ₁ S ₀	X	S ₃ ⁺ S ₂ ⁺ S ₁ ⁺ S ₀ ⁺	Y ⁺
0001	0	0001	0
0001	1	0010	1
0010	0	0100	0
0010	0	0001	0
0100	0	0001	0
0100	1	1000	1
1000	0	1000	0
1000	1	0001	0

Give 4 marks for understanding this and for drawing the table.

By inspection of the table:

$$S_3^+ = S_2 X + S_3 \bar{X}$$

$$S_2^+ = S_1 \bar{X}$$

$$S_1^+ = S_0 X$$

$$S_0^+ = S_0 \bar{X} + S_1 X + S_2 \bar{X} + S_3 X$$

$$Y = S_0 X + S_2 X$$

Give 2 marks for each expression.

[14]