

IMPERIAL COLLEGE LONDON

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING  
EXAMINATIONS 2003

EEE PART III/IV: M.Eng., B.Eng. and ACGI

**ELECTRICAL ENERGY SYSTEMS**

Wednesday, 7 May 10:00 am

Time allowed: 3:00 hours

There are SIX questions on this paper.

Answer FOUR questions.

**Corrected Copy**

*Correction to Q4.  
(made c. 10.30 am)*

*Q2.  
(11.30 am)*

**Any special instructions for invigilators and information for candidates are on page 1.**

Examiners responsible

First Marker(s) : B.C. Pal, D. Popovic

Second Marker(s) : D. Popovic, B.C. Pal



1. Suppose that a radial line of length  $l$  which connects buses 1 and 2 is terminated in its characteristic impedance  $Z_c$  at bus 2. The propagation constant  $\gamma = \alpha + j\beta$ .
  - (a) Find the impedance  $V_1/I_1$ , the voltage gain  $|V_2|/|V_1|$ , the current gain  $|I_2|/|I_1|$ , the complex gain  $-S_{21}/S_{12}$  where  $-S_{21} = V_2 I_2^*$  and  $S_{12} = V_1 I_1^*$ , and the real power efficiency  $-P_{21}/P_{12}$ . [12]
  - (b) Repeat part (a) for the case of a lossless line. [8]

2. Draw a per-unit diagram for the system whose one-line diagram is shown in Figure 2.1 The three phase and line-line ratings are as follows:

Generator G: 15 MVA, 13.8 kV,  $X = 0.15$  p.u.

Motor M1: 5 MVA, 13.2 kV,  $X = 0.15$  p.u.

Motor M2: 5 MVA, 14.4 kV,  $X = 0.15$  p.u.

Transformer T1: 25 MVA, 13.2/161 kV,  $X = 0.1$  p.u.

Transformer T2: 15 MVA, 13.8/161 kV,  $X = 0.1$  p.u.

Line:  $j100\ \Omega$  (actual)

Select a base of 100 MVA and 161 kV in the transmission line.

[20]

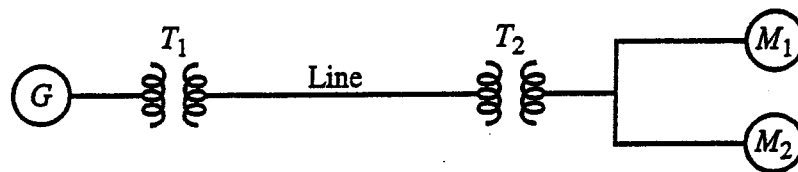


Figure 2.1

3. Figure 3.1 shows a single-line diagram of a three-bus power system. All data are in per-unit. The elements of the symmetric bus admittance matrix  $Y_{BUS}$  are as follows:

$$Y_{11} = Y_{22} = Y_{33} = -j19.98$$

$$Y_{12} = Y_{13} = Y_{23} = j10$$

- (a) Write the power-flow equations to be solved by the Newton-Raphson method. Identify the unknown variables to be solved. [8]
- (b) Use Newton-Raphson method to compute  $\theta_2$ ,  $|V_3|$ ,  $\theta_3$ ,  $S_{G1}$  and  $Q_{G2}$  after two iterations. Use zero initial phase angles and 1.0 per-unit initial bus voltage magnitudes. [12]

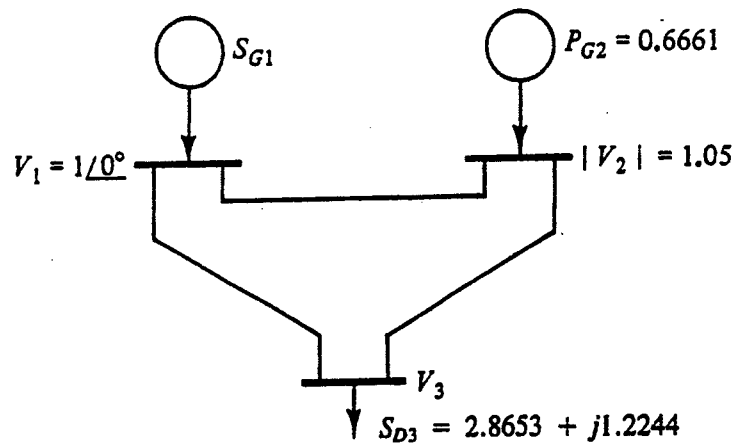


Figure 3.1

4. (a) Why do fuel cost characteristics in fossil-fuel units have minimum limits? [4]
- (b) An area of an interconnected power system has two fossil-fuel units operating on economic dispatch. The variable operating costs of these units are given by

$$C_1 = 10P_1 + 0.008P_1^2 \quad \$/hr \quad 100 \leq P_1 \leq 600 \quad (4.1)$$

$$C_2 = 8P_2 + 0.009P_2^2 \quad \$/hr \quad 400 \leq P_2 \leq 1000 \quad (4.2)$$

where  $P_1$  and  $P_2$  are in MW. Determine the power output of each unit, the incremental operating cost(s) and the total operating cost,  $C_T$ , that minimises cost of operation ( $C_T$ ) for load demand of 1000 and 1400 MW respectively. Transmission losses are neglected. [16]

5. (a) Why is it so important to have constant frequency in system operation? [5]
- (b) Figure 5.1 shows a simple power system supplying power of  $P + jQ$  to a load at voltage  $V$  and at a lagging power factor. The line connecting the sending and the receiving end has an impedance  $R + jX$ .  $\delta$  is the angle between the vectors  $E$  and  $V$ . Show that

$$\Delta V_p = \frac{RP}{V} + \frac{XQ}{V} \quad \text{and} \quad \Delta V_q = \frac{XP}{V} - \frac{RQ}{V}$$

when  $E^2 = (V + \Delta V_p)^2 + \Delta V_q^2$ . When  $X \gg R$  and  $\delta$  is expressed in radian, also show that  $Q \propto \Delta V_p$  and  $P \propto \delta$  in the range  $0 < \delta < \frac{\pi}{4}$ . [15]

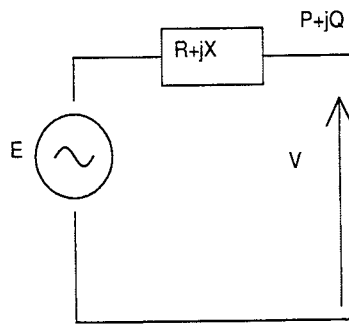


Figure 5.1: A simple power system

6. (a) What is the method of symmetrical components? Discuss its advantages over phase systems? [5]
- (b) Given the line-to-ground voltages  $V_{ag} = 280\angle 0^\circ$ ,  $V_{bg} = 250\angle -110^\circ$  and  $V_{cg} = 290\angle 130^\circ$  volts, calculate in volts
- (i) line-to-line voltages  $V_{ab}$ ,  $V_{bc}$  and  $V_{ca}$  [3]
  - (ii) the sequence components of the line-to-ground voltages  $V_{Lg1}$ ,  $V_{Lg2}$  and  $V_{Lg0}$  [5]
  - (iii) the sequence components of the line-to-line voltage,  $V_{LL1}$ ,  $V_{LL2}$  and  $V_{LL0}$ .  
Also, verify that  $V_{LL1} = \sqrt{3}V_{Lg1}\angle +30^\circ$  and  $V_{LL2} = \sqrt{3}V_{Lg2}\angle -30^\circ$ . [7]