

Question 1

1. a) (i)

$$\begin{aligned} & \overline{A(B+AC)} \\ &= \overline{A(B(AC))} \\ &= \overline{AB(A+C)} \\ &= \overline{AB} + \overline{ABC} \\ &= \overline{AB} \end{aligned}$$

[4]

ii)

$$\begin{aligned} & B + (C \oplus \overline{B})(AB + \overline{C}) \\ &= B + (CB + \overline{C}\overline{B})(AB + \overline{C}) \\ &= B + ABC + \overline{C}\overline{B} \\ &= B + \overline{C}\overline{B} \\ &= B + \overline{C} \end{aligned}$$

[4]

b)

$$\begin{aligned} f &= A\overline{B} + C(\overline{D} \oplus (A \oplus B)) + A\overline{C}D \\ &= A\overline{B} + C(\overline{D}(\overline{A \oplus B}) + D(A \oplus B)) + A\overline{C}D \\ &= A\overline{B} + C(\overline{D}(AB + \overline{A}\overline{B}) + D(\overline{A}B + A\overline{B})) + A\overline{C}D \\ &= A\overline{B} + ABC\overline{D} + \overline{A}BC\overline{D} + \overline{A}BCD + A\overline{B}CD + A\overline{C}D \end{aligned}$$

Here, 2 marks for simplifying the given equation into a form suitable for a Karnaugh map

The equation can now be simplified further using a Karnaugh map:

f

$AB \backslash CD$	00	01	11	10
00	0	0	0	1
01	0	0	1	0
11	0	1	0	1
10	1	1	1	1

$$\Rightarrow f = A\bar{B} + A\bar{C}D + AC\bar{D} + \bar{B}C\bar{D} + \bar{A}BCD$$

Here, 1 mark for drawing the Karnaugh map, 1 for filling it out correctly, 1 for the correct grouping, and 1 for the final expression.

[6]

c)

f

$AB \backslash CD$	00	01	11	10
00	1	1	1	0
01	0	0	1	1
11	0	0	1	1
10	0	0	1	0

$$\Rightarrow f = (\bar{A} + C)(\bar{B} + C)(B + \bar{C} + D)$$

Here, 1 mark for drawing the Karnaugh map, 1 for filling it out correctly, 1 for the correct grouping, and 1 for the final expression.

[4]

d)

Decimal	Hexadecimal	Signed binary	Octal
-2049	F7FF		
		0000 0111 1101 0110	3726
4011	FAB		
-14440		1100 0111 1001 1000	

Give 2 marks per answer.

[8]

e) With two N bit numbers multiplied together, the result has the range:

$$-(2^{2N-2} - 2^{N-1}) \text{ to } 2^{2N-2}$$

[2]

This needs 2N bits. Note that it nearly fits into 2N-1 bits, whose range extends to $2^{2N-2} - 1$.

[2]

f)

Current state	Input	Next state	Output (PQ)	
S0	0	S0	0	1
S0	1	S1	1	0
S1	0	S2	1	1
S1	1	S1	1	0
S2	0	S0	0	1
S2	1	S1	1	0
S3	X	S0	0	1

Give 1 mark for correct current state, 1 for correct inputs, 1 for correct next state and 1 for correct outputs.

[4]

g)

A	B	C	S1 = D0	S0 = A	Q
0	0	0	0	0	0
0	0	1	1	0	1
0	1	0	0	0	1
0	1	1	1	0	1
1	0	0	0	1	0
1	0	1	1	1	1
1	1	0	0	1	0
1	1	1	1	1	1

Give 2 marks for understanding ROM/multiplexer operation, and 2 each for outputs D0 and Q.

[6]

Question 2

2. (a) (i) The required encoder has 12 input lines $I[11:0]$, where only one of these can be zero (active) at a time. There are four output lines $D[3:0]$, giving the binary equivalent of the hexadecimal values 0 – B.

2 marks for understanding the above.

The truth table is then as follows:

Number	I11	I10	I9	I8	I7	I6	I5	I4	I3	I2	I1	I0	D3	D2	D1	D0
0	0												0	0	0	0
1		0											0	0	0	1
2			0										0	0	1	0
3				0									0	0	1	1
4					0								0	1	0	0
5						0							0	1	0	1
6							0						0	1	1	0
7								0					0	1	1	1
8									0				1	0	0	0
9										0			1	0	0	1
10 (A)											0		1	0	1	0
11 (B)												0	1	0	1	1

For clarity, the deactivated input values in the above table are left as empty cells. These are occupied by 1s (deactivated).

2 marks for the inputs and 2 for the outputs.

[6]

- (ii) The Boolean expressions for $D[3:0]$ can be seen by inspection:

$$D0 = (\overline{I1})(\overline{I3})(\overline{I5})(\overline{I7})(\overline{I9})(\overline{I11})$$

$$D1 = (\overline{I2})(\overline{I3})(\overline{I6})(\overline{I7})(\overline{I10})(\overline{I11})$$


$$D2 = (\overline{I4})(\overline{I5})(\overline{I6})(\overline{I7})$$

$$D3 = (\overline{I8})(\overline{I9})(\overline{I10})(\overline{I11})$$

2 marks for each expression.

[8]

(b)

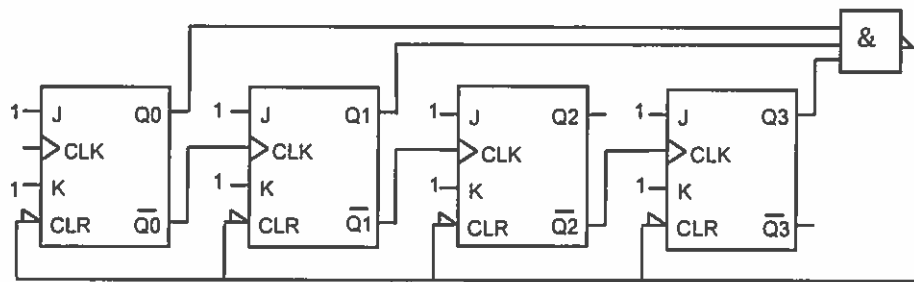

4 marks for correct use of the J-K flip-flops and 2 for the asynchronous reset.

[6]

c) (i) The given Boolean function is:

$$f = \overline{A}\overline{B} + AB + \overline{A}C$$

This corresponds to the truth table:

A	B	C	f
0	0	0	1
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	1


[1]

As BC must be used on the select lines of the 4×1 MUX, we draw a k-map table, with BC arranged along the rows and A along the columns. Furthermore, we choose to connect $C = S_0$ and $B = S_1$.

		S_1		S_0	
		BC			
A		00	01	11	10
	0	1	1	1	0
	1	0	0	1	1
		$I_0 = \overline{A}$	$I_1 = \overline{A}$	$I_3 = 1$	$I_2 = A$

[2]

This gives the following implementation:

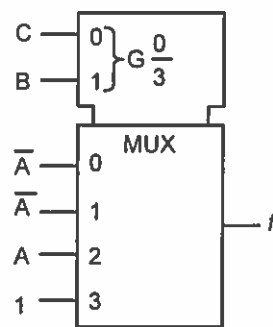

Note: The alternative solution has $B = S_0$ and $C = S_1$. We would then have $I_0 = A(\text{bar})$, $I_1 = A$, $I_3 = 1$, and $I_2 = A(\text{bar})$.

[1]

(ii) Using two 2×1 MUXs, we first need to rearrange the given function in the form of the Boolean function for the output Z for a 2×1 MUX, with select input S:

$$Z = \bar{S}I_0 + SI_1$$

For the given function, we then have:

$$\begin{aligned} f &= \bar{A}\bar{B} + AB + \bar{A}C \\ &= \bar{A}(\bar{B} + C) + AB \end{aligned}$$

[2]

Comparison with the expression for Z implies that:

$$I_0 = (\bar{B} + C) = g$$

$$I_1 = B$$


$$S = A$$

We then need to implement $\bar{B} + C$ using a second 2×1 MUX. Here, either B or C could be connected to the select line. Choosing C for the select line (the alternative of B on the select line is also fine) and inspecting the following map:

		S	
		C	
B	0	0	1
	1	0	1
		I_0	I_1
		$= \bar{B}$	$= 1$

[2]

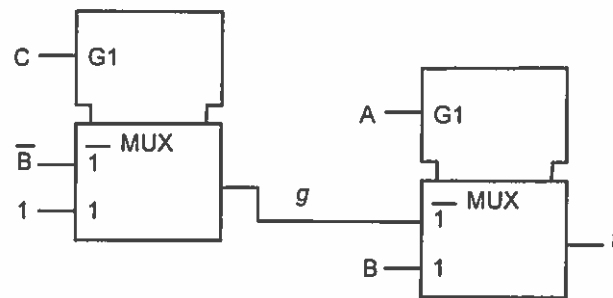This allows implementation of the second 2×1 MUX, with $I_0 = \overline{B}$ and $I_1 = 1$. We then have the following final implementation:




[2]

Question 3

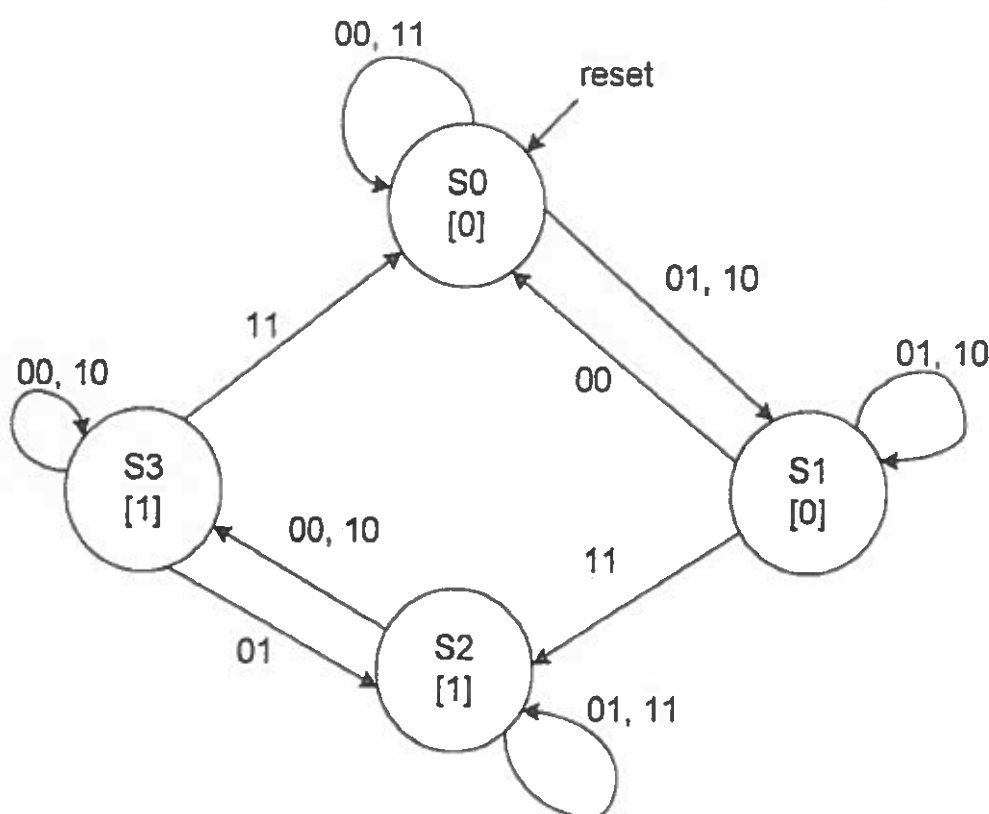3. (a) Using the states S0, S1, S2 and S3 to define the FSM, the following state diagram can be obtained. Note that as there are two inputs X1, X2, each state has $2^2 = 4$ transitions possible. Furthermore, a sequence of two input combinations, one after the other, is needed to change the output. For example, for the sequence $X_1X_2 = 01, 11$, the first part, $X_1X_2 = 01$ causes a transition from S0 to S1, and the second part, $X_1X_2 = 11$, causes a transition from S1 to S2, and $Z = 0$ to $Z = 1$.

Give 2 marks for identifying this reasoning.



Give 2 marks for showing four states, 4 for the correct interconnections, and 4 for the correct input/output values.

[12]

- (b) Using the encoding system given, the state diagram can be converted into the following table, with $Q_3Q_2Q_1Q_0$ as the present state of the FSM, and $Q_3^+Q_2^+Q_1^+Q_0^+$ as the next state:

Q3	Q2	Q1	Q0	X1	X2	Q3*	Q2*	Q1*	Q0*	Z
0	0	0	1	0	0	0	0	0	1	0
0	0	0	1	0	1	0	0	1	0	0
0	0	0	1	1	0	0	0	1	0	0
0	0	0	1	1	1	0	0	0	1	0
0	0	1	0	0	0	0	0	0	1	0
0	0	1	0	0	1	0	0	1	0	0
0	0	1	0	1	0	0	0	1	0	0
0	0	1	0	1	1	0	1	0	0	0
0	1	0	0	0	0	1	0	0	0	1
0	1	0	0	0	1	0	1	0	0	1
0	1	0	0	1	0	1	0	0	0	1
0	1	0	0	1	1	0	1	0	0	1
1	0	0	0	0	0	1	0	0	0	1
1	0	0	0	0	1	0	1	0	0	1
1	0	0	0	1	0	1	0	0	0	1
1	0	0	0	1	1	0	0	0	1	1

Give 0.5 marks for each row.

[8]

(c) As the FSM states are encoded using 1-hot encoding, the Boolean equations can be written directly by inspection:

$$Q0^* = \overline{Q0}X1\overline{X2} + \overline{Q0}X1X2 + \overline{Q1}\overline{X1}\overline{X2} + Q3X1X2$$

$$Q1^* = \overline{Q0}X1\overline{X2} + \overline{Q0}\overline{X1}X2 + \overline{Q1}\overline{X1}X2 + \overline{Q1}X1\overline{X2}$$

$$Q2^* = \overline{Q1}X1X2 + \overline{Q2}\overline{X1}X2 + \overline{Q2}X1X2 + \overline{Q3}\overline{X1}X2$$

$$= \overline{Q1}X1X2 + \overline{Q2}X2 + \overline{Q3}\overline{X1}X2$$

$$Q3^* = \overline{Q2}\overline{X1}\overline{X2} + \overline{Q2}X1\overline{X2} + \overline{Q3}\overline{X1}\overline{X2} + \overline{Q3}X1\overline{X2}$$

$$= \overline{Q2}\overline{X2} + \overline{Q3}\overline{X2}$$

$$Z = Q2 + Q3$$

Give 2 marks for each Boolean expression.

[10]