 


E1.4 SOLUTIONS

Question 1

a) To simplify analysis leading to I_E , replace bias network by Thévenin equivalent:



$$\text{where } V_{\text{BIAS}} = 10 \times 22 / (22 + 100) = 1.803 \text{ V}$$

$$\text{and } R_B = 100\text{k} // 22\text{k} = 18.03 \text{ k}\Omega$$

$$\text{KVL gives: } I_E R_E + V_{\text{BE}} + I_B R_B = V_{\text{BIAS}}$$

$$\Rightarrow I_E = (V_{\text{BIAS}} - V_{\text{BE}}) / [R_E + R_B / (1 + \beta)]$$

$$\text{Assuming } V_{\text{BE}} = 0.7 \text{ V, this gives } I_E = 1.012 \text{ mA}$$

Assuming transistor active, $I_C = \alpha I_E = 1.007 \text{ mA}$.

Check mode: with $I_C = 1.007 \text{ mA}$, $V_C = 10 - 1.007\text{m} \times 5.6\text{k} = 4.36 \text{ V} > V_B$ so active assumption correct. [6]

R_E stabilises the bias current by providing negative feedback. Any change in collector current (for example, due to temperature variations), will produce an opposing change in V_{BE} , via the voltage dropped across R_E . [2]


b) Start by assuming both devices are active (for ease of analysis). In this case the upper device, with $V_{\text{GS}} = 0$, will have a drain current of $I_D = I_{\text{DSS}} = K V_t^2 = 0.2 \text{ mA}$.

The lower device, for which $V_{\text{DS}} = V_{\text{GS}} = V$, must be carrying the same current, so we have $0.2\text{m} = 0.1\text{m} \times (V - 1)^2$. Taking the square root, with +ve sign (since we are assuming the device is above threshold) gives $V = (1 + \sqrt{2}) = 2.414 \text{ V}$.

Lower device: $V_{\text{DS}} = V_{\text{GS}} > V_t$, so **lower device is ACTIVE**.

Upper device: $(V_{\text{DS}} = 5 - 2.414 = 2.586 \text{ V}) > (V_{\text{GS}} - V_t = 1 \text{ V})$, so **upper device is ACTIVE**. [6]

c) Widlar current sink:

 

Ignoring base current, KVL in the loop including R and the EBJs gives:

$$V_{\text{BE1}} = V_{\text{BE2}} + I_{\text{OUT}} R$$

Using the reduced Ebers-Moll eqn we can express the V_{BE} s in terms of the input and output currents:

$$V_T \ln(I_{\text{IN}}/I_S) = V_T \ln(I_{\text{OUT}}/I_S) + I_{\text{OUT}} R$$

Cleaning this up gives:

$$V_T \ln(I_{\text{IN}}/I_{\text{OUT}}) = I_{\text{OUT}} R \quad \text{or} \quad I_{\text{IN}} = I_{\text{OUT}} \exp(I_{\text{OUT}} R / V_T)$$

schematic + analysis = [4 + 4]

d) According to the resistance reflection rule, the input resistance at the base of a BJT is equal to $[r_{be} + (1 + \beta) \times R]$ where r_{be} is the base-emitter resistance and R is the external resistance between the emitter and ground. In the case of the Darlington shown, the resistance in the emitter of Q1 is the parallel combination of R_E and the r_{be} of Q2. The input resistance at the base of Q1 is therefore:

$$R_i = r_{be1} + (1 + \beta_1)(R_E // r_{be2})$$

Alternative solution based on analysis of the SSEC also acceptable.

[6]

e) Initial condition (for $t < 0$): if the input voltage has been +5 V for a long time, the capacitor current will have dropped to zero and the voltage $V_{CAP} = (V_{IN} - V_B)$ across it will be $V_{CAP} = 5 - 0.7 = +4.3$ V. The base will be at 0.7 V because of the base current provided via the 100 k Ω resistor. The value of this current will be $I_B = (5 - 0.7)/100k = 43 \mu A$. Since $\beta I_B \times 1k = 8.6 > 5$ V, we know that the transistor is saturated, and the output voltage will be $V_{OUT} = 0.2$ V.

At $t = 0+$: V_{CAP} cannot change instantaneously, so when V_{IN} falls suddenly to 0 V, V_B will fall suddenly to -4.3 V and the transistor will cut off causing the output to go high.

For $t > 0$: current flowing via the 100 k Ω resistor will charge the capacitor causing V_B to rise. In the absence of the transistor the asymptotic value of V_B would be +5 V. Using the standard result for an RC network, the initial time-variation of V_B is therefore of the form:

$$V_B = 5 + (-4.3 - 5) \exp(-t/\tau)$$

where $\tau = 10n \times 100k = 1$ ms.

The transistor will turn on again, and the output will go low, when V_B reaches ~0.7 V. The pulse duration T will therefore satisfy:

$$0.7 = 5 - 9.3 \exp(-T/\tau) \quad \text{or} \quad T = \tau \ln(9.3/4.3) = 0.77 \text{ ms}$$

[8]

f) The essential elements of a sinusoidal oscillator are a frequency selective block and an amplifying block. These must be connected to form a loop. In order for the circuit to produce stable sinusoidal oscillations, the total gain around the loop must be unity at a unique frequency.


[4]

Question 2

a) Assuming $V_{BE} \approx 0.7$ V, the potential at the base/collector of Q3 is -4.3 V, and the input current to the current mirror formed by Q3, Q4 is $4.3/20k = 215 \mu A$. Taking into account the finite beta error, the output current of the current mirror is $I = 215\mu/(1 + 2/\beta) = 211 \mu A$. [5]

If $V_{IN1} = V_{IN2}$ then the tail current will divide equally between Q1 and Q2, and the collector currents of these transistors will be $I_{C1} = I_{C2} = \alpha I/2 = 105 \mu A$. The quiescent output voltage will then be $V_{OUT} = 5 - 20k \times 105\mu = 2.9$ V. [3]

b) SSEC:

 


If the input signal is a purely differential voltage v_d , as shown, then by symmetry we can say that $v_e = 0$. In this case $v_{be2} = -v_d/2$, the output current of Q2 is $-g_m v_d/2$, and the output voltage is $v_{out} = g_m R_C v_d/2$. The single-ended differential gain is then $A_d = v_{out}/v_d = g_m R_C/2$. [6]

Putting $g_m = I_{C2}/V_T = 4.2$ mS (using $V_T = 25$ mV) gives $A_d = 42$. [4]

The input currents are $\pm i_{in}$ where $i_{in} = v_d/2r_{be}$. The differential input resistance is therefore $R_i = v_d/i_{in} = 2r_{be} = 2\beta/g_m$, which gives $R_i = 47.6$ k Ω . The output resistance is $R_o = 20$ k Ω . [3]

Macromodel:

 

c) Q4 has a finite output resistance given by $r_{o4} = V_A/I$ where V_A is the Early voltage. This needs to be added to the SSEC between the common emitter node of Q1, Q2 and ground. [4]


For the common-mode gain calculation, where $v_{in1} = v_{in2} = v_{in}$, we can again exploit the symmetry of the circuit and analyse just the RH half-circuit as a common-emitter stage with a collector resistance R_C and an emitter resistance $2r_{o4}$. Using the standard result (no need to prove it), the common-mode gain is then $A_{cm} = -\alpha R_C/2r_{o4}$. With $V_A = 120$ V and $I = 211 \mu A$, $r_{o4} = 569$ k Ω and $A_{cm} = -0.0174$. [5]

The common-mode rejection ratio is then $|A_d/A_{cm}| = 42/0.0174 = 2414$ (allow for rounding).

Calculation based a standard formula, e.g. $|A_d/A_{cm}| = V_A/2V_T$, is also acceptable.

Question 3

a) SSEC ignoring r_o is:

 

From the SSEC, we have:

$$\begin{aligned} V_{out} &= g_m V_{gs} R_S = g_m (v_{in} - v_{out}) R_S \\ \Rightarrow v_{out} (1 + g_m R_S) &= g_m R_S v_{in} \\ A_v = v_{out}/v_{in} &= g_m R_S / (1 + g_m R_S) \end{aligned}$$

Applying a test source v_x to the output with $v_{in} = 0$, the current into the output will be:

$$\begin{aligned} i_x &= v_x / R_S + g_m v_x \\ \Rightarrow R_o = v_x / i_x &= 1 / (1/R_S + g_m) = R_S // (1/g_m) \end{aligned}$$


gain + output resistance = [6 + 4]

b)i) The $10\text{ M}\Omega$ resistor sets the operating points of Q1 and Q2 by forcing the DC voltages at input and output to be equal (because $I_{G1} = 0$). The quiescent output voltage must therefore be whatever gate voltage is required to give a drain current of 1 mA in Q1. We can therefore write: $1\text{ mA} = K_1 (V_{OUT} - V_{t1})^2$, with $K_1 = 0.25\text{ mA/V}^2$ and $V_{t1} = 1\text{ V}$. Taking the +ve square root (Q1 above threshold) gives $V_{OUT} = 3\text{ V}$. [4]

With $V_{OUT} = 3\text{ V}$, the drain current of Q2 is $I_{D2} = 3\text{ mA}$. [2]

If Q2 is carrying 3 mA then its gate-source voltage must satisfy $3\text{ mA} = K_2 (V_{GS2} - V_{t2})^2$. With $K_2 = 1.5\text{ mA/V}^2$ and $V_{t2} = 1\text{ V}$, and once again taking the +ve square root, this gives $V_{GS2} = (1 + \sqrt{2})$, implying that $V_X = (4 + \sqrt{2})\text{ V}$. [2]

b)ii) SSEC in mid-band:

 

From the SSEC, ignoring the $10\text{ M}\Omega$:

$$\begin{aligned} v_x &= -g_{m1} V_{g1} r_{o1} = -g_{m1} v_{in} r_{o1} \\ \Rightarrow A_{v1} &= -g_{m1} r_{o1} \\ \text{Putting } g_{m1} &= 2\sqrt{(K_1 I_{D1})} = 1\text{ mA/V and } r_{o1} = V_A / I_{D1} = 100\text{ k}\Omega, A_{v1} = -100. \end{aligned}$$

SSEC + analysis = [4 + 4]

b)iii) Using the result given in part a), the gain of the source follower is;

$$A_{v2} = R_S / (R_S + 1/g_{m2}) \quad \text{with } R_S = 1\text{ k}\Omega$$

With $g_{m2} = 2\sqrt{(K_2 I_{D2})} = 3\sqrt{2}\text{ mA/V}$ (corresponding to $1/g_m = 236\text{ }\Omega$) this gives $A_{v2} = 0.809$. The overall gain A_v is just the product of the two individual stage gains, so $A_v = -80.9$.

Using the result from part a), the output resistance is $(1\text{ k}/236) = 191\text{ }\Omega$ [4]