

1. This question consists of 5 sub-questions. Each item can be answered in a few words or a short paragraph with use of a diagram and/or expression where helpful. Please answer all sub-questions and simplify expressions where possible stating any assumptions made.

a) Which of the topologies shown below in Fig. 1.1 would have better performance? Explain why. [5]

 


Fig. 1.1(a)

 


Fig. 1.1(b)


Although both the circuits have the same function [1]
 — common source amplifier with active load
 ($A_v = -g_{m_x}(r_{o1} || r_{o2})$ with $x =$ CS amplifier transistor), [1]
 in ckt. (a) amplifier is NMOS whereas in (b) is
 PMOS. Assuming device sizes are identical
 design (a) would be preferable. This is
 because $\mu_n > \mu_p$ (approx. $\times 3$) [1] and therefore
 $g_m(\text{NMOS amp}) > g_m(\text{PMOS amp})$ [1] $\therefore A_v$ also
 higher. [1]

most students identified fact that topologies are
 the same \rightarrow but attributed difference to
 body effect and not mobility. Body
 effect is not relevant as $V_{SB} = 0$ for
 both.

- b) Propose a circuit topology (e.g. common source amplifier with resistive load), for each of the following applications, in each case justifying your selection, and sketching the circuit schematic.

(i) A pre-amplifier to interface to a capacitive microphone.

[5]

 


A capacitive microphone would have a very high impedance \therefore [1]
can provide no output current so amp with very high Z_{in} [1]
needed not to load. Such an amp. is CS amplifier (MOSFET) also to provide moderate [1]
voltage gain.

Many students incorrectly attempted to propose a circuit for good high frequency performance. [5]

(ii) A circuit to increase the DC level of a signal by 1V.

[5]

 


CS (or source follower) stage(s) biased with constant current - appropriate for level shift. [1]
Each stage can achieve $+V_{GS}$ DC level shift. Suggest 2 stages identical \rightarrow each $+0.5V$ (Amos) [1]

Surprisingly about 1/2 students proposed CS topology. Very few mentioned 2 stages.

(iii) A high frequency amplifier providing relatively high isolation between the input and output.

[5]

 

CG (or CB) amplifier exhibit very good high frequency response as there is no parasitic capacitance between i/p and o/p. [1]
As a result does not suffer from the Miller effect. [1] Furthermore CG amp can be designed to match a 50 Ω load (since $Z_{in} \approx 1/g_m$). [1]

Most correct. Confused by "isolation" [1]

- c) An inverting amplifier must provide a nominal gain of 20 with a gain error of 0.5%. Determine the minimum required op-amp gain.

$$\text{Gain error} = \frac{1}{A_o} \left(1 + \frac{R_1}{R_2}\right) \quad [5] \quad [3] - 2 \text{ for deriving} \\ 1 \text{ for expression}$$

$$\frac{1}{A_o} (1+20) = 0.5\% \rightarrow A_o = 4200 \quad [1] \quad [1]$$

very well answered.

- d) Determine the closed loop gain of the circuit shown below in Fig. 1.2. Assume $\lambda = 0$.

[5]


 


Fig. 1.2

Break the loop:

 

$$\left. \frac{V_{out}}{V_{in}} \right|_{\text{open-loop}} = \frac{V_{out}}{V_x} \cdot \frac{V_x}{V_{in}} = \frac{-R_{D1}}{\frac{1}{g_{m1}} + R_1 \parallel R_2} \times -g_{m2} (R_1 + R_2) \quad [2]$$

$$= \frac{g_{m1} g_{m2} R_{D1} (R_1 + R_2)}{1 + g_{m1} (R_1 \parallel R_2)} \quad [2]$$

$$k = \frac{R_2}{R_1 + R_2}$$

$$\therefore A_v \bigg|_{\text{closed-loop}} = \frac{A_v(\text{OL})}{1 + k A_v(\text{OL})} = \frac{\frac{g_{m1} g_{m2} R_{D1} (R_1 + R_2)}{1 + g_{m1} (R_1 \parallel R_2)}}{1 + \frac{g_{m1} g_{m2} R_{D1} R_2}{1 + g_{m1} (R_1 \parallel R_2)}} \quad [1]$$

like wise. Most answered correctly

- e) Derive expressions (by inspection) for the *output resistance* of the amplifier circuits shown below in Fig. 1.2 (including r_o).

[10]

 


Fig. 1.2(a)


 


Fig. 1.2(b)

 (i) R_G effectively makes M_2 diode connected [1]




Many students identified no current through R_G so removed. Only about 1/4 identified that it makes M_2 effectively diode-connected.

$$\therefore R_{out} = g_{m1} r_{o1} \left(\frac{1}{g_{m2}} \parallel r_{o2} \right) + r_{o1} + \frac{1}{g_{m2}} \parallel r_{o2} [1]$$

$$\approx g_{m1} r_{o1} \left(\frac{1}{g_{m2}} \parallel r_{o2} \right) [1]$$

 (assuming 1st term greater than others) [1]



$$R_{out} = r_{o1} + g_{m1} (R_1 \parallel r_{\pi 2} \parallel r_{\pi 1}) r_{o1} + R_1 \parallel r_{\pi 1} \parallel r_{\pi 2} [1]$$

$$= r_{o1} + (1 + g_{m1} r_{o1}) (r_{\pi 1} \parallel R_1 \parallel r_{\pi 2}) [1]$$

Answered well

1 mark for not simplifying/approximating

2. The circuit shown below in Fig. 2.1 is a single-stage fully differential amplifier with corresponding transistor dimensions shown in Table 2.1.

 


Fig. 2.1

Table 2.1. Transistor sizes

M_1	M_2	M_3	M_4	M_5	M_6	M_7
200/0.5	200/0.5	9/0.18	9/0.18	50/1	50/1	50/1

Assume all devices are in saturation and assume $\lambda \neq 0$. Use the following expression for the large signal drain current of a MOSFET (in saturation) with corresponding transistor parameters:


$$I_D = \frac{1}{2} \mu C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2$$

$$\begin{aligned} \mu_n C_{ox} &= 200 \mu\text{A/V}^2 \\ \mu_p C_{ox} &= 100 \mu\text{A/V}^2 \end{aligned}$$

$$\begin{aligned} V_{THN} &= 0.4\text{V} \\ V_{THP} &= -0.5\text{V} \end{aligned}$$

$$\begin{aligned} \lambda_N &= 0.1\text{V}^{-1} \\ \lambda_P &= 0.2\text{V}^{-1} \end{aligned}$$

 - a) Design a voltage reference circuit to generate V_{b2} from a 1.8V supply such that $I_{D7} = 2\text{mA}$. [5]



$$\begin{aligned} V_{b2} = V_{GS7} &= \sqrt{\frac{2I_{D7}}{\mu_n C_{ox} \left(\frac{W}{L}\right)_7}} + V_{THN} \\ &= \sqrt{\frac{2(2\text{mA})}{200 \mu\text{A/V}^2 (50)}} + 0.4 \\ &= 1.03\text{V} \end{aligned}$$

Assuming 1:1 mirror $M_{ref} \left(\frac{W}{L}\right) = \frac{50}{1}$


$$R_{Bias} = \frac{1.8 - 1.03}{2\text{mA}} = 385\Omega$$

most students designed a potential divider
→ ok → but I expected mention of
sensitivity to VDD variation

 b) Determine an expression for the differential voltage gain of the amplifier.

[5]

Assuming perfect symmetry \rightarrow equivalent $1/2$ ckt approx. [1]



\therefore CS amplifier

$$A_v = -g_m (R_D \parallel r_o) \quad [1]$$

$$= -g_{m1} (r_{o1} \parallel (g_{m3} r_{o3} r_{o5} + r_{o3} + r_{o5})) \quad [1]$$

$$\approx -g_{m1} r_{o1}$$



$$(\text{since } r_{o1} \ll g_{m3} r_{o3} r_{o5}) \quad [1]$$

many students missed this

  c) Determine an expression for the common-mode voltage gain of the amplifier.

[5]

Short $v_{in1} = v_{in2}$ and draw eqn. ckt. for CM gain



$A_v =$ CS with degen.

$$= \frac{-R_D}{1/g_m + R_S} \quad [1]$$

$$= \frac{-g_{m3} r_{o3} r_{o5}}{2} \cdot \frac{1}{\frac{1}{2g_{m1}} + r_{o7}}$$

$$= \frac{-2g_{m1} g_{m3} r_{o3} r_{o5}}{2(1 + 2g_{m1} r_{o7})} \quad [1]$$

\downarrow
Since $g_{m1} r_{o7} \gg 1$

$$\approx \frac{-g_{m3} r_{o3} r_{o5}}{2 r_{o7}} \quad [1]$$

Here several students incorrectly used $G_m = g_{m1}$.

d) Use your answers to parts (b) and (c) to evaluate the common-mode rejection ratio.

[10]

$$CMRR = \frac{A_v(OM)}{A_v(CM)} \quad [1]$$

$$A_v(OM) = -g_{m1} r_{o1}$$

$$g_{m1} = \sqrt{2I_D \mu_n C_{ox} \frac{W}{L}} = \sqrt{2(1mA) 200\mu(400)} = 12.6mS$$

$$r_{o1} = 1/\lambda_n I_D = 1/(0.01)(1mA) = 10k\Omega$$

$$\therefore A_v = -126.49 \quad [1]$$

[2]

$$A_v(CM) = \frac{-g_{m3} r_{o3} r_{o5}}{2r_{o7}}$$

$$g_{m3} = \sqrt{2(1mA)(100\mu)(50)} = 3.16mS$$

$$r_{o3} = 1/\lambda_p I_{D3} = 1/0.2(1mA) = 5k\Omega$$

$$r_{o5} = 1/\lambda_p I_{D5} = 1/0.2(1mA) = 5k\Omega$$

$$r_{o7} = 1/\lambda_n I_{D7} = 1/0.1(2mA) = 5k\Omega$$

$$A_v(CM) = \frac{-3.16mS(5k)(5k)}{2(5k)} = -7.9 \quad [1]$$

$$CMRR = \frac{126.49}{7.9} = 16.01 \quad [1]$$

$$= 20\log(16.01) = 24.1dB \quad [1]$$

Good

e) State the function of transistors $M_1 - M_2$, $M_3 - M_4$, $M_5 - M_6$, and M_7 and comment on the specified device sizes.

[5]

M_1/M_2 - differential pair. Large $\frac{W}{L} \rightarrow$ large $g_m \rightarrow$ large $A_v(OM)$ [1]

M_3/M_4 - cascode \rightarrow minimize W.L \rightarrow minimize capacitance [1]

M_5/M_6 } current sources/sinks. Large $\frac{W}{L}$ to generate relatively large I_D for acceptable V_{GS} [1]

only about 1/2 students commented on device sizes. [1]

3. The circuit below in Fig. 3.1 illustrates a cascade of two identical common source stages.

 


Fig. 3.1

- a) Neglecting channel-length modulation and other capacitances, construct the Bode plot of V_{out}/V_{in} including both the magnitude and phase responses.

[8]

Assuming $\lambda = 0$ and neglecting other capacitances.


DC gain: $\frac{v_x}{v_{in}} = -g_{m1} R_D$

$\frac{v_{out}}{v_x} = -g_{m2} R_D$

$A_v = \frac{v_{out}}{v_{in}} = (g_m R_D)^2$ [1]

with 2 poles

@ $\frac{1}{R_D C_L}$ [1]

 

- b) Annotate your plot with the following: (i) Bandwidth; (ii) Phase margin; (iii) Gain Margin.

[5]

Also PM + GM annotated horizontally (in freq)

was not annotated correctly instead of BW \rightarrow GBP

- c) Derive the transfer function of the circuit, substitute $s = j\omega$, and obtain an expression for $|V_{out}/V_{in}|$. Determine the -3dB bandwidth of the circuit.

[10]

$$\frac{V_x}{V_{in}}(s) = -g_m(R_D \parallel \frac{1}{C_L s}) = -g_m \left(\frac{R_D}{R_D C_L s + 1} \right) \quad [1]$$

$$\frac{V_{out}}{V_x}(s) = -g_m \left(\frac{R_D}{R_D C_L s + 1} \right) \quad [1]$$

$$H(s) = \frac{V_x}{V_{in}}(s) \cdot \frac{V_{out}}{V_x}(s) = \left(\frac{g_m R_D}{R_D C_L s + 1} \right)^2 \quad [1]$$

$$s \rightarrow j\omega \quad H(j\omega) = \left(\frac{g_m R_D}{1 + R_D C_L j\omega} \right)^2$$

$$|H(j\omega)| = \frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2} \quad [1]$$

-3dB bandwidth:

$$\frac{(g_m R_D)^2}{1 + (R_D C_L \omega)^2} = \frac{(g_m R_D)^2}{\sqrt{2}} \quad [2]$$

$$\Rightarrow (R_D C_L \omega)^2 + 1 = \sqrt{2}$$

$$\Rightarrow \omega = \frac{\sqrt{\sqrt{2}-1}}{R_D C_L} = \frac{0.6436}{R_D C_L} \quad (\text{rad/s}) \quad [1]$$

$$2\pi f = \frac{0.6436}{R_D C_L} \Rightarrow f = \frac{0.1024}{R_D C_L} \quad (\text{Hz}) \quad [2]$$

most students missed these last steps.

i.e. Solving for -3dB BW

- d) Using your answers to parts (b) and (c), design the two-stage amplifier for a total voltage gain of 15 and -3dB bandwidth of 1.8GHz . Assume each stage carries a bias current of 1mA , $C_L=40\text{fF}$, and $\mu_n C_{ox} = 200\mu\text{A}/\text{V}^2$.

[7]

Bias current = 1mA (each stage)

$$C_L = 40\text{fF}$$

$$\mu_n C_{ox} = 200\mu\text{A}/\text{V}^2, A_v = 15, -3\text{dB} : 1.8\text{GHz}$$

$$\text{DC gain: } (g_m R_D)^2 = 15 \quad [1]$$

$$-3\text{dB BW: } \frac{0.16243}{R_D C_L} = 1.8\text{GHz} \quad [1]$$

$$\text{Since } C_L = 40\text{fF} \rightarrow R_D = 1422.6\Omega \quad [1]$$

$$(g_m R_D)^2 = 15 \Rightarrow g_m = 0.0027\text{S} = \frac{2I_D}{V_{GS} - V_{TH}} \quad [1]$$

$$\Rightarrow V_{GS} - V_{TH} = 0.741\text{V} \quad [1]$$

$$g_m = \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH}) \Rightarrow \frac{W}{L} = \frac{g_m}{\mu_n C_{ox} (V_{GS} - V_{TH})} = 18.2 \quad [1]$$

$$\therefore R_D = 1.42\text{k}\Omega$$

$$C_L = 40\text{fF}$$

$$V_{GS} - V_{TH} = 0.741\text{V}$$

$$\frac{W}{L} = 18.2$$

Method mostly ok. very few numerically correct answers.