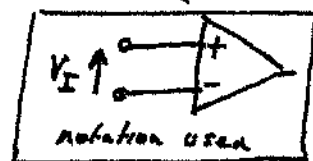


Answer 1


(a) (A) Resistors are irrelevant. Voltage V_I between input terminals (see sketch) is positive, therefore $V = +10$ volts

(B) Circuit is a voltage follower, hence $V = 2$ volts

(C) V_I is negative (-1 volt) hence $V = -10$ volts.



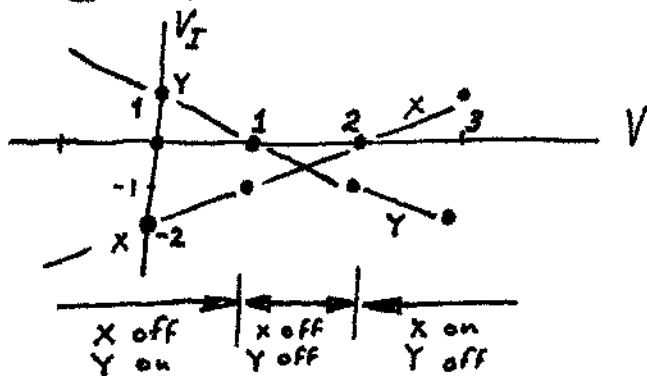(b) Plot V_I of opamps X and Y versus the voltage V :




which shows that when V is between 1 volt and 2 volts, the output voltages of both opamps are at -10 volts, and no current flows in the $10\text{ k}\Omega$ resistor


(c) The circuit is a Schmitt Trigger, with two stable states.

Assume $V_A = -10$ volts. By voltage divider action the voltage at the $+$ input is -6 volts. So as V decreases, $V_A \rightarrow 10$ volts as V reaches -6 volts. Therefore, with $V = -8\text{V}$, V_A must be at 10 volts. At that value of V_A the threshold voltage at the $+$ terminal is 6 volts. So the voltage V_A changes from $+10$ volts to -10 volts when V reaches 6 volts

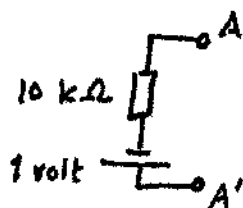
(d) To the left of AA' the Thevenin model is as shown immediately below:



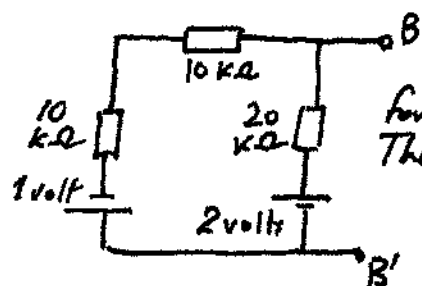
So that the circuit to the left of BB' is:



for which the Thevenin model is:

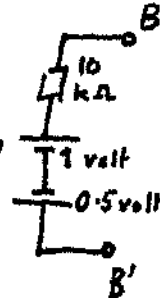


which when connected to the circuit to the right of BB' gives an inverting circuit:

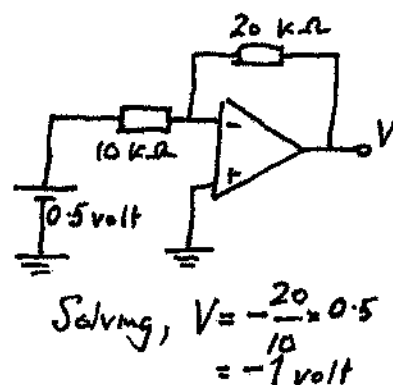


Answer 2

- (a) Left circuit: current in $1\text{ k}\Omega = (20-5)/1 = 15\text{ mA}$. Current in $2\text{ k}\Omega$ is $5/2 = 2.5\text{ mA}$.
Therefore current flows in Zener, $V=5\text{ volt}$. Power dissipation $= 5 \times (15-2.5)$
Middle circuit: Current in Zener $= 15\text{ mA}$, $V=5\text{ volts}$, Power dissipation $= 62.5\text{ mW}$
 $= 5 \times 15 = 75\text{ mW}$
Right circuit: If $V=5\text{ volts}$, current in 200Ω would be 25 mA , which exceeds that available through the $1\text{ k}\Omega$ resistor. Therefore zero current in Zener, Power dissipation $= 0$ and, by voltage divider action, $V = \frac{200}{1200} \times 20 = \frac{10}{3}\text{ volts}$.

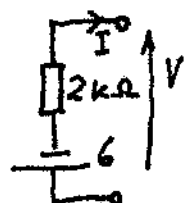- b) Thevenin Equivalent circuit to left of X is

whose current-voltage relation can be plotted on the same graph as for the device X.
Intersects at $V=0, I=-3\text{ mA}$
 $I=0, V=-6\text{ volts}$


See plot at right.

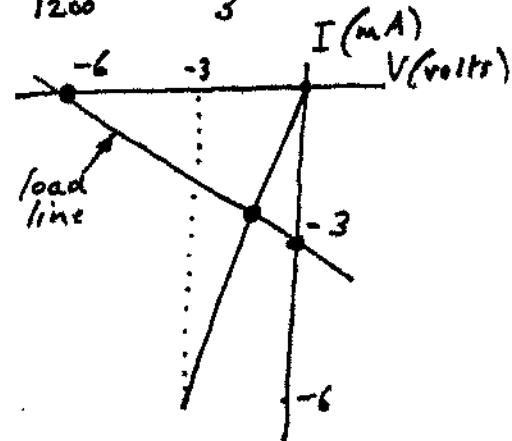Intersection occurs at $V=-2\text{ volts}$
 $I=-3\text{ mA}$




With reference to Figure 2b, if $V=-2$ then $V_A = 7\text{ volts}$.

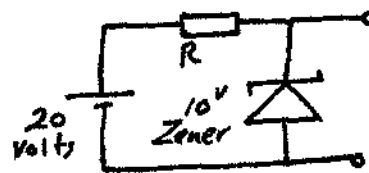- (c) Use the circuit shown at right, where the Zener diode has a Zener voltage of 10 volts .



When current drawn is 200 mA there must be at least 200 mA in R . We choose to have 220 mA flowing in R , giving $R = 10\text{ volts}/220\text{ mA} = 45\Omega$

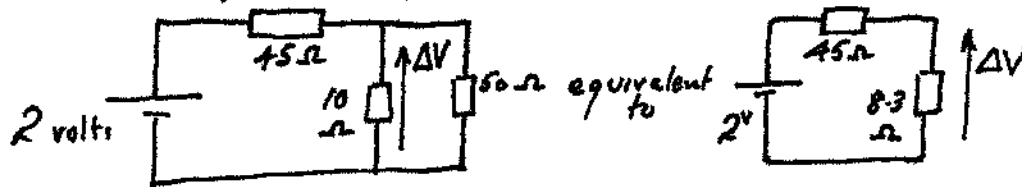- 2) If 200 mA is being drawn from the circuit, it corresponds to a resistance of 50 ohms . The required change circuit is therefore



giving $\Delta V = \frac{8.3}{53.3} \times 2 = 0.31\text{ volt}$

Thus, with a 2 volt variation in the 20 volt source there is a 0.31 volt change in the nominal voltage of 10 volts .

Answer 3



$$Z = R + j\omega L$$

$$(a) \quad Y = \frac{1}{Z} = \frac{1}{R + j\omega L}$$



$$Y = 1/R + j\omega C$$

$$Z = \frac{1}{Y} = \frac{R}{1 + j\omega CR}$$


$$(b) \quad (X) \quad V_o = \frac{V_{in}}{R_1 + \frac{1}{j\omega C}} \times R_2 \quad (Y) \quad V_o = \frac{V_{in}}{R_1} \times (R_2 + j\omega L) \quad (Z) \quad V_o = \frac{V_{in}}{R_1} \times \frac{R_2}{1 + j\omega CR_2}$$

$$\frac{V_o}{V_{in}} = \frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{1}{j\omega CR_1}} \quad \frac{V_o}{V_{in}} = \frac{R_2}{R_1} \cdot (1 + j\omega L/R_2) \quad \frac{V_o}{V_{in}} = \frac{R_2}{R_1} \cdot \frac{1}{1 + j\omega CR_2}$$

$$(c) \quad \omega \rightarrow 0 \quad \left| \frac{V_o}{V_{in}} \right| \rightarrow \omega CR_2 \quad \omega \rightarrow 0 \quad \left| \frac{V_o}{V_{in}} \right| \rightarrow \frac{R_2}{R_1} \quad \omega \rightarrow 0 \quad \left| \frac{V_o}{V_{in}} \right| \rightarrow \frac{R_2}{R_1}$$

$$\omega \rightarrow \infty \quad \left| \frac{V_o}{V_{in}} \right| \rightarrow \frac{R_2}{R_1} \quad \omega \rightarrow \infty \quad \left| \frac{V_o}{V_{in}} \right| \rightarrow \frac{\omega L}{R_1} \quad \omega \rightarrow \infty \quad \left| \frac{V_o}{V_{in}} \right| \rightarrow \frac{1}{\omega CR_1}$$

Log-log plots are as follows:

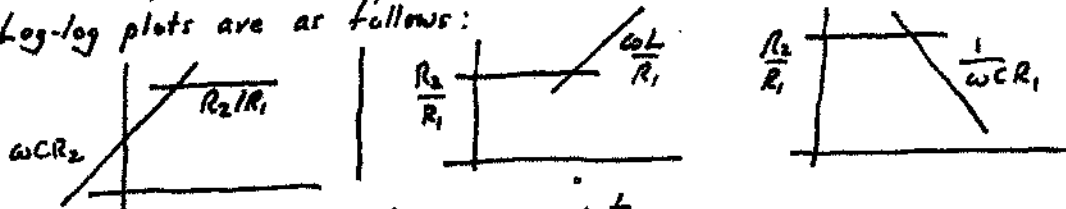

and correspond to

(A)

(B)

(C)


(d) See the log-log plots of (c) above. Asymptote intersections are given by

$$(X) \quad \omega = \frac{1}{CR_1}$$

$$(Y) \quad \omega = \frac{R_2}{L}$$

$$(Z) \quad \omega = \frac{1}{CR_2}$$

(e) Suggested circuit is:

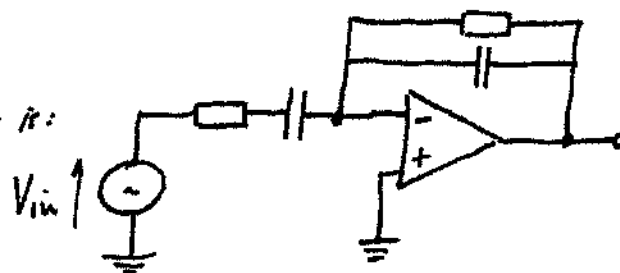


Bioengineering Exam First Year 2016 Electrical Engineering

Answer 4



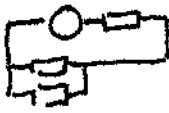Parallel connection of $6k\Omega$ and $3k\Omega$ equivalent to $2k\Omega$. By Ohm's Law, $V = 6$ volts. Hence $I = 6/3 = 2$ mA



By Ohm's Law, $V = -4$ volts. Parallel connection of $6k\Omega$ and $3k\Omega$ is equivalent to $2k\Omega$, so voltage across $3k\Omega$ is $2 \times 2 = 4$ volts and current through $3k\Omega$ is $4/3$ mA (1.33 mA)




By Ohm's Law, current in $17k\Omega$ is $-(20-3)/17 = -1$ mA
 $V = -17$ volts.




Whatever the voltage across the source, voltage divider ensure that $V = 0$.
Parallel connection of $10k\Omega$ and $20k\Omega$ is equivalent to $200/30 k\Omega$ so voltage across the source will be $(200/30) \times 3 = 20$ volts so that $I = 2$ mA


(b) With only 10^v source

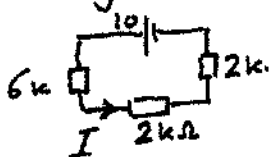

current in horizontal $2k\Omega$ is 1 mA

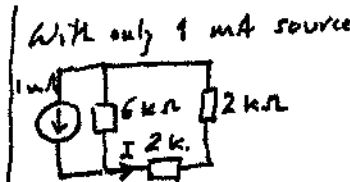

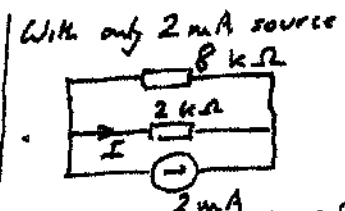
Parallel connection of $6k\Omega$ and $4k\Omega$ is $2.4k\Omega$ so voltage across $2.4k\Omega$ is 2.4 volts and $I = \frac{2.4}{4} = 0.6$ mA



Parallel connection of $8k\Omega$ and $2k\Omega$ is $1.6k\Omega$ so voltage across the $2k\Omega$ is 3.2 volts and $I = -\frac{3.2}{2} = -1.6$ mA

Therefore, by Superposition,

$$I = 1 + 0.6 - 1.6 = 0 \text{ mA}$$

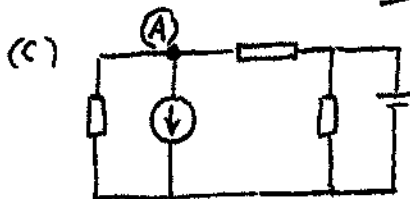


KCL at (A) (out) gives $\frac{V_A}{10} + \frac{(V_A-5)}{2} + 0.2(5-V_A) = 0$
which simplifies to $V_A = 15/4$ volts.

(d) To find V_{oc} due to 9 volts




No current in $2k\Omega$ so $V_{oc} = 6$ volts (A more positive)

To find V_{oc} due to 2 mA

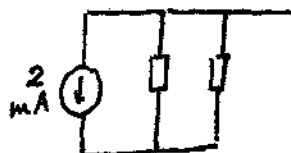

$6k\Omega$ and $3k\Omega$ in parallel equivalent to $2k\Omega$ so $V_{oc} = 4$ volts (A more positive)

To find R_0

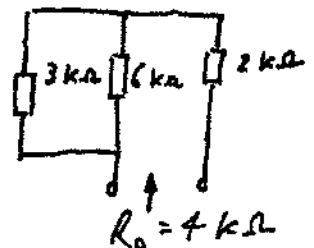

$R_0 = 4k\Omega$

\therefore Actual $V_{oc} = 10$ volts (by Superposition)

So the Thevenin model is

