

# Analogue Electronics II (E2-2) — SOLUTION


① (a) (i) Circuit shown is a "digital" inverter. Should identify ① that this is in fact two CS amps.

$\therefore A_V = -G_m R_{out}$  where  $G_m = g_{m1} + g_{m2}$

② or  $G_m = 2g_{m1}$  (assuming  $g_{m1}$ 's are matched)

$R_{out} = r_{o1} \parallel r_{o2}$

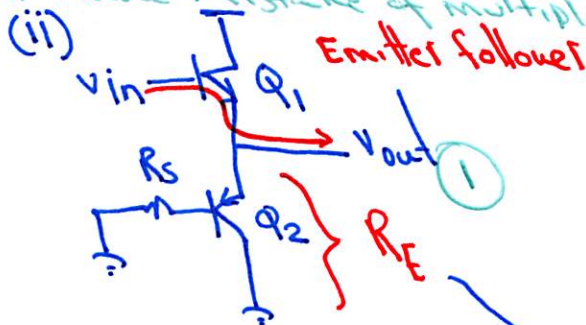most students realised this was 2 CS amplifiers in parallel but several made mistake of multiplying  $g_m$ s instead of adding




from formula sheet

$A_V = \frac{R_E \parallel r_o}{\frac{1}{g_m} + R_E \parallel r_o}$  ①

from formula sheet

$R_E = \frac{1}{g_m} + \frac{R_S}{\beta + 1}$  ①

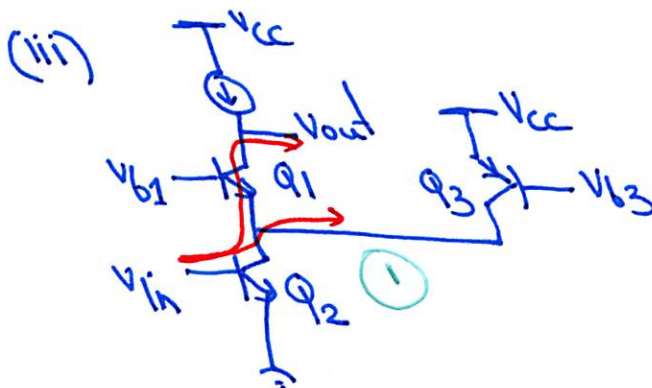$\therefore A_V = \frac{\left(\frac{1}{g_{m2}} + \frac{R_S}{\beta + 1}\right) \parallel r_{o1}}{\left(\frac{1}{g_{m2}} + \frac{R_S}{\beta + 1}\right) \parallel r_{o1} + \frac{1}{g_{m1}}}$  ②



use  $A_V = -G_m R_{out}$

for  $G_m \rightarrow v_{in} = v_{be2}$

$i_{out} \neq i_{c2}$

$\therefore$  need  $\frac{i_{out}}{i_{c2}} \rightarrow$  current splitter

$G_m = \frac{r_{o2} \parallel r_{o3}}{r_{o2} \parallel r_{o3} + \frac{1}{g_{m1}}} (g_{m2})$  ②

$R_{out} = g_{m1} r_{o1} (r_{o2} \parallel r_{o3} \parallel r_{\pi1}) + r_{o1} + (r_{o2} \parallel r_{o3} \parallel r_{\pi1})$  ②






(c) answer well

Direct coupling is when amplifier stages are directly cascaded and thus biasing is all dependent. ①  
In IC design large capacitors are undesirable ∴ capacitive coupling is undesirable for LF signals. ①



In capacitive coupling each amplifier stage is independently biased and subsequent stages are cascaded using an AC coupling capacitor. ①

(capacitive coupling)

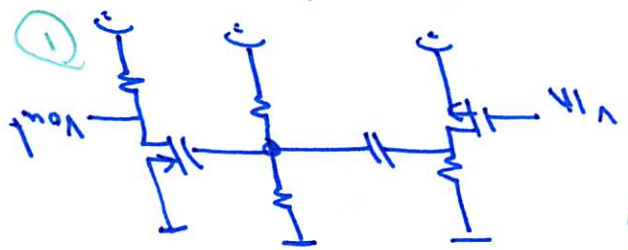


(c)


(Direct coupling)

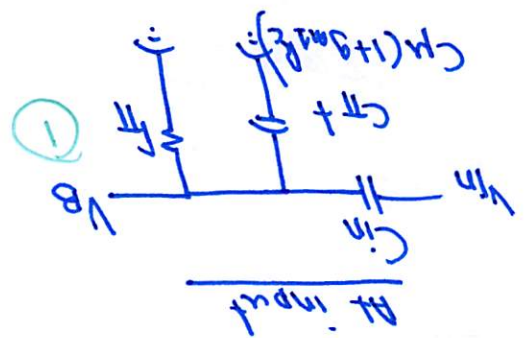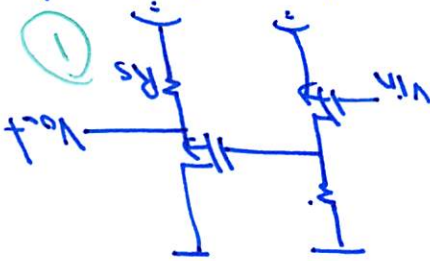


At input

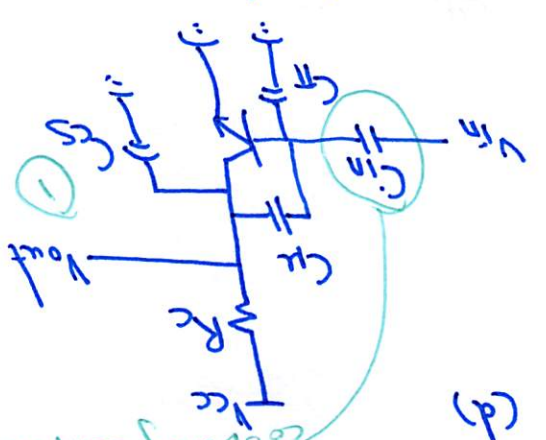

(d)

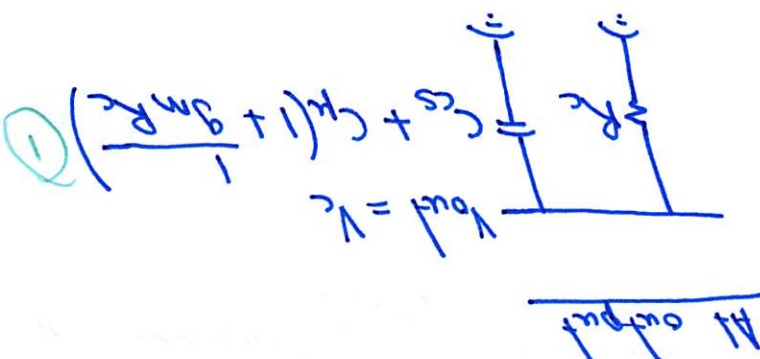


At output

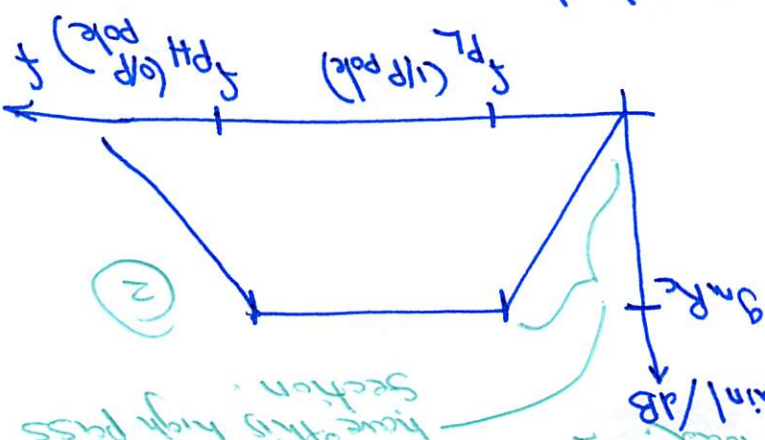

Coupling capacitors did not have this high pass section. ②  
C<sub>in</sub> was in many cases not series coupling but parallel load. ②

② (a) Since input = current }  $\therefore$  Transimpedance amplifier (units of gain = Ohms) }  $\left. \begin{array}{l} \text{is} \\ \text{of} \\ \text{to} \end{array} \right\}$   
 output = voltage  
 ideally  $R_{in} = \infty$ ,  $R_{out} = \infty$ .

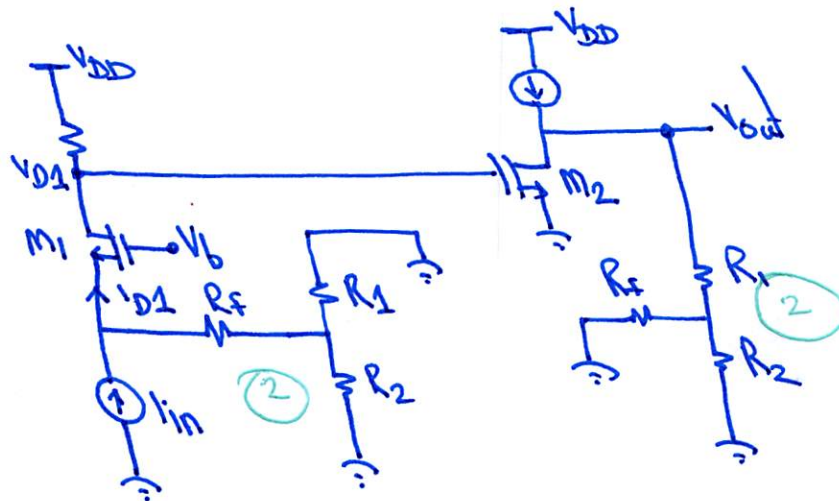(b) (i) To determine open loop gain, i.e.  $\left( \frac{V_{out}}{I_{in}} \right)_{OL}$  need to break feedback loop.



$$A_{OL} = \frac{V_{out}}{I_{in}} = \frac{I_{D1}}{I_{in}} \times \frac{V_{D1}}{I_{D1}} \times \frac{V_{out}}{V_{D1}}$$

$$\frac{I_{D1}}{I_{in}} = \frac{(R_F + R_1 \parallel R_2)}{(R_F + R_1 \parallel R_2) + 1/g_{m1}}$$


several students assumed  $I_{in} = I_{D1}$

$$V_{D1} = I_{D1} R_{D1}$$

$$\frac{V_{out}}{V_{D1}} = -g_{m2} (R_{D2} \parallel (R_1 + R_F \parallel R_2))$$

$$\therefore A_{OL} = -g_{m2} [R_{D2} \parallel (R_1 + R_F \parallel R_2)] R_{D1} \frac{R_F + R_1 \parallel R_2}{\frac{1}{g_{m1}} + R_F + R_1 \parallel R_2}$$

(ii)

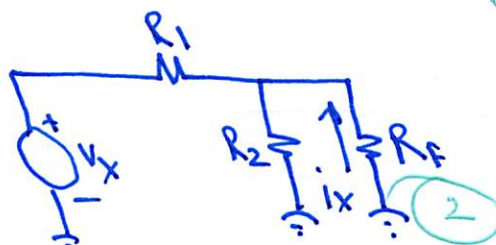

$$K = \frac{V_x}{V_x}$$

generally macromodel provided by most



$$\frac{V_y}{V_{in2}-V_{in1}} = -g_{m1}(r_{o2}||r_{o4}) \quad (\text{assuming good matching})$$

$$(b) A_v = \frac{V_{out}}{V_{in2}-V_{in1}} = \frac{V_{out}}{V_z} \times \frac{V_z}{V_y} \times \frac{V_y}{V_{in2}-V_{in1}}$$

$$\therefore P_{total} = 23.85 \text{ mW} \quad \text{---} \text{ } \textcircled{2} \text{ ---} \text{ most obtained correct value.}$$

$$\therefore I_{total} = I_{ref} (1+4+8+40) = 0.25 \text{ mA} (53) = 13.25 \text{ mA}$$

$$\text{from } \frac{W}{L} \text{ ratio } (I_{ref}: I_{D7}: I_{D8}: I_{D9}) = 1:4:8:40$$

$$I_{total} = I_{ref} + I_{D7} + I_{D8} + I_{D9} \quad \textcircled{2}$$

$$\textcircled{3} (a) P_{total} = V_{DD} \times I_{total}$$

$$R_{out, closed} = \frac{1 + A_{OL}K}{r_{o2} || (R_1 + R_2 || R_F)} \quad \textcircled{2}$$

$$R_{in, closed} = \frac{1 + A_{OL}K}{\frac{1}{g_{m1}} || (R_F + R_1 || R_2)} \quad \textcircled{2}$$

few shaded got complete, correct expressions

$$1 + A_{OL}K =$$

$$\left\{ \frac{R_2 || R_F}{R_F (R_1 + R_2 || R_F)} \right\}$$

$$(iv) \frac{V_{out}}{V_{in}} = - \frac{g_{m2} [r_{o2} || (R_1 + R_2 || R_F)] R_{D2} \frac{1}{g_{m1}} + R_1 || R_2}{R_F + R_1 || R_2} \quad \textcircled{3}$$

$$R_{out, open} = r_{o2} || (R_1 + R_2 || R_F) \quad \textcircled{2}$$

$$(iii) R_{in, open} = \frac{1}{g_{m1}} || (R_F + R_1 || R_2) \quad \textcircled{3}$$

assured very well

$$K = \frac{V_x}{V_y} = \frac{-R_2}{-R_2 || R_F} = \frac{R_F (R_1 + R_2 || R_F)}{-R_2 || R_F} \quad \textcircled{3}$$

about 1/2 student got this

$$\frac{v_z}{v_y} = -g_{m5}(r_{o5} \parallel r_{o8})$$

$$\frac{v_{out}}{v_z} = \frac{r_{o6} \parallel r_{o9}}{r_{o6} \parallel r_{o9} + 1/g_{m6}}$$

$$\therefore A_v = g_{m1} g_{m5} (r_{o2} \parallel r_{o4}) (r_{o5} \parallel r_{o8}) \frac{r_{o6} \parallel r_{o9}}{r_{o6} \parallel r_{o9} + 1/g_{m6}} \quad (5)$$

answered  
very well

$$g_{m1} = \sqrt{2 \mu_n C_{ox} \left(\frac{W}{L}\right)_1 I_{D1}} = \sqrt{2 (200 \mu) (250) (0.5 \text{ mA})} = 7.07 \text{ mS}$$

$$g_{m5} = \sqrt{2 (100 \mu) 50 (2 \text{ mA})} = 4.47 \text{ mS}$$

$$g_{m6} = \sqrt{2 (200 \mu) 50 (10 \text{ mA})} = 14.14 \text{ mS}$$

$$r_{o2} = \frac{1}{\lambda_n I_{D2}} = \frac{1}{(0.1) (0.5 \text{ mA})} = 20 \text{ k}\Omega$$

$$r_{o4} = \frac{1}{(0.2) (0.5 \text{ mA})} = 10 \text{ k}\Omega$$

$$r_{o5} = \frac{1}{(0.2) (2 \text{ mA})} = 2.5 \text{ k}\Omega \quad r_{o6} = \frac{1}{(0.1) (10 \text{ mA})} = 1 \text{ k}\Omega$$

$$r_{o8} = \frac{1}{(0.1) (2 \text{ mA})} = 5 \text{ k}\Omega \quad r_{o9} = \frac{1}{(0.1) (10 \text{ mA})} = 1 \text{ k}\Omega$$

or incorrect  
expression  
but generally  
some rounding errors  
most followed correct method

$$A_v = (7.07 \text{ mS}) (4.47 \text{ mS}) (20 \text{ k}\Omega \parallel 10 \text{ k}\Omega) (2.5 \text{ k}\Omega \parallel 5 \text{ k}\Omega) \frac{1 \text{ k}\Omega \parallel 1 \text{ k}\Omega}{1 \text{ k}\Omega \parallel 1 \text{ k}\Omega + \frac{1}{14.14 \text{ mS}}} \\ = 293.65 = 49.36 \text{ dB} \quad (2)$$

$$(c) R_{out} = \frac{1}{g_{m6}} \parallel r_{o6} \parallel r_{o9} = \frac{1}{14.14 \text{ mS}} \parallel 1 \text{ k}\Omega \parallel 1 \text{ k}\Omega = 61.96 \Omega \quad (2)$$

(d) Nodes in signal path:  $v_{in1}, v_{in2}, v_x, v_y, v_{out}, v_z$

However can exclude low  $Z$  nodes (source connections) such as  $v_x, v_{out}$ . (1)

$\therefore$  Remaining high  $Z$  nodes  $v_y$  and  $v_z$

many incorrectly  
identified  $v_{out}$   
as high  $Z$




Although method followed correctly by many, either due to selecting wrong nodes, or incorrect calculation of capacitances, final pole frequencies were incorrect. Most students however received credit for correct method.

$$f_{py} = \frac{1}{2\pi R_y C_y} = 17.82 \text{ MHz}$$


$$= 1.34 \text{ pf}$$

$$C_y = C_{d4} + C_{d2} \left(1 - \frac{1}{A_{v2}}\right) + C_{d5} + C_{d3} (1 - A_{v5}) = 0.5f(5) + 20f(250)(21) + 20f(50)(1) + 0.5f(50)(1+1.45)$$
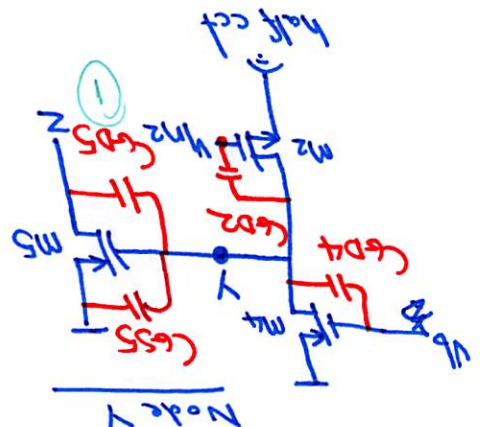
$$R_y = r_{o4} \parallel r_{o2} = 10k\Omega \parallel 20k\Omega = 6.6k\Omega$$



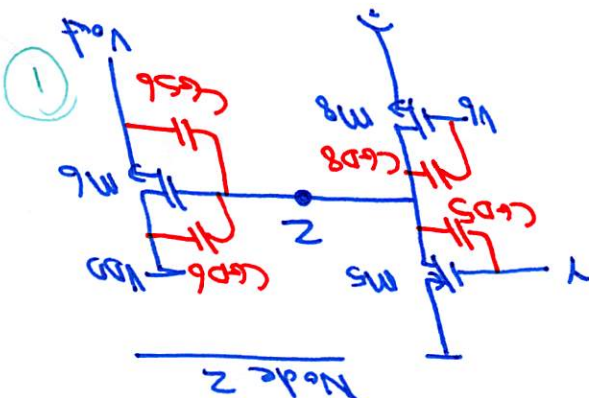(e) Need to determine RCs of nodes Y and Z.



$$R_z = r_{o5} \parallel r_{o8} = 2.5k\Omega \parallel 5k\Omega = 1.6k\Omega$$

$$C_z = C_{d5} \left(1 - \frac{1}{A_{v5}}\right) + C_{d8} + C_{d6} + C_{d3} (1 - A_{v6}) = 0.5f(50) \left(1 + \frac{1}{1.45}\right) + 0.5f(16) + 0.5f(50) + 20f(50)(1-0.98)$$

$$= 178 \text{ fF}$$

$$f_{pz} = \frac{1}{2\pi R_z C_z} = 536.69 \text{ MHz}$$