

IMPERIAL COLLEGE LONDON

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING  
EXAMINATIONS 2009

MSc and EEE PART III/IV: MEng, BEng.and ACGI

**ANALOGUE INTEGRATED CIRCUITS AND SYSTEMS**

Wednesday, 13 May 10:00 am

Time allowed: 3:00 hours

Corrected Copy

Q6

**There are SIX questions on this paper.**

**Answer FOUR questions.**

*All questions carry equal marks*

**Any special instructions for invigilators and information for candidates are on page 1.**

Examiners responsible	First Marker(s) :	C. Toumazou
	Second Marker(s) :	E. Rodriguez-Villegas

1. (a) Voltage and current-sources are key components in analogue circuit design. Sketch a typical band-gap voltage reference circuit and prove that the temperature coefficient of the output voltage  $V_o$  is zero if  $V_o = 1.283$  V. Assume the temperature coefficient of  $V_{BE}$  to be  $-2.5\text{mV}/^\circ\text{C}$ , Boltzmann's constant  $k = 1.38 \times 10^{-23}$  J/K and electron charge  $q = 1.6 \times 10^{-19}$  C.
- (b) Calculate the fractional temperature coefficient for the constant current generator of Figure 1.1 at room temperature, given that  $R$  is a polysilicon resistor with a temperature coefficient of  $1500$  ppm/ $^\circ\text{C}$ .
- (c) Explain qualitatively why the four-transistor voltage potential divider of Figure 1.2 can have smaller chip area than an equivalent two-transistor voltage potential divider with the same power consumption.

[11]

[5]

[4]

 


Figure 1.1

**This question is continued on page 2.**

 


Figure 1.2

2.

- (a) A fundamental limitation imposed on the Dynamic Range (DR) of any high performance A/D converter will ultimately be switch noise. Prove that the fundamental limit is given by,

$$DR = \frac{V_{ref}}{\sqrt{(10kTRf_c)}}$$

where  $V_{ref}$  is the reference voltage,  $k$  is the Boltzmann's constant,  $T$  is absolute temperature,  $R$  is switch resistance and  $f_c$  is the clock frequency of the switch. You may assume that the system settles in  $10\tau$  (where  $\tau$  is the time constant), over one period of the clock frequency.

[8]

- (b) A very high resolution analogue-to-digital converter is the oversampling converter sometimes referred to as the sigma-delta modulator. Sketch a typical architecture for such a converter and explain its principles of operation, in particular the feedback noise shaping mechanism.

[12]

3. (a) Sketch typical circuit diagrams for a two-stage cascoded and a single-stage CMOS op-amp. Explain why the single-stage design has potentially much higher bandwidth than the two-stage design and in particular why it is not necessary to Miller compensate the single-stage architecture. Give one advantage and one disadvantage of the cascoded op-amp. [8]
- (b) Estimate the low-frequency differential voltage gain, and, gain-bandwidth product of the two-stage CMOS op-amp shown in Figure 3.1. Aspect ratios of all devices are shown on the circuit. Assume all bulk effects are negligible. Device model parameters are given below. [10]
- (c) Explain qualitatively why the addition of a load capacitor to the output of a two-stage op-amp degrades amplifier stability, whereas an additional load capacitor connected to the output of a single-stage op-amp improves amplifier stability. [2]

#### CMOS TRANSISTOR PARAMETERS

MODEL PARAMETERS	$K_p (\mu A/V^2)$	$\lambda (V^{-1})$	$V_{T0} (V)$
PMOS	20	0.03	-0.8
NMOS	30	0.02	1.0

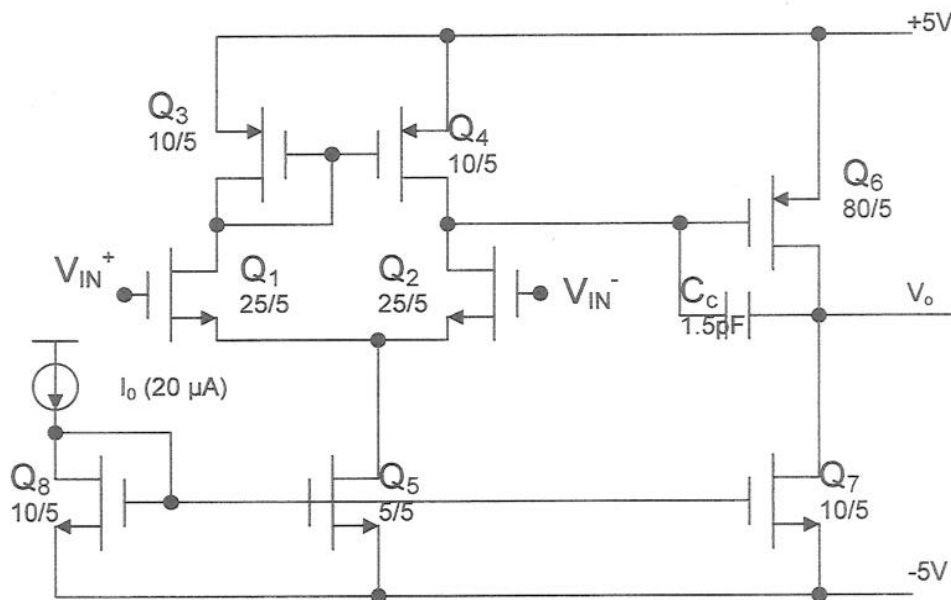


Figure 3.1

4. (a) Give one advantage and one disadvantage of each of the two CMOS current mirror circuits shown in Figures 4.1 and 4.2 [6]
- (b) For the current mirror of Figure 4.2 derive this voltage swing in terms of device threshold voltage  $V_T$ , clearly stating any assumptions you make. [7]
- (c) With the aid of a macromodel, explain the theoretical concept of current feedback and how it results in constant bandwidth application. [7]

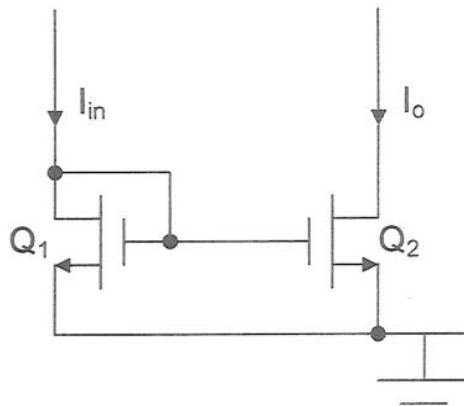


Figure 4.1

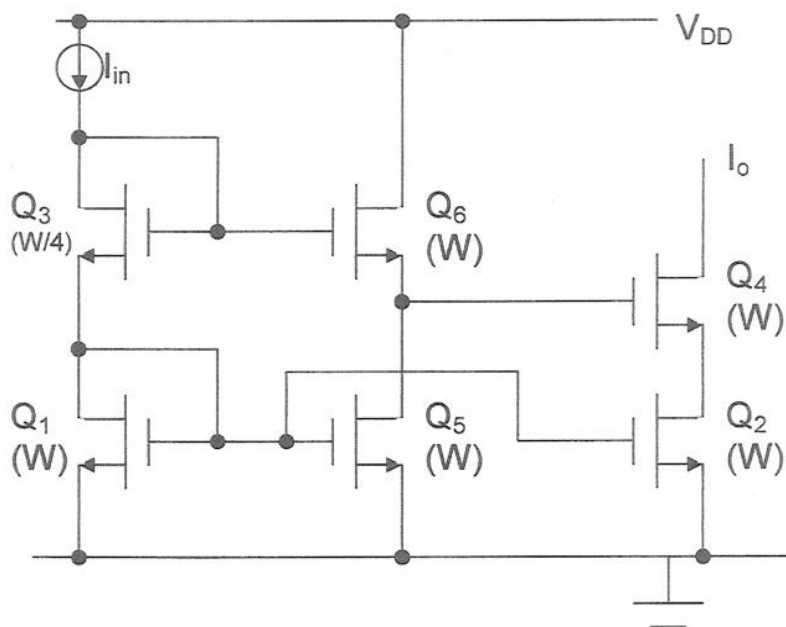


Figure 4.2

5. (a) Sketch the circuit for a differential switched-capacitor integrator and derive an expression for its transfer function.

[10]

- (b) Figure 5.1 shows one section of a switched capacitor ladder filter. Based on this filter structure, design a 3<sup>rd</sup>-order Chebyshev low-pass filter with a cut-off frequency of 5 kHz and a 1.0 dB pass band ripple. Assume a clock frequency of 100 kHz. Passive component values for the LC prototype, normalised to 1 rad/s, are  $C_1 = C_3 = 2.0236$ ,  $L_2 = 0.994$ . In your analysis assume all integrators to be lossless.

[10]

 


Figure 5.1

6. (a) Under what operating conditions does the MOSFET of Figure 6(a) realise a linear floating resistor between terminals A and B? Show that under these conditions the equivalent resistance  $R_{AB}$  can be approximated by

$$R_{AB} = \frac{L}{KW(V_{GS} - V_T)}$$

stating any assumptions. All symbols have their usual meaning.

[5]

- (b) Discuss three sources of non-linearity in the single MOSFET resistor realisation of Figure 4(a) and suggest one suitable circuit design to help eliminate one or more of these non-linear terms showing the necessary circuit analysis to confirm your design.

[5]

- (c) For the current mirror of Figure 6(b), derive the expression for minimum output voltage while still maintaining saturated devices. Derive this voltage in terms of device threshold voltage  $V_T$  clearly stating any assumptions you make.

[4]

- (d) Sketch a regulated cascode current-source and explain why the output resistance of the current source is higher than that of a standard cascode mirror.

[6]

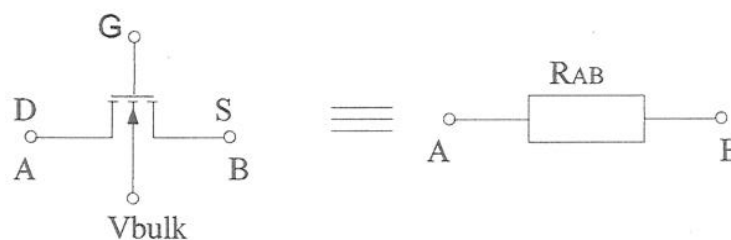


Figure 6(a)

 


Figure 6(b)



2009 - EXAM

E3.01

AC1

3rd Year / MSc

Analogue Integrated Circuits  
and Systems.

E3.01 / AC1

SOLUTIONS


1st Marker

C. Tournaton

2nd Marker

E. Rodriguez

Q1

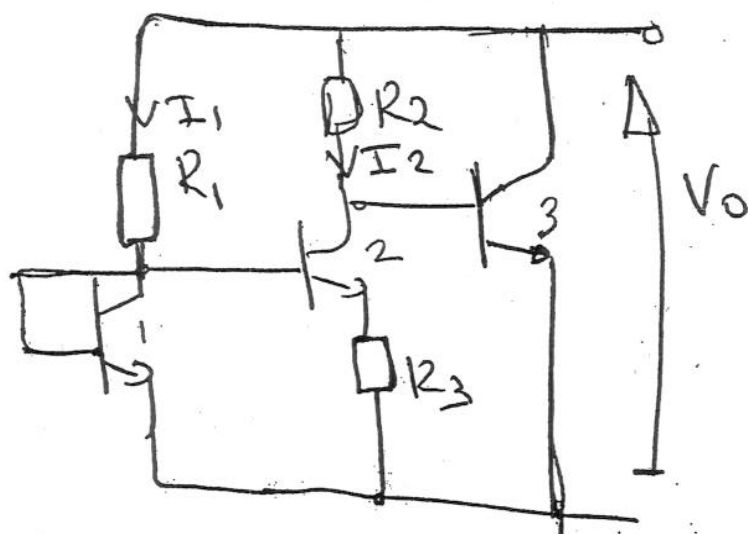

Bandgap.

1/18

5/5

$$V_{BE1} = V_{BE2} + I_2 R_3$$

$$\beta \gg 1$$

Since  $V_{BE1} - V_{BE2} = V_T \ln(I_1/I_2)$   
 Then  $V_0 = V_{BE3} + R_2/R_3 V_T \ln(I_1/I_2)$   
 $V_T \ln(I_3/I_2) \rightarrow$  assume  
 Now - temp

For  $dV_0/dT = 0$ , then  $dV_{BE3}/dT$   
 $= \frac{V_T}{T} \frac{R_2}{R_3} \ln\left(\frac{I_1}{I_2}\right)$

Since  $\frac{dV_{BE}}{dT} = -2.5 \text{ mV}/^\circ\text{C}$ ,  $\frac{V_T}{T} = \frac{1.38 \times 10^{-23}}{1.6 \times 10^{-19}}$

Then  $\left(\frac{R_2}{R_3}\right) \ln\left(\frac{I_1}{I_2}\right) = 29$  and so

$$V_0 = 1.283 \text{ V}$$

For PTAT temperature coefficient of  $V_T$  cancels with negative temp coefficient of Resistor

5/5

$$\therefore T_{CF} = \frac{1}{V_T} \frac{\partial V_T}{\partial T} - \frac{1}{R} \frac{\partial R}{\partial T}$$

$$= \frac{1}{T} - 1500 \times 10^{-6} @ \text{Room } T = 1833 \text{ ppm/}^\circ\text{C}$$

|||||


Figure 1(b).

Since  $I = \frac{KW}{2L} (V_{GS} - V_T)^2$

Then if  $V_{GS}$  is small  $\approx V_T$   
 When  $(W/L)$  large.

If  $V_{GS} \gg V_T$   
 When  $(W/L)$  small  
 Small  $(W/L)$  gives large chip area

 2(c)  
 $\therefore$  Two transistor P.D  
 has larger  $V_{GS}$  / transistor  
 than four transistor P.D has same  
 supply.




4/4

# Q2 / Constraint

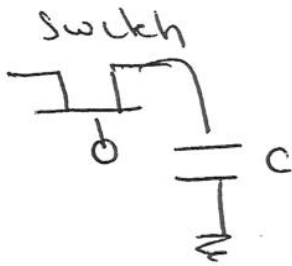Q2 2

a.) Dynamic Range  $\Delta V_{ref}/noise = 2^N$



Rms noise of switch  
driving Capacitor  
 $= \sqrt{\frac{kT}{C}}$


$$\therefore DR = \frac{V_{ref}}{\sqrt{\frac{kT}{C}}} = 2^N$$

Assume  $f_c = 1/(10RC)$

then solving for C gives

$$DR = 2^N = V_{ref} / \sqrt{kT \cdot 10RC}$$

b)

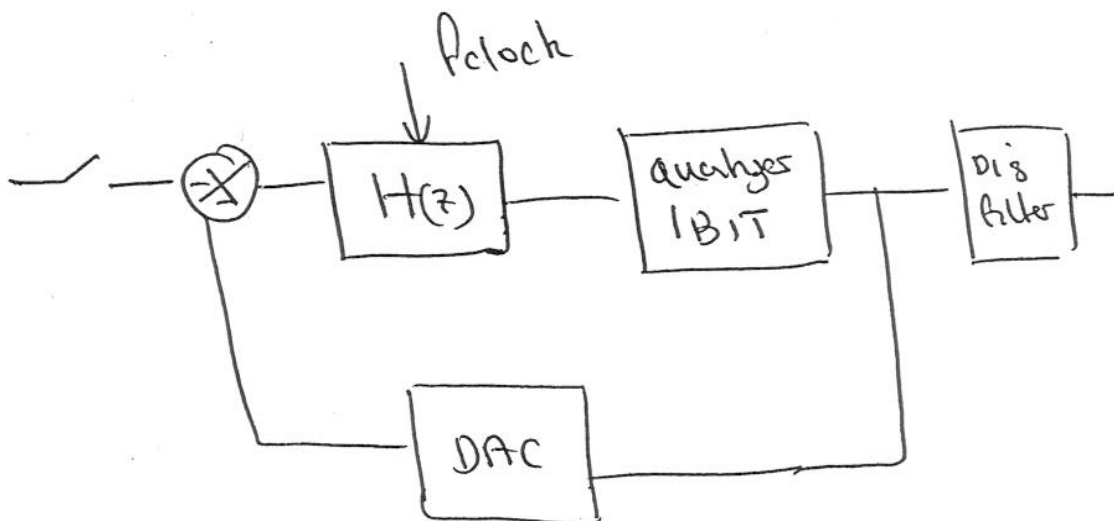

Basic idea is that coarse quantization noise gets shaped by  $1/(H(z))$  via feedback

8/8



p. 3  
Ct

Generally  $H(z)$  is an Integrator so noise is shaped differentially. This reduces requirements upon component accuracy.

The architecture includes a negative feedback loop producing the coarse estimate that oscillates about the true value of input, the digital filter averages this coarse estimate to produce a finer approximation.

The feedback DFE and forward integrator force the quantization error to have a high frequency spectrum. The output of the digital filter is downsampled and gives a multibit digital representation. High frequency quantization noise is reduced. Noise shaped away using  $(S/N)$  at low frequency.

Q3.

 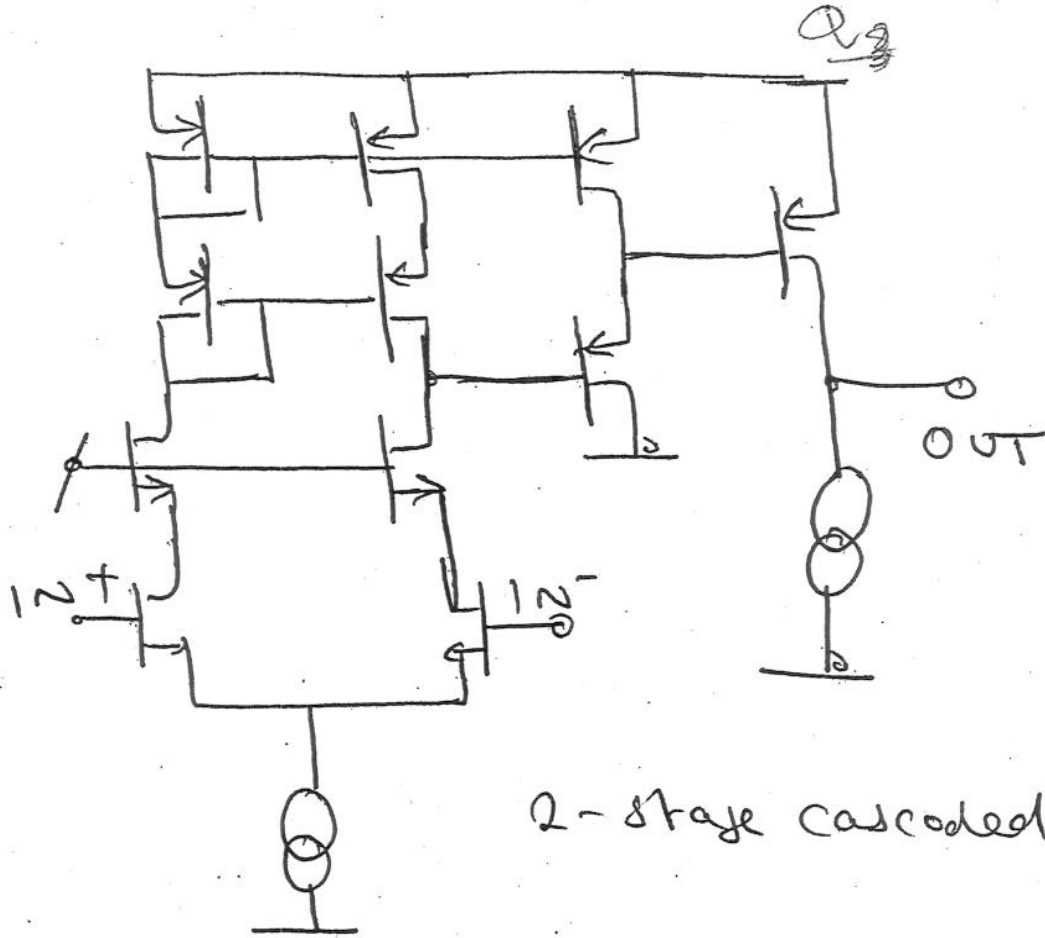

single-stage.

3/3

3/3

40.10M

In a single-stage the main high impedance node is at the output. Compensation is then provided via a load capacitor at the output. The internal poles at the lower impedance nodes are now secondary and will only affect the phase margin of the amplifier.

In a two-stage design, the requirement for a single high internal impedance to achieve voltage gain means that the amplifier requires internal frequency (Miller) compensation to be stable. Because of this compensation the bandwidth is reduced.

(2/2) The main advantage of a cascaded op-amp is voltage gain, the main disadvantage is CMVR or signal swing limitations.

Op-Amp

(3/2) 
$$A_{v1} = -g_{m2} / (g_{o2} + g_{o4})$$
$$(g_{o2} + g_{o4}) = I_{D2} (-10^{-7} - 1p) =$$
$$5 \times 10^{-6} \times 0.05 = 2.5 \times 10^{-7} \text{ mho}$$

(2/2) 
$$g_{m2} = 2 \sqrt{\beta_2 I_D} \Rightarrow \beta_2 = \frac{k_n}{2} \left( \frac{W}{L} \right)_2 = 7.5 \times 10^{-5} \text{ A/V}$$

$$g_{m2} = 3.87 \times 10^{-5} \text{ S}, \quad A_1 = -154.9$$

$$A_2 = -g_{m6} / (g_{o7} + g_{o6})$$

Q3-Cont

$$(g_{o6} + g_{o7}) = I_{D6} (\lambda_{np} + \lambda_n) = 20 \times 10^{-6} \times 0.05 \\ = 10 \times 10^{-7} \Omega^{-1}$$

(3/2)

$$g_{m6} = 2 \sqrt{\beta_6 I_{D6}} \Rightarrow \beta_6 = \frac{I_{D6}}{2} \left( \frac{W}{L} \right)_6 = 1.6 \times 10^{-4} \text{ A/V}$$

$$g_{m6} = 1.13 \times 10^{-4}, A_2 = 113$$

$$A_{\text{total}} = A_1 A_2 = 17503$$

(2/2)

$$G.B.P = g_{m2} / 2\pi f_c = 4.1 \text{ MHz}$$

- In 2-stage load is 2nd Pole hence  
reducing load increases stability  
with single stage load forms dominant pole  
hence reducing load increases bandwidth

(2/2)



Qn 4/.

a)

Fig 4.1 - Simple mirror

Advantages - High frequency  
- High output swing

② Disadvantage - very inaccurate

Fig 4.2 - High swing cascode

Advantage - Higher output swing than cascode

② Disadvantage - Complex, poor frequency performance.

Figure 4.3 - Regulated cascode

Advantage - Highest output swing  
Highest output resistance

Disadvantage - inaccuracy of input  
current - mirror

- feedback leading  
to potential instability.


②

6/6

Qn 4 cont.

output Swing

Current includes all saturation Voltages

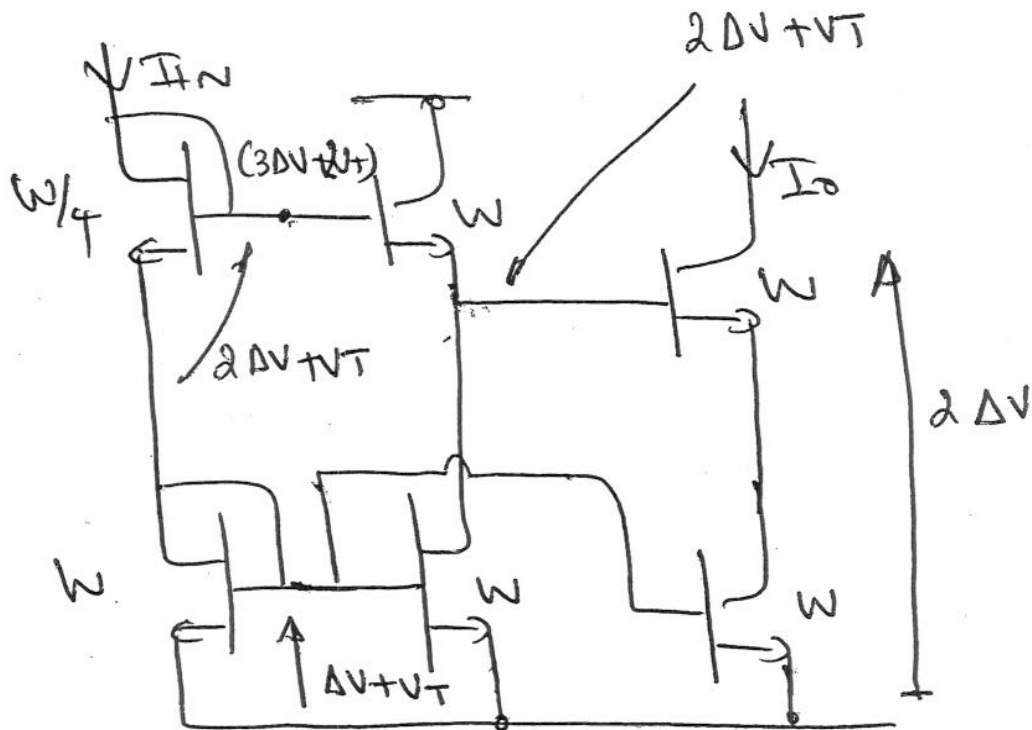

Assuming equal  $L$ 's

$$I_O = I_{IN}$$

$$\beta_1 = \beta_2 = \beta_4 \quad \beta_5 = \beta_6 = \beta$$

$$\beta_3 = \beta/4$$

$$\therefore V_{sat} = 2(V_{GS} - V_T)$$


NOTE  $\Delta V = (V_{GS} - V_T)$

Swing  $2\Delta V$

(7/7)

Que 4 cont

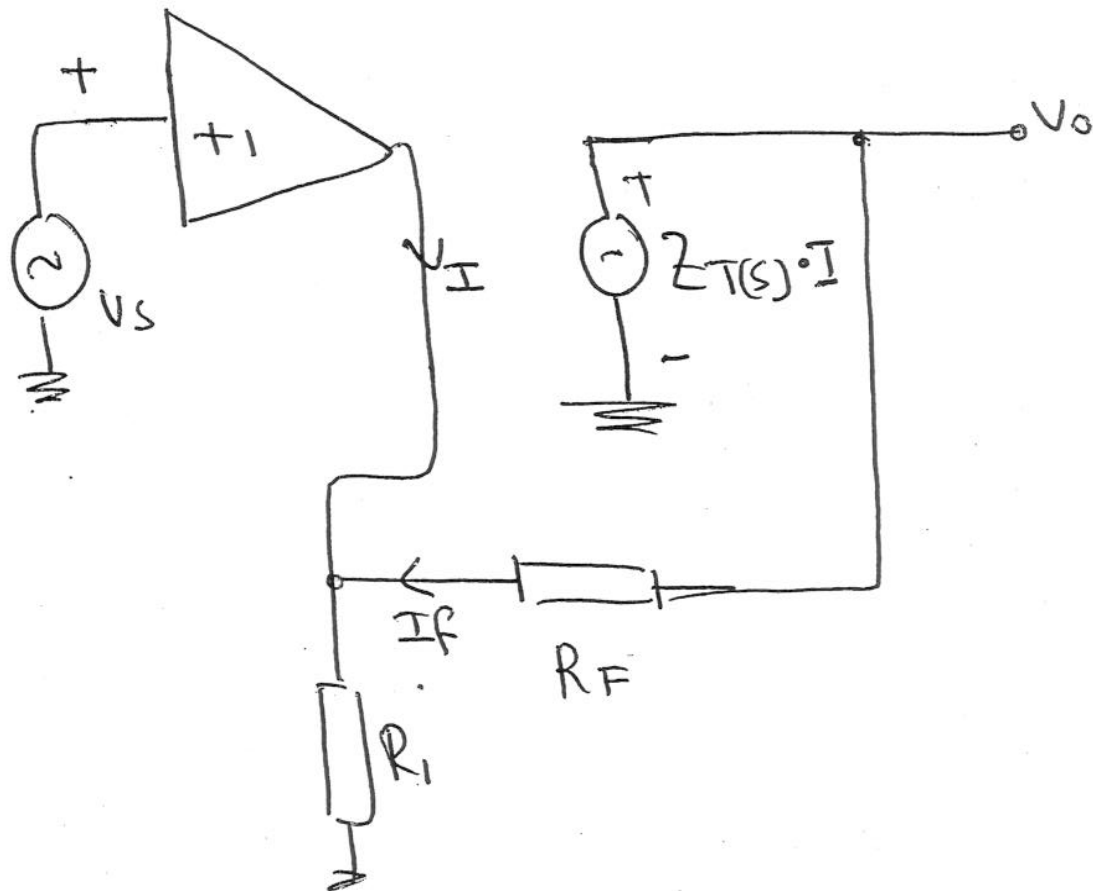macromodel of Current-feedback op-amp.  
c).



$$Z_T(s) = Z_{T0} / (1 + s\tau / \omega_p) \Rightarrow \text{hp dominant Pole}$$

From model

$$I_f = (V_o - V_s) / R_F$$

$$I_i = V_s / R_i$$

$$V_o = Z_T(s) I = Z_T(s) (I_i - I_f)$$

From above

$$(V_o / V_s) = (1 + R_F / R_i) \left[ \frac{Z_T(s)}{R_F + Z_T(s)} \right]$$

Qm4 cont.

substitute  $Z(s)$ s, and assume  $Z_{T0} \gg R_F$

$$\left( \frac{V_o}{V_s} \right)_{j\omega} = \left( 1 + \frac{R_F}{R_1} \right) \left[ \frac{Z_{T0}}{Z_{T0} + R_F} \right] \left( \frac{1}{1 + jf / \frac{R_F}{R_F} \left( \frac{Z_{T0} + R_F}{R_F} \right)} \right)$$

Assume  $Z_{T0} \gg R_F$

$$\left( \frac{V_o}{V_s} \right)_{j\omega} = \left( 1 + \frac{R_F}{R_1} \right) \frac{1}{1 + jf / \frac{GB}{R_F}}$$

where  $G.B = f_p Z_{T0}$

$$f_{p \text{ closed}} = \underline{\underline{G.B / R_F}} \Rightarrow \text{determined by } R_F$$

Gain determined by  $R_1$

$$\underline{\underline{A_c = \left( 1 + \frac{R_F}{R_1} \right)}}$$


(7/7)

Ans

(11)

Ans/

a) Differential Integrator

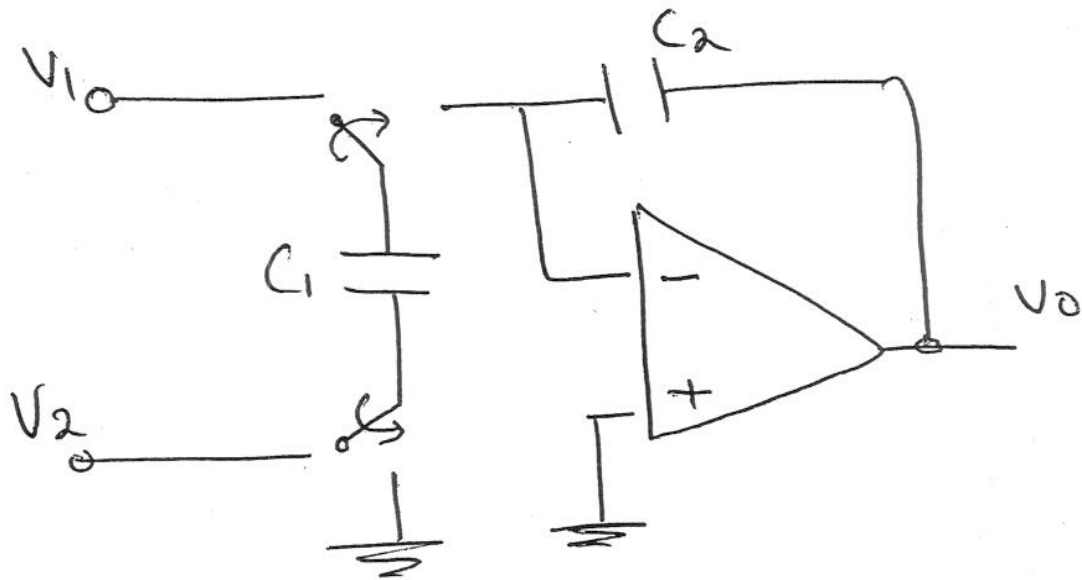

During  $\phi_1$  :  $Q = C_1 [V_1 - V_2]$

$$I_{av} = f_c C_1 [V_1 - V_2]$$

$f_c$  = clock frequency

During  $\phi_2 \Rightarrow I_{av} = -f_c (V_1 - V_2) C_1$

$$\therefore V_0 = \frac{-1}{j\omega C_2} f_c C_1 [V_1 - V_2]$$


$$\therefore \frac{V_0}{(V_1 - V_2)} = -\frac{f_c}{j\omega} \frac{C_1}{C_2} \approx T = \frac{C_1}{C_2} f_c$$

(5/5)

p. 12  
✓

Ques 2

## Lossy Integrator

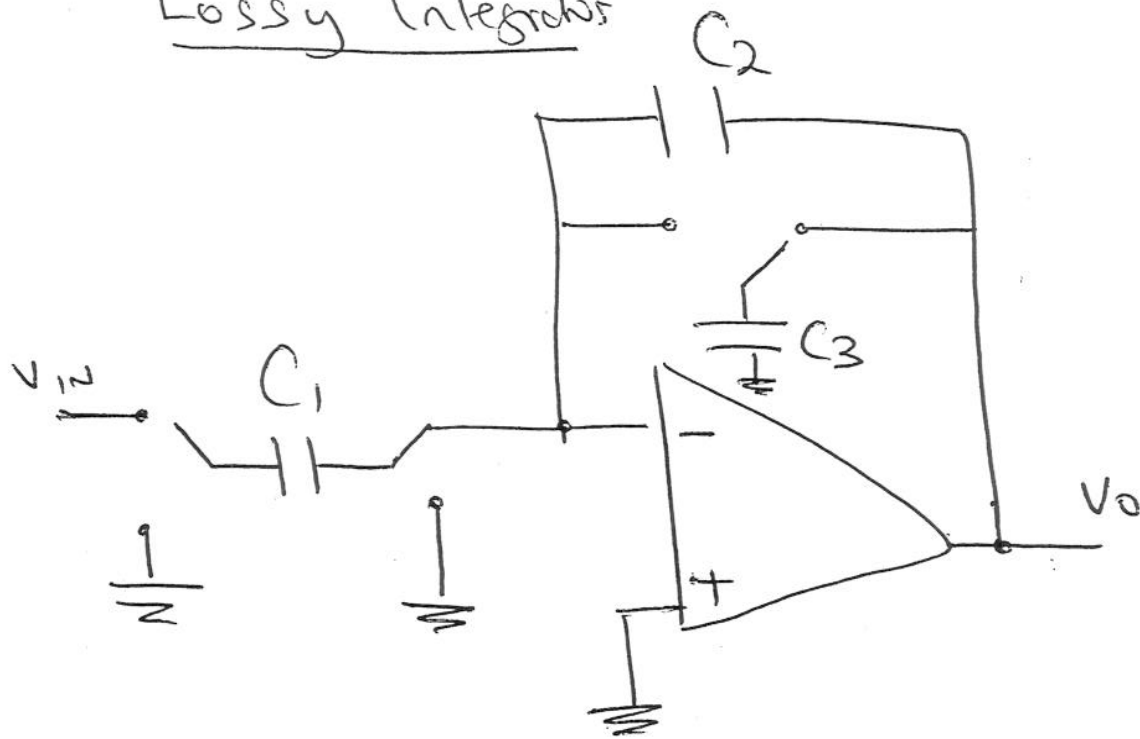

During  $\phi_1$   $Q = C_1 V_{IN} \Rightarrow I_{avg} = f_c C_1 V_{IN}$

During  $\phi_2$

$$I_{avg} = -[f_c (C_3 V_O + j\omega C_2 V_O)]$$

$$\therefore f_c C_1 V_{IN} = -[f_c (C_3 V_O + j\omega C_2 V_O)]$$


$$V_{IN} = -\left[ \frac{C_3}{C_1} V_O + \frac{j\omega C_2 V_O}{C_1 f_c} \right]$$

5/s  $\therefore \frac{V_O}{V_{IN}} = -\frac{C_1}{C_3} \left( \frac{1}{1 + \frac{C_2 j\omega}{C_3 f_c}} \right)$


$$\therefore T = \left( \frac{C_2}{C_3} \right) \frac{1}{f_c}$$

p.13

Q4 5 (cont)  
section of LCR prototype.

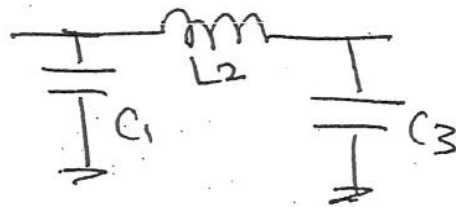

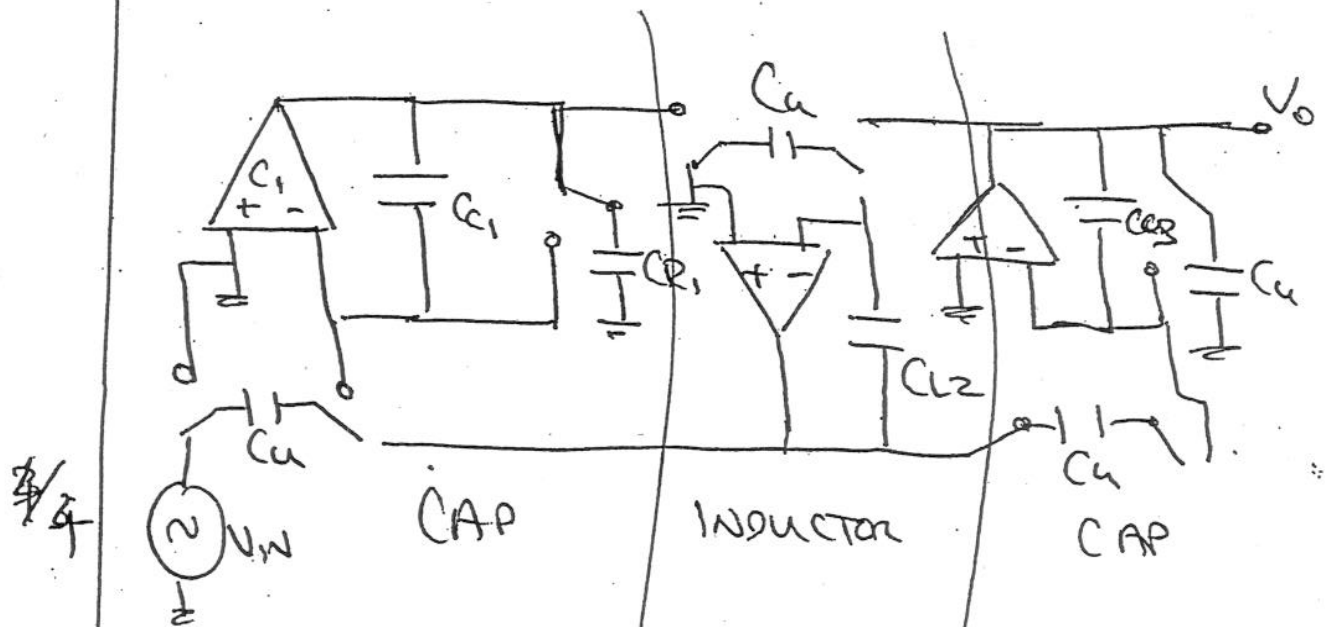General transformation Rules (not really required but the bright students may include)



Conversion into differential integrators.

Inductor transformation

$$(L_2/R_s) f_c = C_{12}/C_u$$

Capacitor Transformation

$$C_3/C_u = f_c R_s C_3$$

where \$R\_s\$ is normalising dummy scaling resistor. Assuming \$R\_s = 1\$

$$\left. \begin{aligned} C_1/C_u &= f_c C_1 \\ C_3/C_u &= f_c C_3 \\ C_{12}/C_u &= f_c L_2 \end{aligned} \right\} \text{general transformation}$$

Qu5 cont

Table values of  $C_1$ ,  $L_2$  and  $C_3$   
are normalized to  $1 \text{ rad/s} \div 2\pi f_p$

$$f_p = 5 \text{ kHz}$$

$$C_1 = C_3 = 2.0236 / (2\pi 5 \times 10^3) \\ = 6.44 \times 10^{-5} \text{ F}$$

$$C_{L2} = 0.994 / (2\pi 5 \times 10^3) \\ = 3.164 \times 10^{-5} \text{ F}$$

For termination  $R_s$

assume  $C_{u1} = C_{r1} = C_{r0} = 1 \text{ pF}$

Then

$$\left[ \begin{array}{l} C_{L1} = C_{L3} = 6.44 \text{ pF} \\ C_{L2} = 3.164 \text{ pF} \end{array} \right]$$

6/6

toom 20/20



Q6 /

Assumption is that if  $(V_{DS} \geq 0)$  or  $(V_{DS} < (V_{GS} - V_T))$  device acts in linear region. From

$$I_D = \frac{\mu_n C_{ox}}{L} \left[ (V_{GS} - V_T) V_{DS} - \frac{V_{DS}^2}{2} \right] \left[ 1 + \lambda V_{DS} \right]$$

for  $V_{DS} \ll (V_{GS} - V_T)$ , then  $\lambda V_{DS} \ll 1$

$$\text{so } I_D = \frac{\mu_n C_{ox}}{L} (V_{GS} - V_T) V_{DS}$$

$$\text{OR } R_{AB} = V_{DS} / I_D = L / (\mu_n C_{ox} (V_{GS} - V_T)) \quad 5$$

Three sources of Non-linearity

(i) Limited due to  $V_{GS}$  change  $V_T$

for negative  $V_{GS}$  due to body-effect.

$$\text{i.e. } V_T = V_{T0} + \gamma \left[ \sqrt{-V_{BS} - 2\phi_F} - \sqrt{2\phi_F} \right]$$

$\gamma$  = bulk threshold parameter

$\phi_F$  = Fermi-level potential

(ii) Limited due to  $V_{DS}$  approaching

$(V_{GS} - V_T)$  hence saturation region


for large positive  $V_{DS}$ .

(iii) For large values of  $V_{DS}$  the


$V_{DS}^2/2$  term introduces large

Non-linearity.

Q.6 cont.

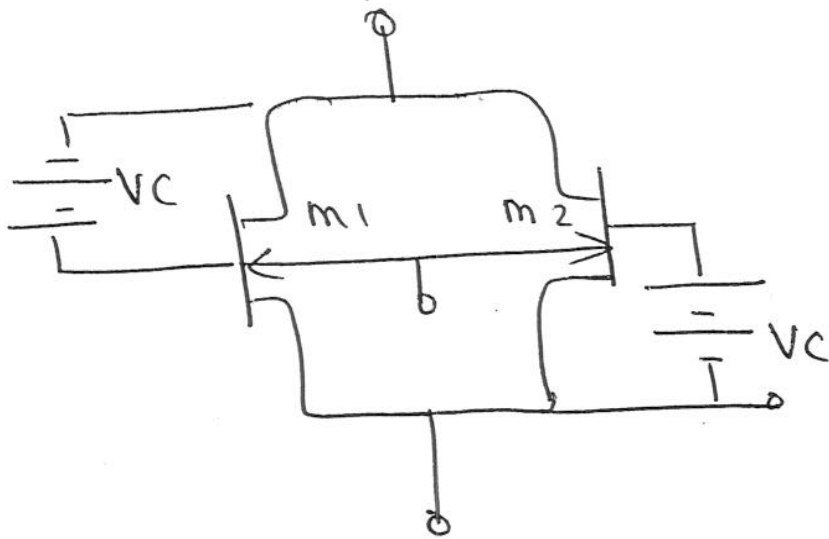


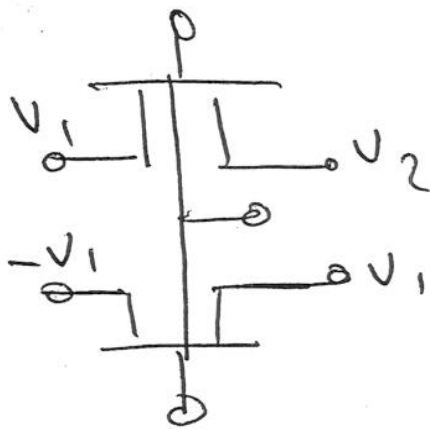Parallel current - eliminates  $V_{DS}^2/2$  term.



Differential scheme

Effects of  $V_{DS}$  cancelled.

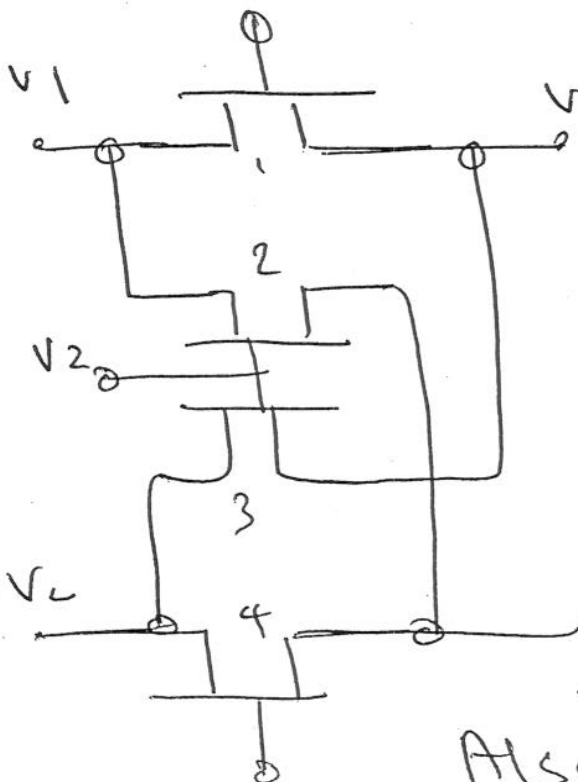

Double differential MOS

Eliminates

$-V_{DS}$  and  $V_T$  term


Any one will do

Also expect analysis of particular cell.

2

p17.  
Et

Q6 cont.

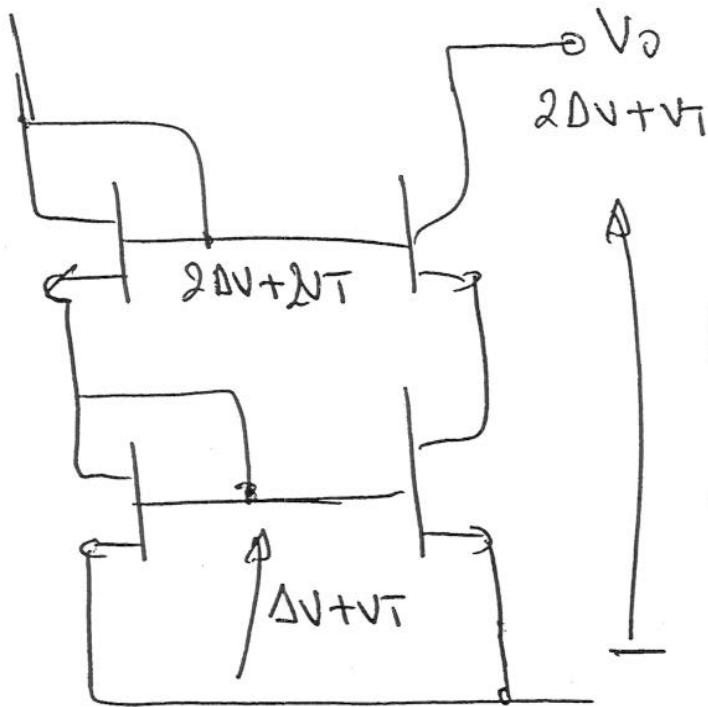


Assume  
 $\Delta V = V_{GS} - V_T$   
 For Sat  
 $V_{DS} \geq V_{GS} - V_T$

$$(V_O)_{mn} = 2(\Delta V + V_T) - V_T$$

$$= \underline{2\Delta V + V_T}$$

4

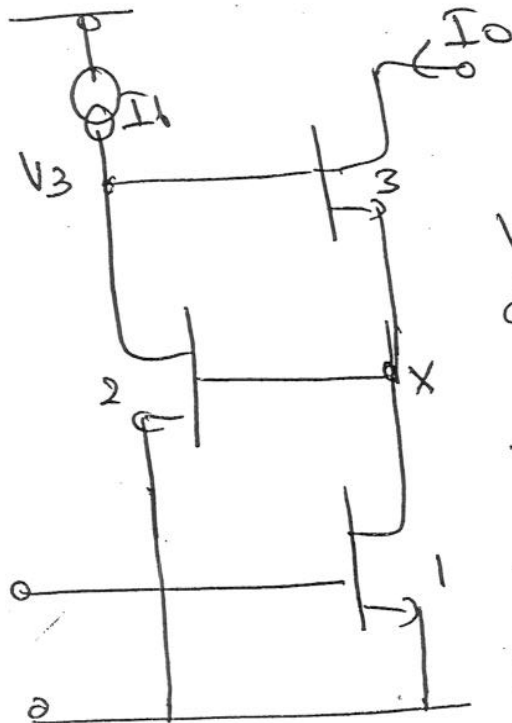

Q3 cascodes Q1  
 hence output resistance  
 due to Q3 is  
 $R_{O3} \approx r_{ds1} \parallel g_{m3} r_{ds3}$

Transistor Q2 senses  
 Change in voltage at  
 node (X) and  
 reduces these changes  
 by the loop gain

6

of the amplifier (Q2 and Q4) hence this further  
 increases the output resistance of the circuit to  
 $R_{out} = R_{O3} \parallel g_{m2} r_{ds2} \parallel g_{m3} r_{ds3} r_{ds1} \approx (g_{m2}^2 / g_{o3})$   
 Assume equal  $\Delta V$  and  $Q_{01}$ .

P. 18.  
 (T)