

E1.2 Digital Electronics 1
Solutions 2008

All questions are unseen.

Answer to Question 1 (Compulsory)

a) i)

$$\begin{aligned}
 & ABC + \bar{A}CD + \bar{B}CD \\
 &= C(AB + \bar{A}D + \bar{B}D) \\
 &= C(AB + D(\bar{A} + \bar{B})) \\
 &= C(AB + \overline{ABD}) \\
 &= C(AB + D) \\
 &= ABC + CD
 \end{aligned}$$

[4]

ii)

$$\begin{aligned}
 & AB + (C + \bar{B})(AB + \bar{C}) \\
 &= AB + C(AB + \bar{C}) + \bar{B}(AB + \bar{C}) \\
 &= AB + ABC + \bar{B}\bar{C} \\
 &= AB(1 + C) + \bar{B}\bar{C} \\
 &= AB + \bar{B}\bar{C}
 \end{aligned}$$

[4]

b)

YZ					
		00	01	11	10
X	0	0	1	1	0
	1	1	1	0	1

$$\begin{aligned}
 & F(X, Y, Z) \\
 &= \bar{X}Z + X\bar{Z} + X\bar{Y} \quad \text{or} \\
 &= \bar{X}Z + X\bar{Z} + \bar{Y}Z
 \end{aligned}$$

[4]


c)

CD					
		00	01	11	10
AB	00	1	1	0	1
	01	0	1	0	0
	11	0	0	0	0
	10	1	1	0	1

$$F = (\bar{A} + \bar{B})(\bar{C} + \bar{D})(\bar{B} + D)$$

[4]

d)

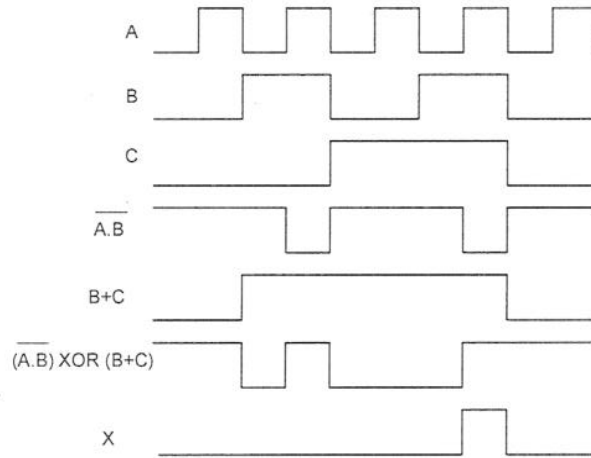

[4]


e)

Binary	Hexadecimal	Unsigned Decimal	Signed Decimal	ASCII
0100 0110		70		'F'
	D4	212	-44	

2 marks each.


[8]

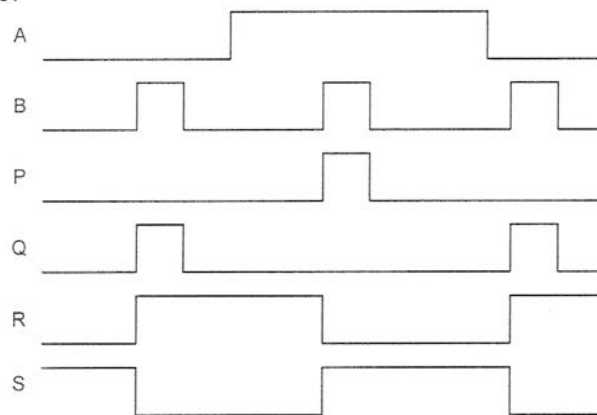- f) P is reset input (high active), and Q is set input to the flip-flop (R=1 is set state). The two AND gates and the inverter forms a steering circuit, steering the clock pulse on B depending on value of A. When A is high, the clock pulse is steered to reset input and when A is low, the clock pulse is steered to the set input. Hence the waveforms are:



[6]

g)

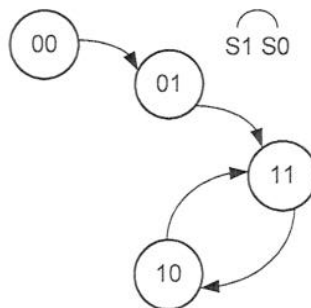

[6]

Answer to Question 2

a)

PQ					
B _{in}		00	01	11	10
		D			
0		0	1	0	1
1		1	0	1	0

PQ					
B _{in}		00	01	11	10
		B _{out}			
0		0	1	0	0
1		1	1	1	0

$$D = \bar{P}\bar{Q}B_{in} + P\bar{Q}\bar{B}_{in} + \bar{P}Q\bar{B}_{in} + PQB_{in} \quad B_{out} = \bar{P}Q + B_{in}Q + B_{in}\bar{P}$$

[8]

b) Need to express both equations as NOR or inverter functions only:


$$\begin{aligned} D &= \bar{P}\bar{Q}B_{in} + P\bar{Q}\bar{B}_{in} + \bar{P}Q\bar{B}_{in} + PQB_{in} \\ &= \overline{\overline{\bar{P}\bar{Q}B_{in}} + \overline{P\bar{Q}\bar{B}_{in}} + \overline{\bar{P}Q\bar{B}_{in}} + \overline{PQB_{in}}} \\ &= \overline{\overline{\bar{P}\bar{Q}B_{in}} + \overline{P\bar{Q}\bar{B}_{in}} + \overline{\bar{P}Q\bar{B}_{in}} + \overline{PQB_{in}}} \\ &= \overline{(P + Q + \bar{B}_{in}) + (\bar{P} + \bar{Q} + B_{in}) + (P + \bar{Q} + B_{in}) + (\bar{P} + \bar{Q} + \bar{B}_{in})} \end{aligned}$$

[4]

$$\begin{aligned} B_{out} &= \bar{P}Q + B_{in}Q + B_{in}\bar{P} \\ &= \overline{\overline{\bar{P}Q} + \overline{B_{in}Q} + \overline{B_{in}\bar{P}}} \\ &= \overline{\overline{\bar{P}Q} + \overline{B_{in}Q} + \overline{B_{in}\bar{P}}} \\ &= \overline{(P + \bar{Q}) + (\bar{B}_{in} + \bar{Q}) + (\bar{B}_{in} + P)} \end{aligned}$$

[4]


c)

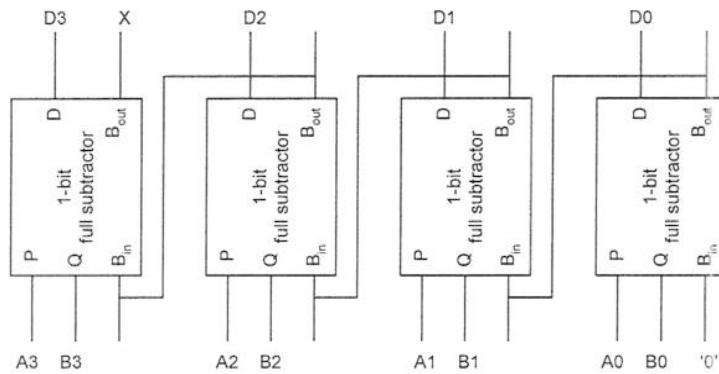

$$X = \text{Borrow_out from MSB} = (B > A)$$

[8]

d)

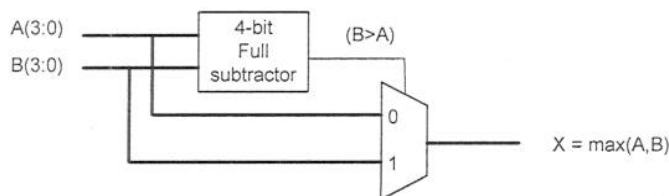

[6]


Answer to Question 3

a)

$$\begin{aligned} Z &= (D\bar{C} + 1 \bullet C)\bar{B} + (D\bar{A} + 1 \bullet A)B \\ &= (D + C)\bar{B} + (D + A)B \\ &= \bar{B}D + \bar{B}C + BD + AB \\ &= AB + BC + D \end{aligned}$$


[10]

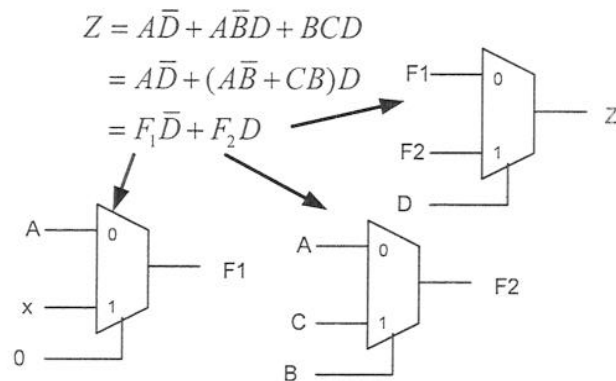b) Need to express the Boolean equation in the form: $Z = F_1\bar{D} + F_2D$




Hence to implement the required equation, we want:
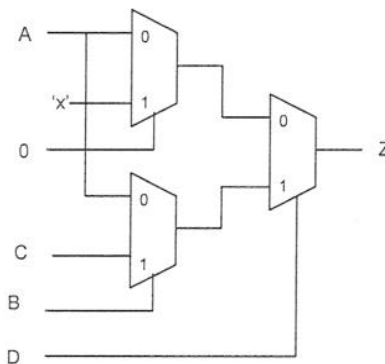
$$A0 = B0 = A, A1 = 'x', SA = '0', B1 = C, SB = B, S = D$$



[10]

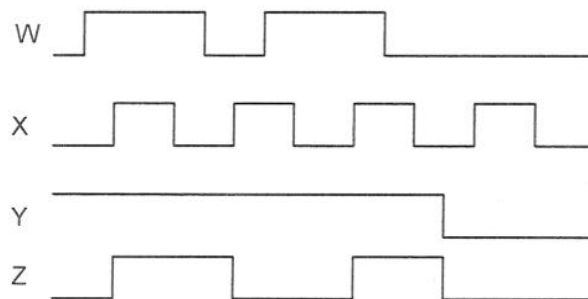c) This is a positive edge trigger D flip-flop, with asynchronous clear. Data input = W, clock input is X, clear control is Y.



[10]

Answer to Question 4

a)

A	B	X	NextA	NextB	Y
0	0	0	0	0	0
0	0	1	0	1	1
0	1	0	1	0	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	0
1	1	1	0	0	0

[6]

b)

		AB			
NextA		00	01	11	10
X	0	0	1	1	1
	1	0	0	0	1
		AB			
NextB		00	01	11	10
X	0	0	0	1	0
	1	1	1	0	1
		AB			
Y		00	01	11	10
X	0	0	0	0	0
	1	1	0	0	1

$\text{NextA} = \overline{B}X + A\overline{B}$
 $\text{NextB} = \overline{A}X + \overline{B}X + AB\overline{X}$
 $Y = \overline{B}X$

[14]

c)

This new encoding (known as one-hot encoding) allows very simple implementation of next state equations and outputs. By inspection:

$$\text{NextS1} = \text{S0 } X$$

$$\text{NextS2} = \text{S1 } X$$

$$\text{NextS3} = \text{S2 } X$$

$$\text{Next S0} = \text{S3 } X$$

$$Y = \text{S0 } X + \text{S2 } X$$

[10]